

**Md. Abdul Malek**

Assistant Professor, Dept. of Electrical & Electronic Engineering (EEE)

Rajshahi University of Engineering & Technology (RUET)

# Nodal Analysis


Nodal analysis provides a procedure for analyzing circuits using node voltages as the circuit variables.

## Steps to Determine Node Voltages:

1. Select a node as the reference node. Assign voltages  $v_1, v_2, \dots, v_{n-1}$  to the remaining  $n - 1$  nodes. The voltages are referenced with respect to the reference node.
2. Apply KCL to each of the  $n - 1$  nonreference nodes. Use Ohm's law to express the branch currents in terms of node voltages.
3. Solve the resulting simultaneous equations to obtain the unknown node voltages.

# Nodal Analysis

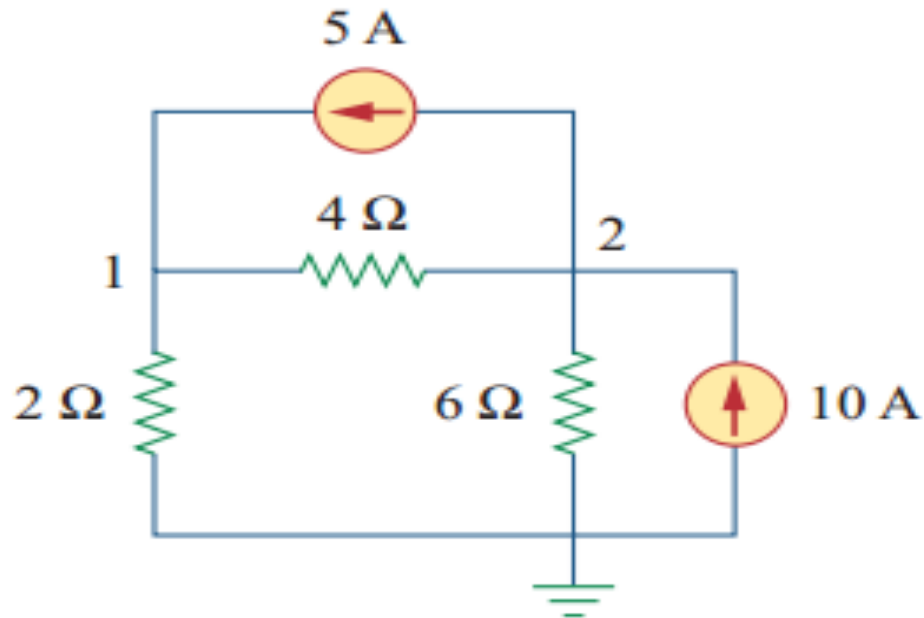Problem: Calculate the node voltages in the circuit.



# Nodal Analysis

Solution: Assign node voltages


Labeling of the currents is arbitrary

At node 1, applying KCL

$$i_1 = i_2 + i_3$$

$$5 = \frac{v_1 - v_2}{4} + \frac{v_1 - 0}{2}$$

$$3v_1 - v_2 = 20 \dots (i)$$

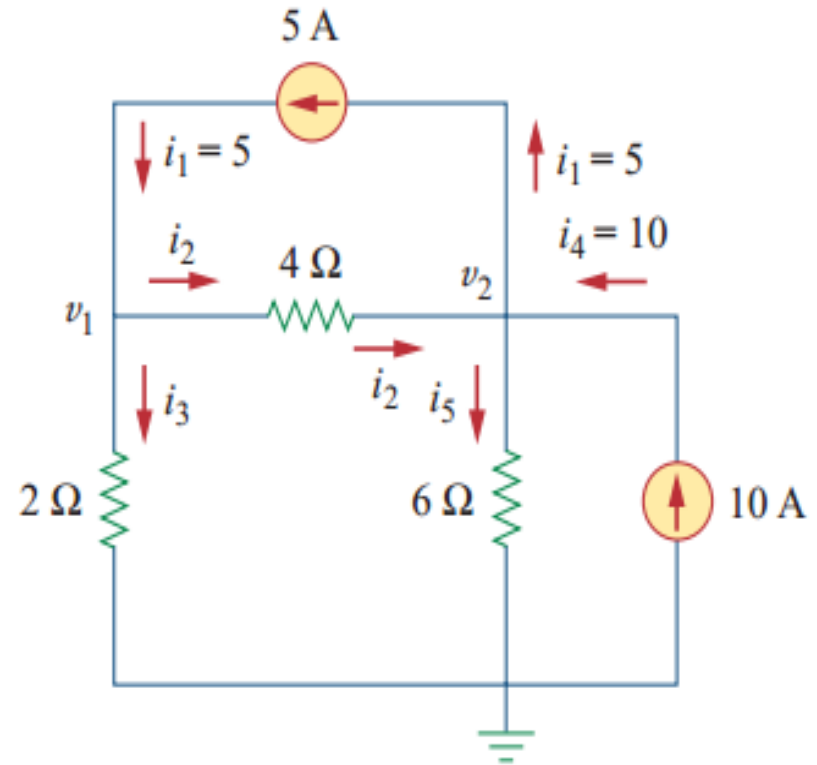


# Nodal Analysis

At node 2, applying KCL

$$i_2 + i_4 = i_1 + i_5$$

$$\frac{v_1 - v_2}{4} + 10 = 5 + \frac{v_2 - 0}{6}$$
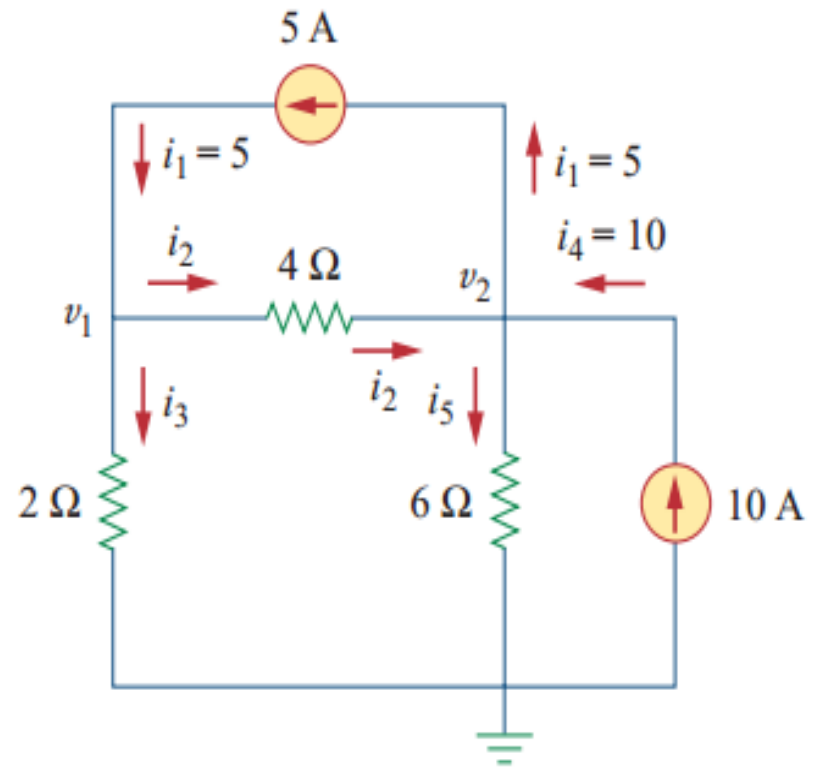
$$\frac{v_1 - v_2 + 40}{4} = \frac{30 + v_2}{6}$$



$$-3v_1 + 5v_2 = 60 \dots (ii)$$

# Nodal Analysis


After solving equation (i) and (ii), we get,

$$v_1 = 13.333 \text{ V}$$

$$v_2 = 20 \text{ V}$$

# Nodal Analysis

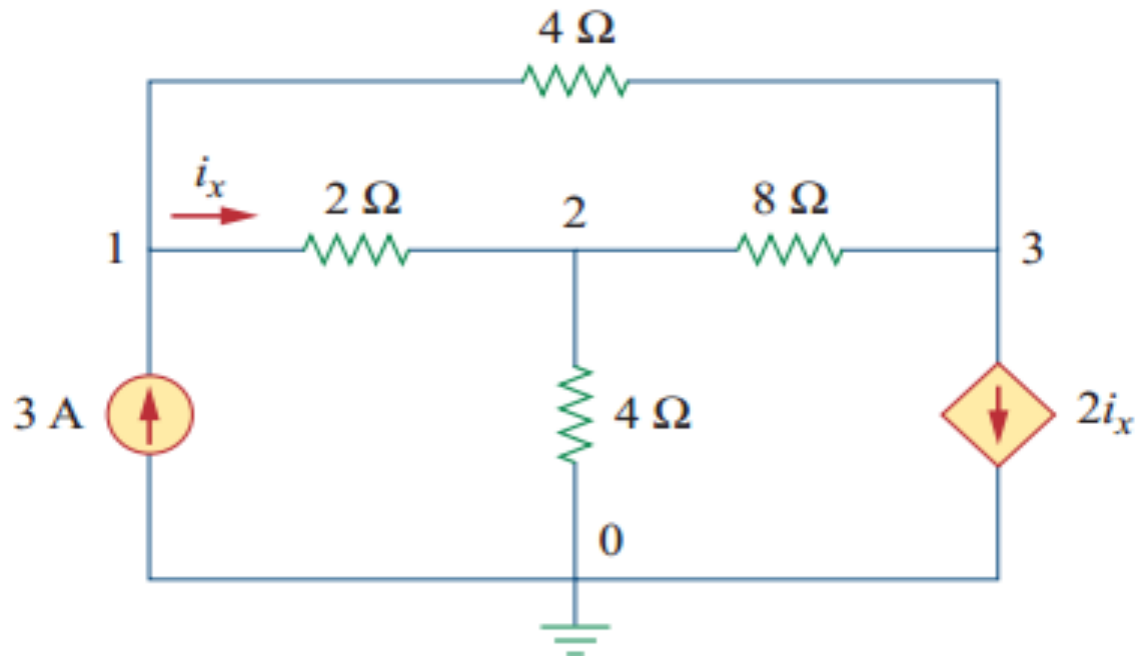Problem: Determine the voltages at the nodes.



# Nodal Analysis


Solution: Assign node voltages and labeling the current

At node 1, applying KCL

$$3 = i_1 + i_x$$

$$3 = \frac{v_1 - v_3}{4} + \frac{v_1 - v_2}{2}$$
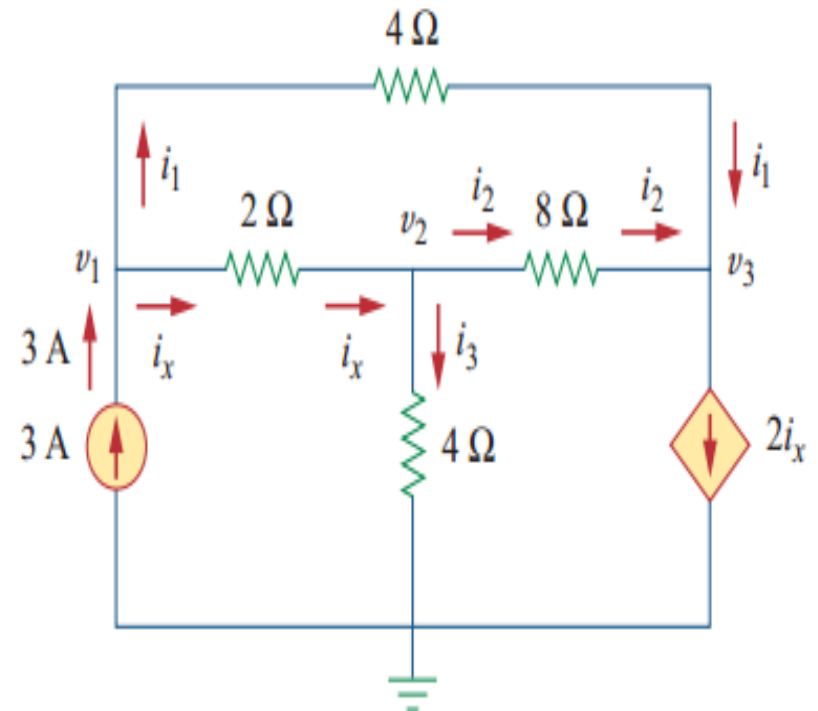
$$3 = \frac{v_1 - v_3 + 2v_1 - 2v_2}{4}$$



$$3v_1 - 2v_2 - v_3 = 12 \dots (i)$$




# Nodal Analysis

At node 2, applying KCL

$$i_x = i_2 + i_3$$

$$\frac{v_1 - v_2}{2} = \frac{v_2 - v_3}{8} + \frac{v_2 - 0}{4}$$

$$-4v_1 + 7v_2 - v_3 = 0 \dots (ii)$$

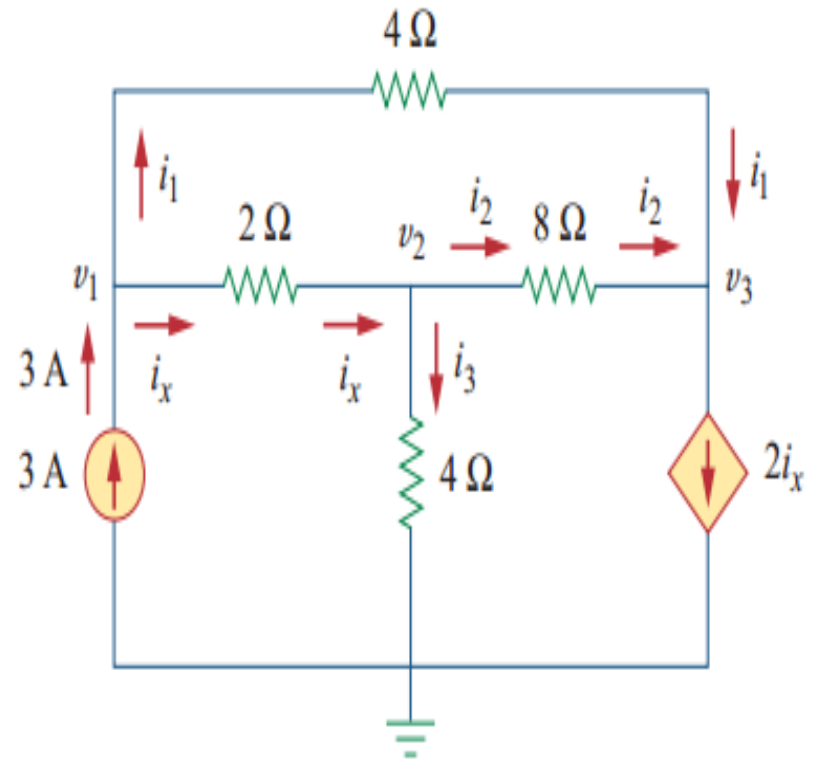

# Nodal Analysis


At node 3, applying KCL

$$i_1 + i_2 = 2i_x$$

$$\frac{v_1 - v_3}{4} + \frac{v_2 - v_3}{8} = 2 \frac{v_1 - v_2}{2}$$

$$\frac{2v_1 - 2v_3 + v_2 - v_3}{8} = v_1 - v_2$$

$$6v_1 - 7v_2 + v_3 = 0 \dots (iii)$$

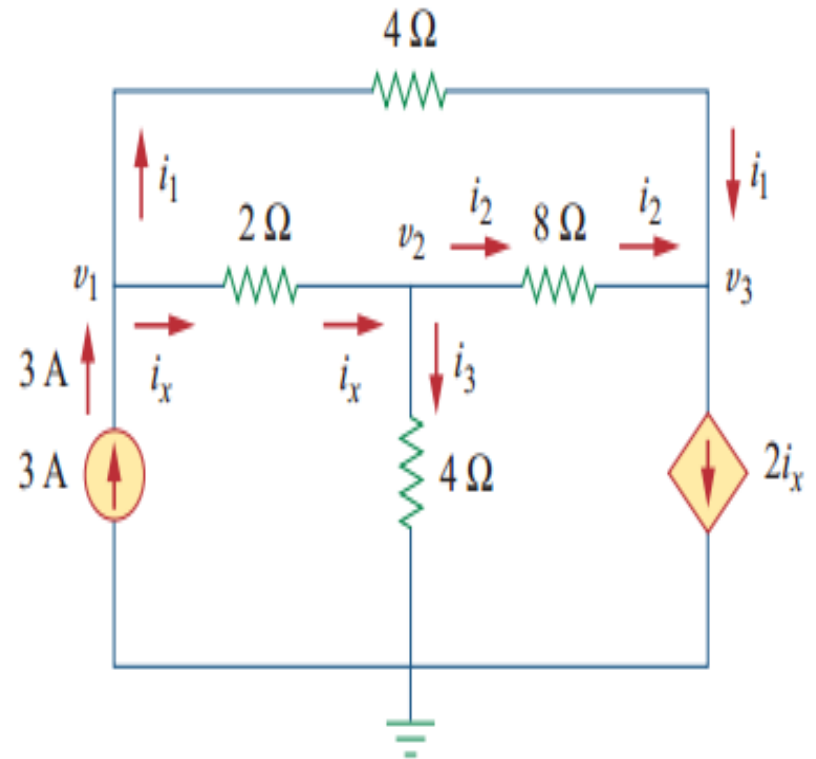

# Nodal Analysis

After solving equation (i), (ii) and (iii), we get,

$$v_1 = 4.8 \text{ V}$$


$$v_2 = 2.4 \text{ V}$$

$$v_3 = -2.4 \text{ V}$$

# Nodal Analysis with Voltage Sources


If a voltage source is connected between the reference node and a nonreference node, we simply set the voltage at the nonreference node equal to the voltage of the voltage source.

$$v_1 = 10 \text{ V}$$

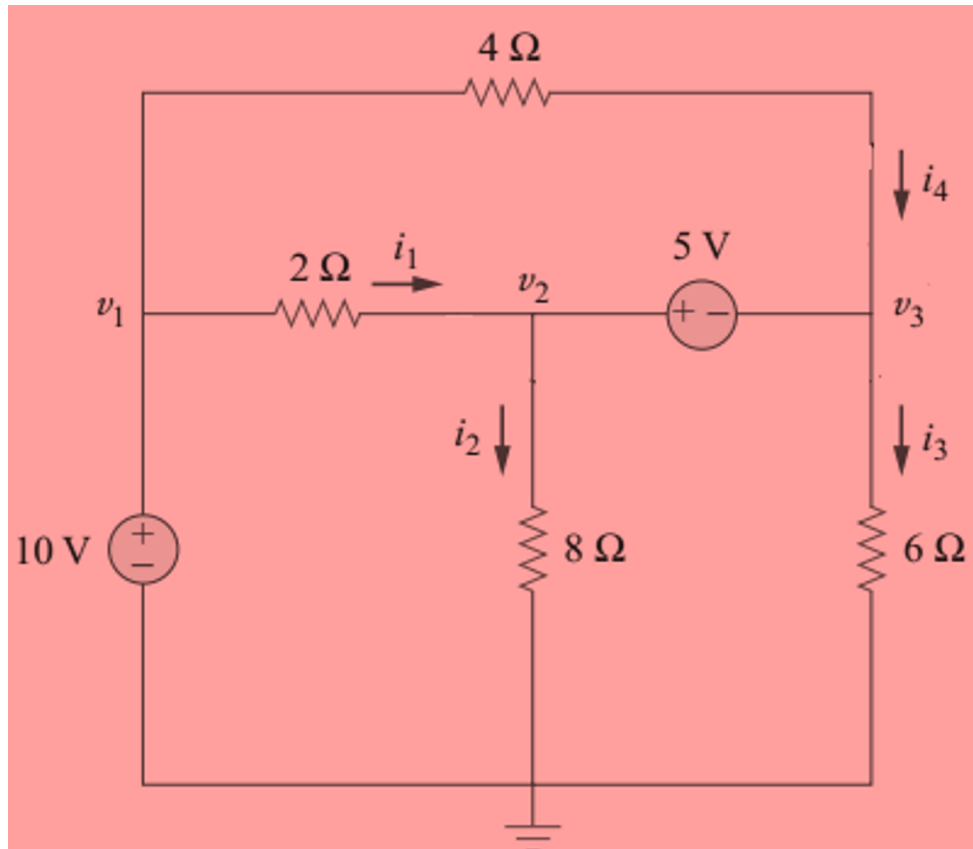
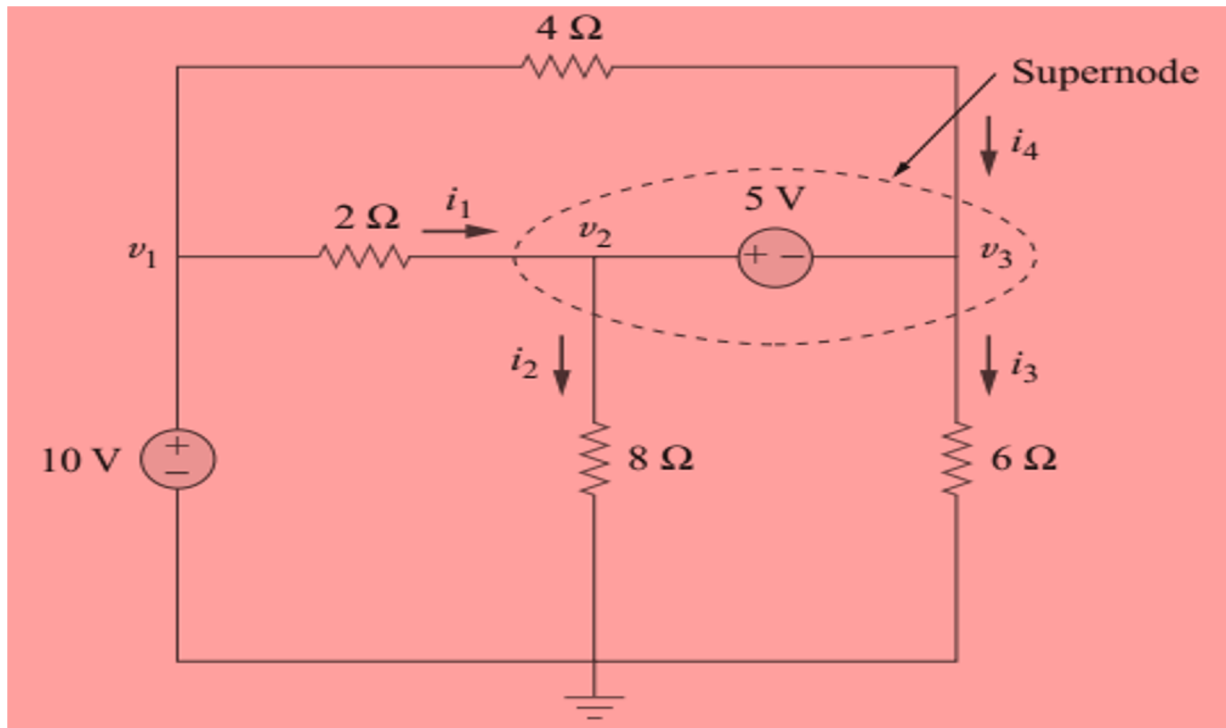
# Nodal Analysis with Voltage Sources

If the voltage source (dependent or independent) is connected between two nonreference nodes, the two nonreference nodes form a generalized node or supernode; we apply both KCL and KVL to determine the node voltages.



# Nodal Analysis with Voltage Sources


A supernode is formed by enclosing a (dependent or independent) voltage source connected between two nonreference nodes and any elements connected in parallel with it.

A supernode has no voltage of its own.

A supernode requires the application of both KCL and KVL

# Nodal Analysis with Voltage Sources

Determine the voltages at the nodes.

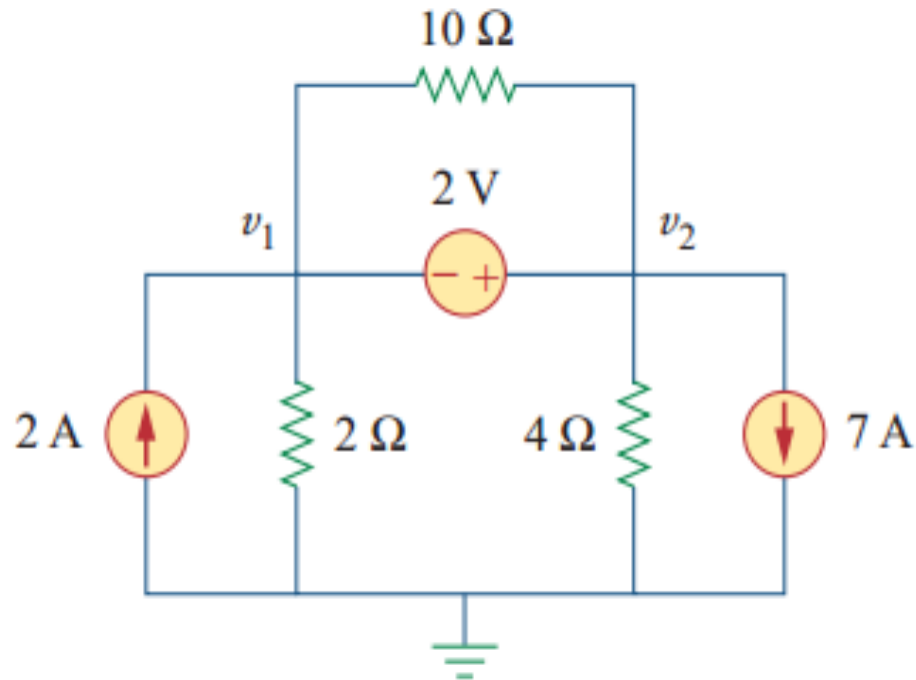

# Nodal Analysis with Voltage Sources

Solution: The supernode contains the 2V source, nodes 1 and 2, and the 10Ω resistor.

Labeling of the currents is arbitrary


Applying KCL at supernode,

$$2 = i_1 + i_2 + 7$$

$$2 = \frac{v_1 - 0}{2} + \frac{v_2 - 0}{4} + 7$$

$$2 = \frac{2v_1 + v_2 + 28}{4}$$

$$2v_1 + v_2 = -20 \dots\dots (i)$$

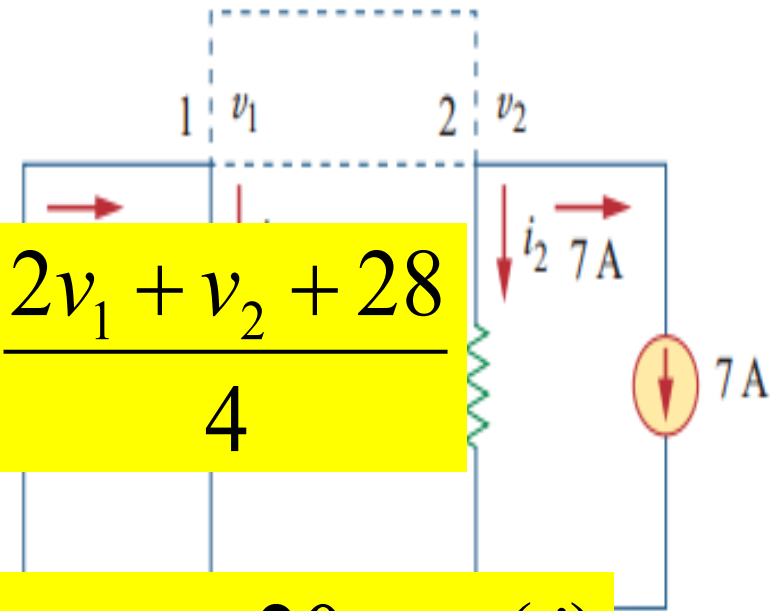



# Nodal Analysis with Voltage Sources

To get the relationship between  $v_1$  and  $v_2$  we apply KVL


$$-v_1 - 2 + v_2 = 0$$

$$-v_1 + v_2 = 2 \dots\dots (ii)$$

After solving equation (i) and (ii), we get,


$$v_1 = -7.333V$$

$$v_2 = -5.333V$$

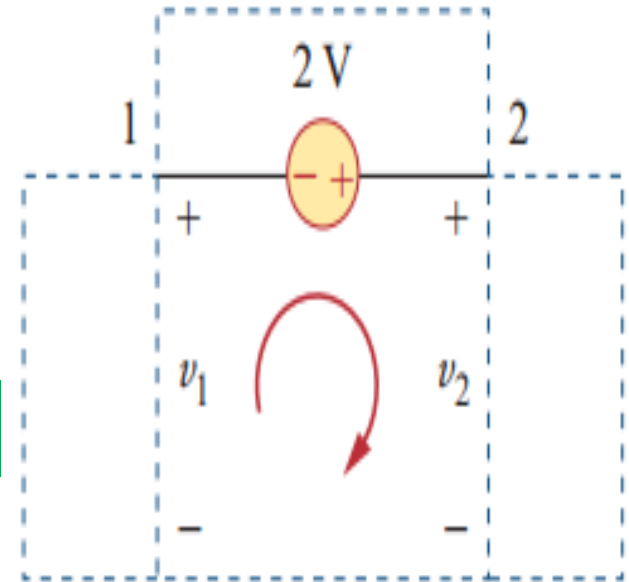

# Nodal Analysis with Voltage Sources

Problem: Find the node voltages

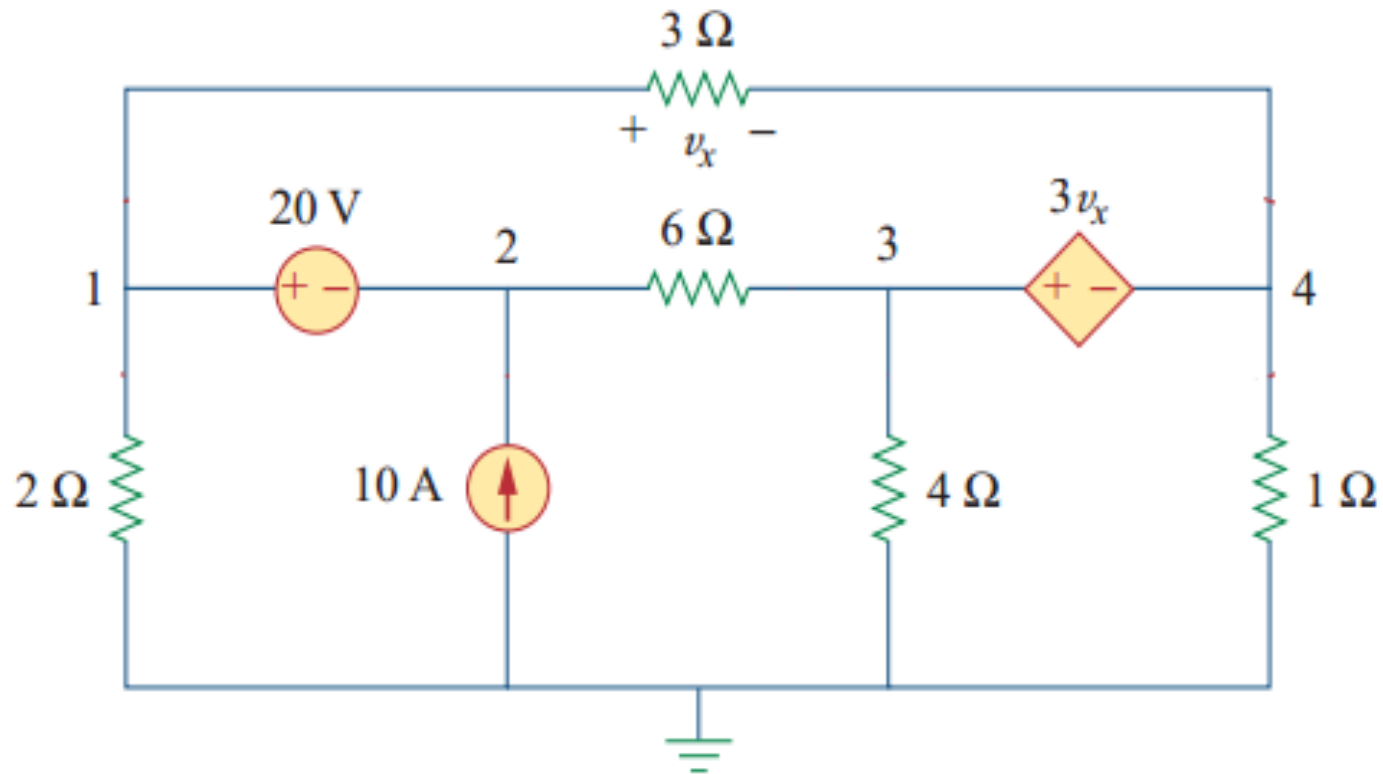


# Nodal Analysis with Voltage Sources

Solution: Nodes 1 and 2 form a supernode

Nodes 3 and 4 form another supernode


Labeling the direction of currents

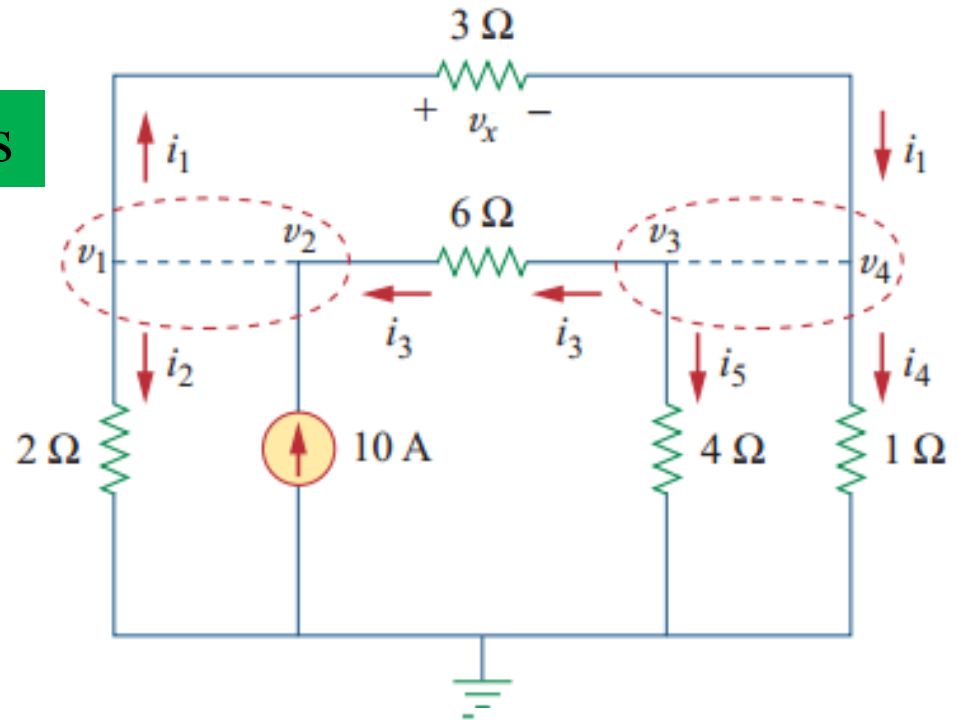

# Nodal Analysis with Voltage Sources

Applying KCL at supernode 1-2,

$$i_3 + 10 = i_1 + i_2$$

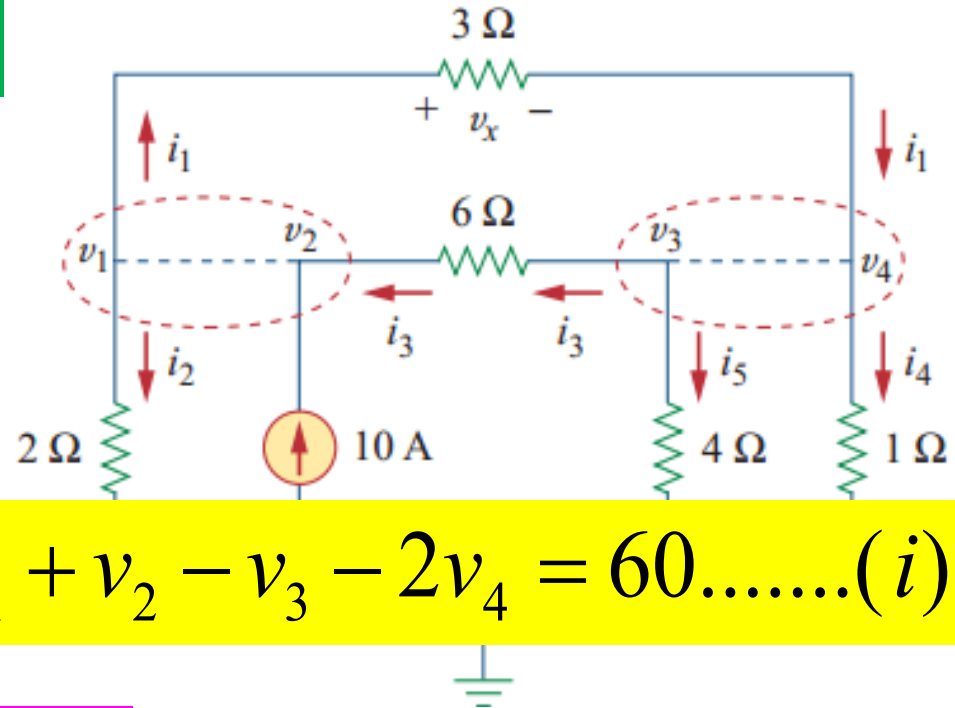


$$5v_1 + v_2 - v_3 - 2v_4 = 60 \dots\dots(i)$$

$$\frac{v_3 - v_2}{6} + 10 = \frac{v_1 - v_4}{3} + \frac{v_1 - 0}{2}$$

# Nodal Analysis with Voltage Sources

Applying KCL at supernode 3-4,

$$i_1 = i_3 + i_4 + i_5$$

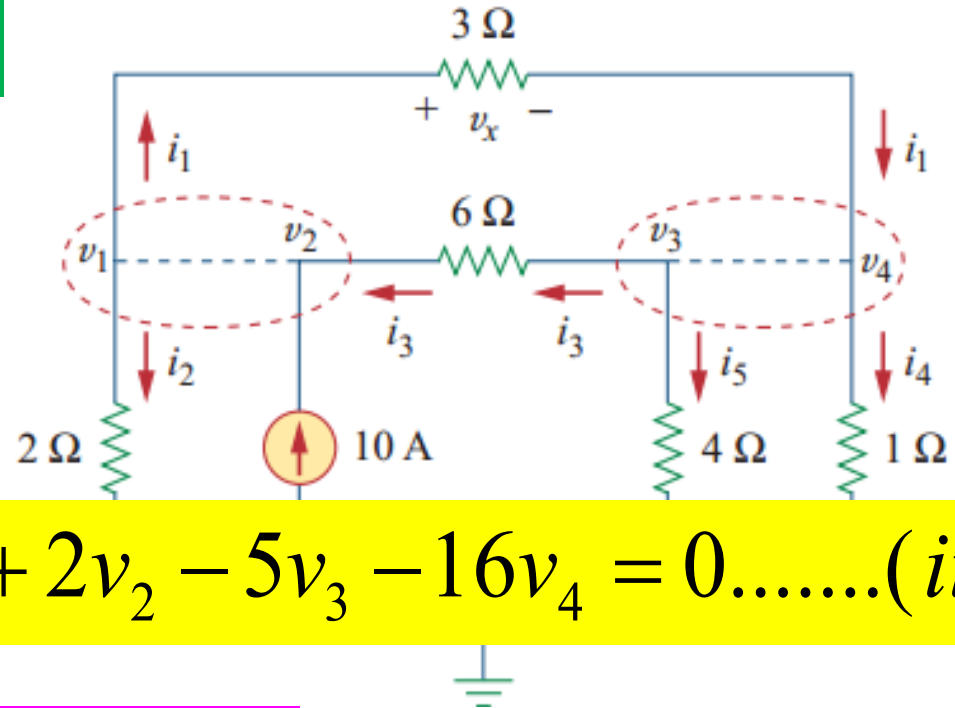

$$4v_1 + 2v_2 - 5v_3 - 16v_4 = 0 \dots\dots(ii)$$

$$\frac{v_1 - v_4}{3} = \frac{v_3 - v_2}{6} + \frac{v_4 - 0}{1} + \frac{v_3 - 0}{4}$$

# Nodal Analysis with Voltage Sources

Apply KVL to loop 1,


$$-v_1 + 20 + v_2 = 0$$

$$v_1 - v_2 = 20 \dots (iii)$$

Apply KVL to loop 2,

$$-v_3 + 3v_x + v_4 = 0$$

$$3v_1 - v_3 - 2v_4 = 0 \dots (iv)$$

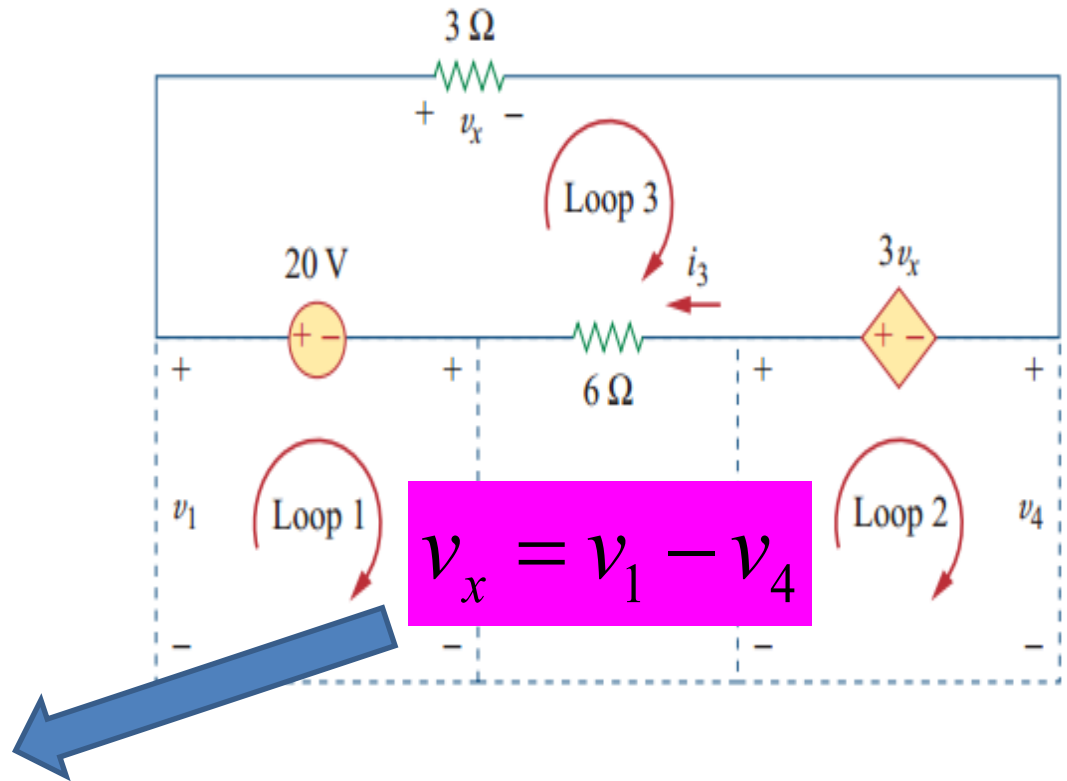

# Nodal Analysis with Voltage Sources

After solving equation (i), (ii), (iii) and (iv), we get,

$$v_1 = 26.67 V$$

$$v_3 = 173.33 V$$

$$v_2 = 6.667 V$$

$$v_4 = -46.67 V$$

**Thank You**