

FET Biasing

Text Book

Electronic Devices and Circuit Theory

by R Boylestad and L Nashelsky

Things to Remember

- ❖ distinct difference between the analysis of BJT and FET transistors is that the input controlling variable for a BJT transistor is a current level, while for the FET a voltage is the controlling variable.

The general relationships that can be applied to the dc analysis of all FET amplifiers are

$$I_G \cong 0 \text{ A} \quad (6.1)$$

and

$$I_D = I_S \quad (6.2)$$

For JFETs and depletion-type MOSFETs, Shockley's equation is applied to relate the input and output quantities:

$$I_D = I_{DSS} \left(\frac{1 - V_{GS}}{V_P} \right)^2 \quad (6.3)$$

For enhancement-type MOSFETs, the following equation is applicable:

$$I_D = k(V_{GS} - V_T)^2 \quad (6.4)$$

Fixed bias circuit

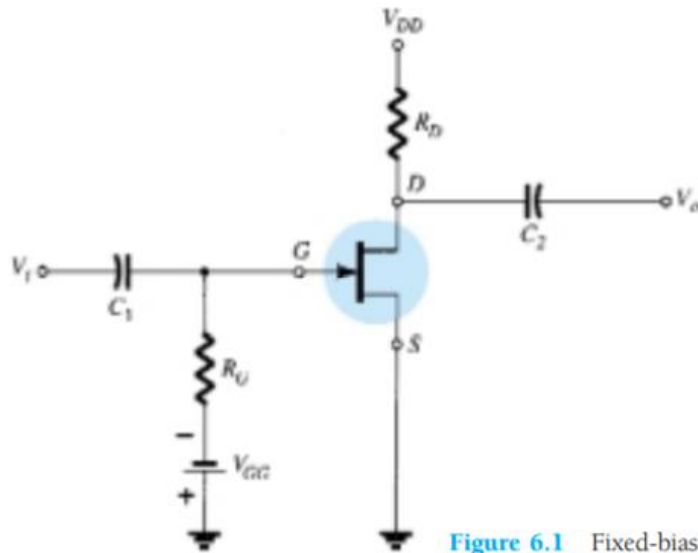


Figure 6.1 Fixed-bias configuration.


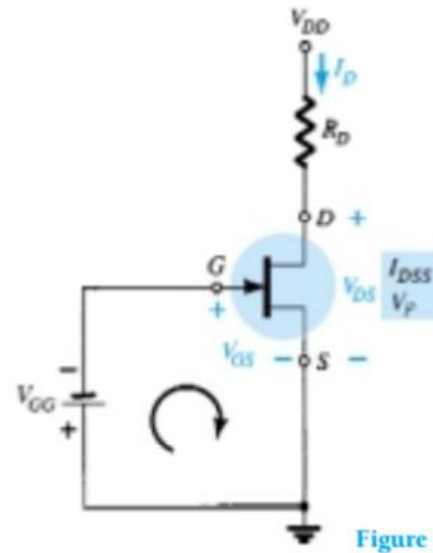
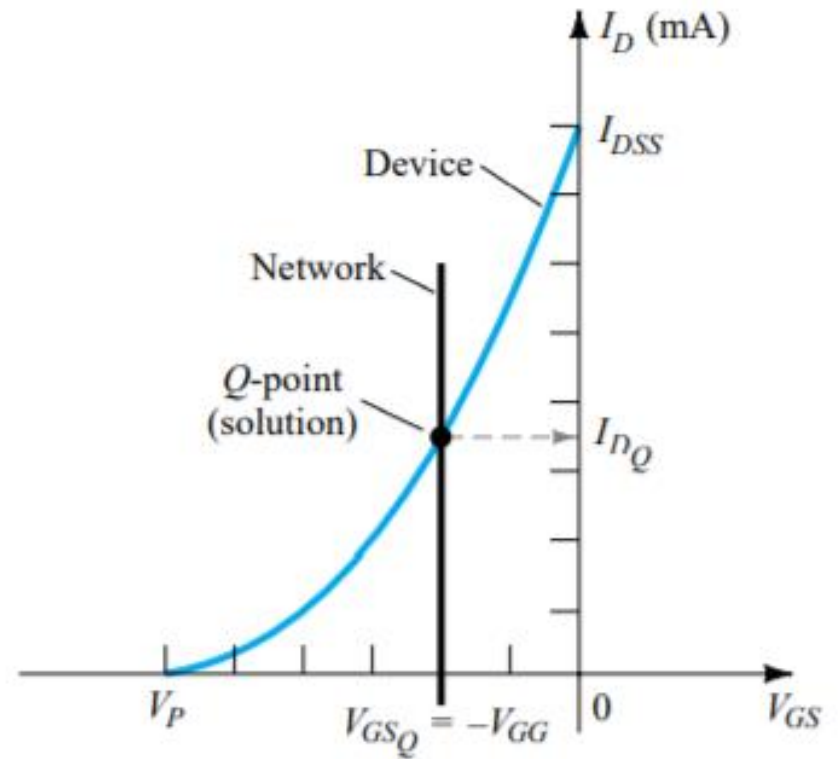


Figure 6.2 Network for dc analysis.

$$-V_{GG} - V_{GS} = 0$$

$$V_{GS} = -V_{GG}$$

Graphical Approach

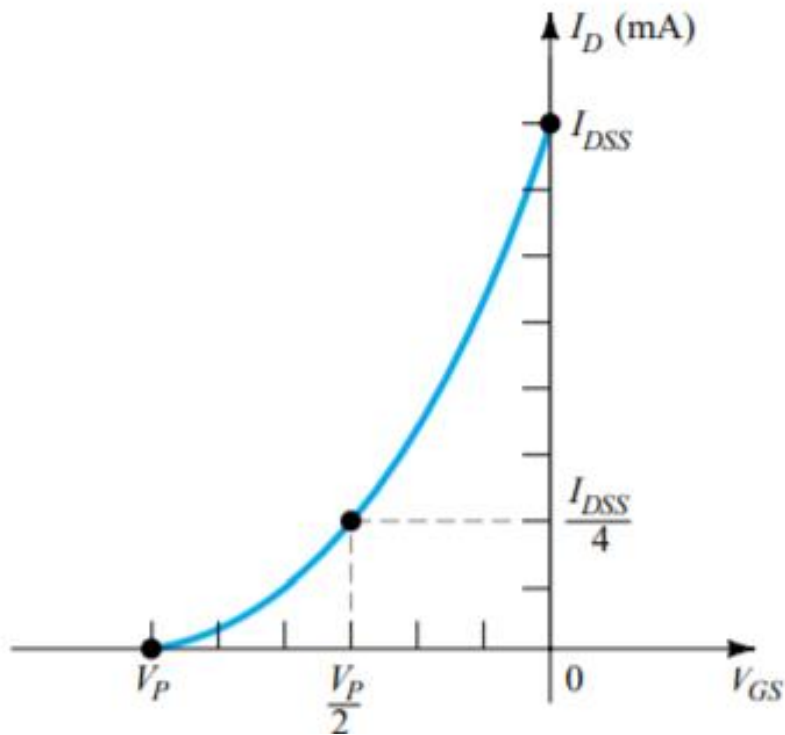

Output quantities

The drain-to-source voltage of the output section can be determined using Kirchhoff's voltage law as follows:

$$+V_{DS} + I_D R_D - V_{DD} = 0$$

and

$$V_{DS} = V_{DD} - I_D R_D$$

Recall that single-subscript voltages refer to the voltage at a point ground. For the configuration of Fig. 6.2,

$$V_S = 0 \text{ V}$$

Using double-subscript notation:

$$V_{DS} = V_D - V_S$$

or

$$V_D = V_{DS} + V_S = V_{DS} + 0 \text{ V}$$

and

$$V_D = V_{DS}$$

In addition,


$$V_{GS} = V_G - V_S$$

or

$$V_G = V_{GS} + V_S = V_{GS} + 0 \text{ V}$$

and

$$V_G = V_{GS}$$

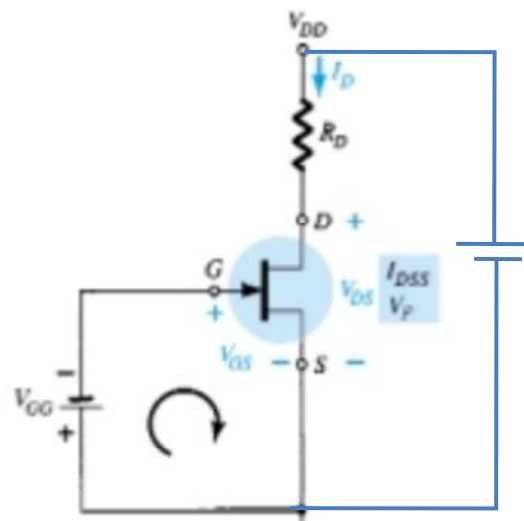


(6.8)

(6.9)

Example-1

Determine the following for the network of Fig. 6.6.

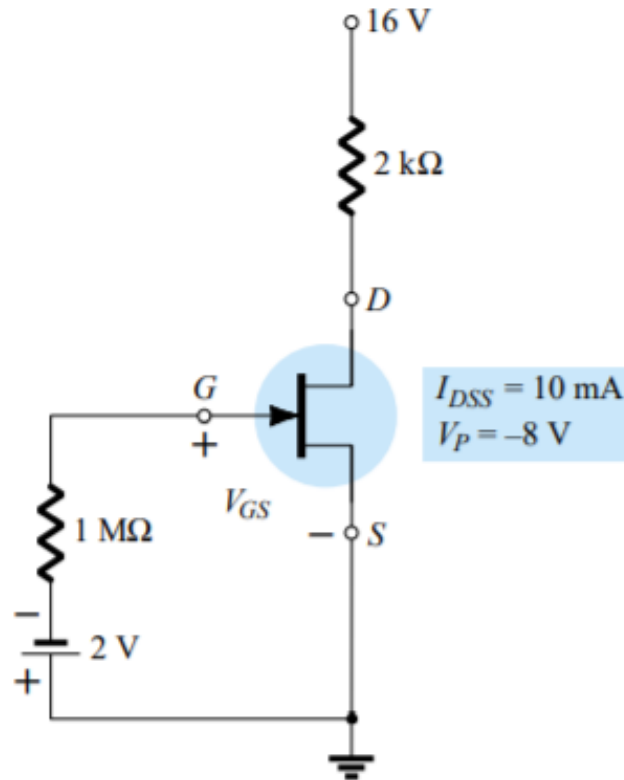- (a) V_{GSQ} .
- (b) I_{DQ} .
- (c) V_{DS} .
- (d) V_D .
- (e) V_G .
- (f) V_S .



Analytical Approach

Mathematical Approach:

(a) $V_{GSQ} = -V_{GG} = \mathbf{-2\text{ V}}$

(b) $I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = 10\text{ mA} \left(1 - \frac{-2\text{ V}}{-8\text{ V}} \right)^2$
 $= 10\text{ mA} (1 - 0.25)^2 = 10\text{ mA} (0.75)^2 = 10\text{ mA} (0.5625)$
 $= \mathbf{5.625\text{ mA}}$

(c) $V_{DS} = V_{DD} - I_D R_D = 16\text{ V} - (5.625\text{ mA})(2\text{ k}\Omega)$
 $= 16\text{ V} - 11.25\text{ V} = \mathbf{4.75\text{ V}}$

(d) $V_D = V_{DS} = \mathbf{4.75\text{ V}}$

(e) $V_G = V_{GS} = \mathbf{-2\text{ V}}$

(f) $V_S = \mathbf{0\text{ V}}$

Graphical Approach

$$V_{GSQ} = -V_{GG} = -2 \text{ V}$$


(b) $I_{DQ} = 5.6 \text{ mA}$

(c) $V_{DS} = V_{DD} - I_D R_D = 16 \text{ V} - (5.6 \text{ mA})(2 \text{ k}\Omega)$
 $= 16 \text{ V} - 11.2 \text{ V} = 4.8 \text{ V}$


(d) $V_D = V_{DS} = 4.8 \text{ V}$

(e) $V_G = V_{GS} = -2 \text{ V}$

(f) $V_S = 0 \text{ V}$

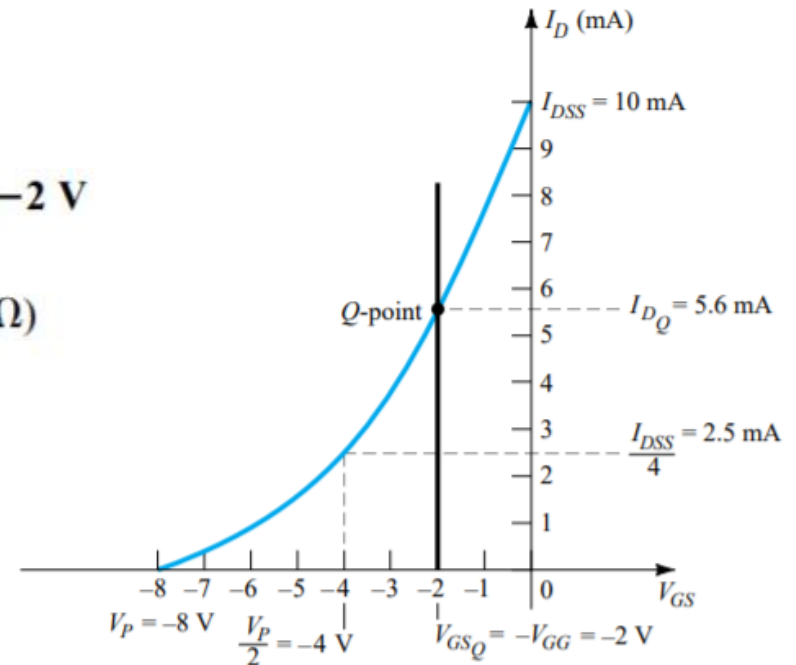

Self bias circuit

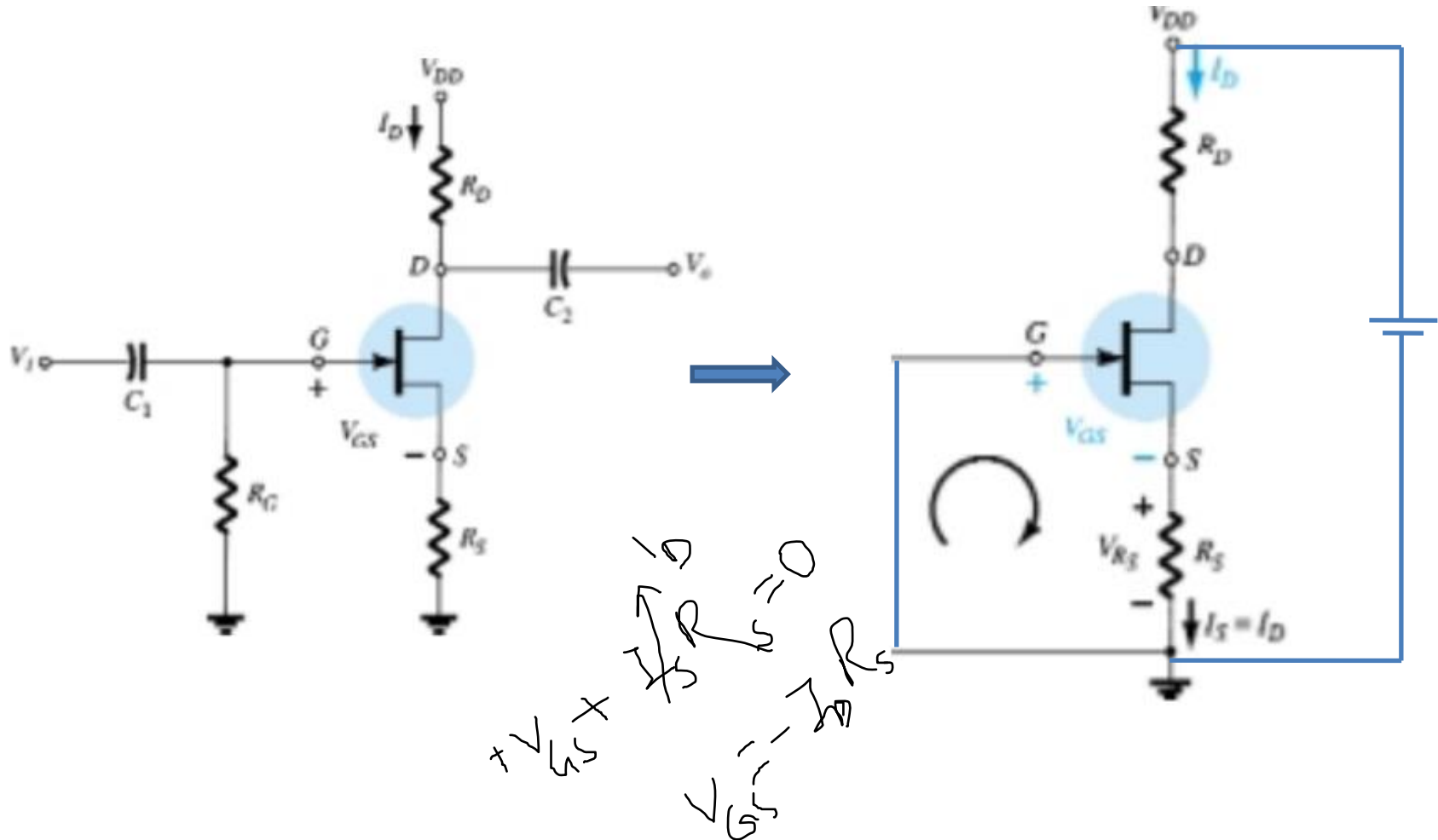

Finding V_{GS}

$$V_{R_S} = I_D R_S$$

For the indicated closed loop of Fig. 6.9, we find that

$$-V_{GS} - V_{R_S} = 0$$

and

$$V_{GS} = -V_{R_S}$$

or

$$V_{GS} = -I_D R_S$$

$$\begin{aligned} I_D &= I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \\ &= I_{DSS} \left(1 - \frac{-I_D R_S}{V_P} \right)^2 \end{aligned}$$

or

$$I_D = I_{DSS} \left(1 + \frac{I_D R_S}{V_P} \right)^2$$

By performing the squaring process indicated and rearranging terms, an equation of the following form can be obtained:

$$I_D^2 + K_1 I_D + K_2 = 0$$

Graphical Method

The level of V_{DS} can be determined by applying Kirchhoff's voltage law to the output circuit, with the result that

$$V_{R_S} + V_{DS} + V_{R_D} - V_{DD} = 0$$

and $V_{DS} = V_{DD} - V_{R_S} - V_{R_D} = V_{DD} - I_S R_S - I_D R_D$

but $I_D = I_S$


and
$$V_{DS} = V_{DD} - I_D(R_S + R_D)$$

In addition:

$$V_S = I_D R_S$$

$$V_G = 0 \text{ V}$$

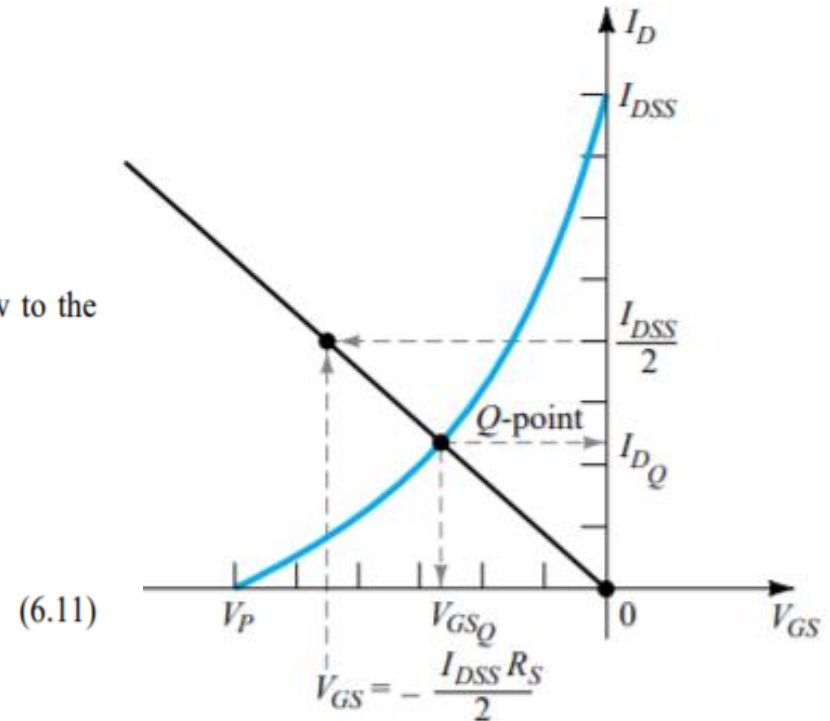and
$$V_D = V_{DS} + V_S = V_{DD} - V_{R_D}$$



$$(6.12)$$

$$(6.13)$$


$$(6.14)$$

Example-2

EXAMPLE 6.2

Determine the following for the network of Fig. 6.12.

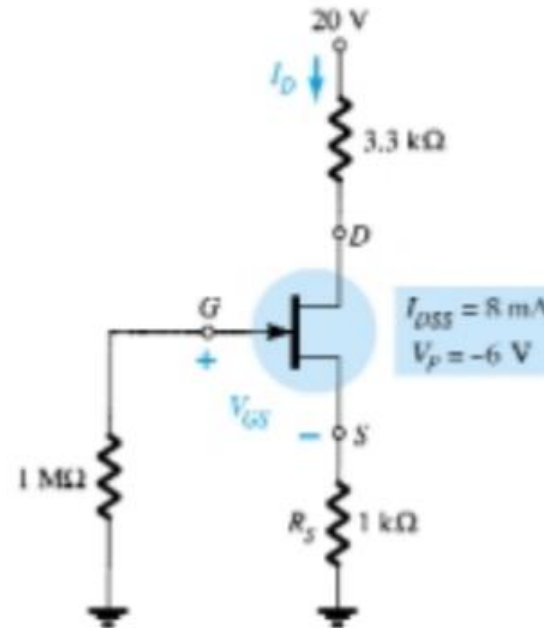- (a) V_{GS_Q} .
- (b) I_{D_Q} .
- (c) V_{DS} .
- (d) V_S .
- (e) V_G .
- (f) V_D .



Solution

(b) At the quiescent point:

$$I_{DQ} = 2.6 \text{ mA}$$


(c) Eq. (6.11): $V_{DS} = V_{DD} - I_D(R_S + R_D)$
 $= 20 \text{ V} - (2.6 \text{ mA})(1 \text{ k}\Omega + 3.3 \text{ k}\Omega)$
 $= 20 \text{ V} - 11.18 \text{ V}$
 $= \mathbf{8.82 \text{ V}}$

(d) Eq. (6.12): $V_S = I_D R_S$
 $= (2.6 \text{ mA})(1 \text{ k}\Omega)$
 $= \mathbf{2.6 \text{ V}}$


(e) Eq. (6.13): $V_G = \mathbf{0 \text{ V}}$

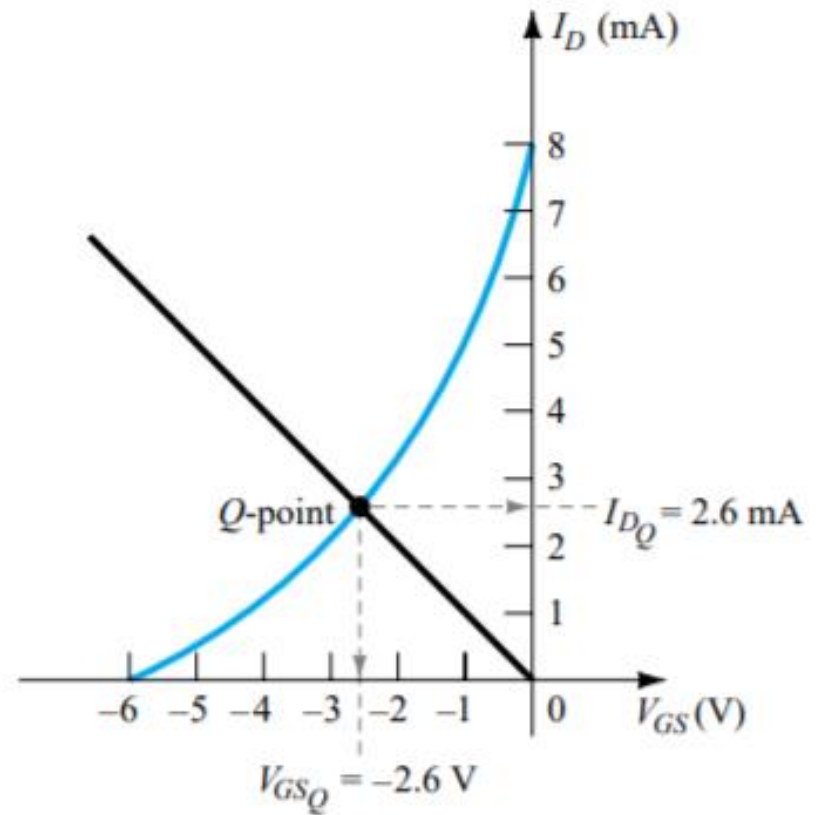(f) Eq. (6.14): $V_D = V_{DS} + V_S = 8.82 \text{ V} + 2.6 \text{ V} = \mathbf{11.42 \text{ V}}$

or $V_D = V_{DD} - I_D R_D = 20 \text{ V} - (2.6 \text{ mA})(3.3 \text{ k}\Omega) = \mathbf{11.42 \text{ V}}$



Voltage Divider bias

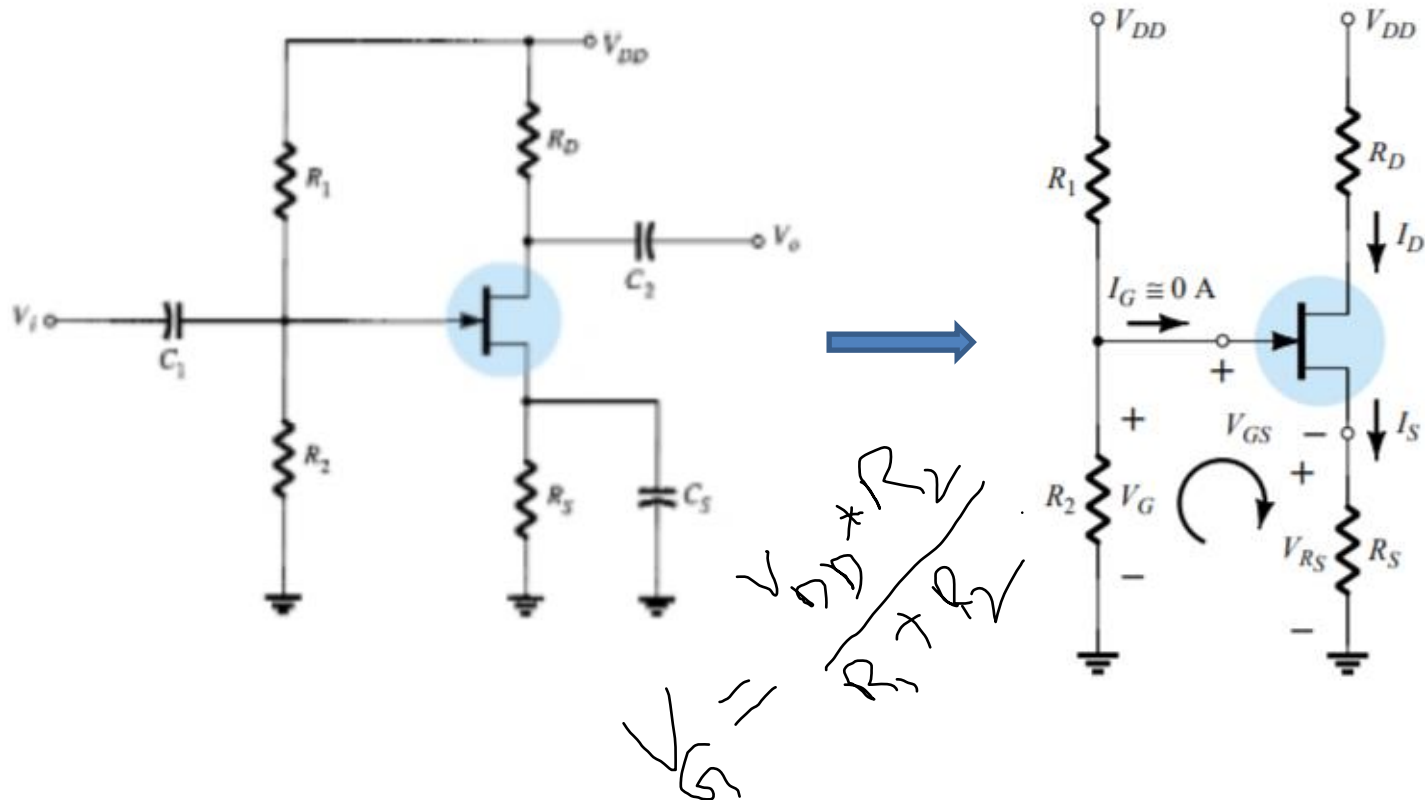

Solution

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2} \quad (6.15)$$

Applying Kirchhoff's voltage law in the clockwise direction to the indicated loop of Fig. 6.21 will result in


$$V_G - V_{GS} - V_{R_S} = 0$$

and

$$V_{GS} = V_G - V_{R_S}$$

Substituting $V_{R_S} = I_S R_S = I_D R_S$, we have

$$V_{GS} = V_G - I_D R_S \quad (6.16)$$

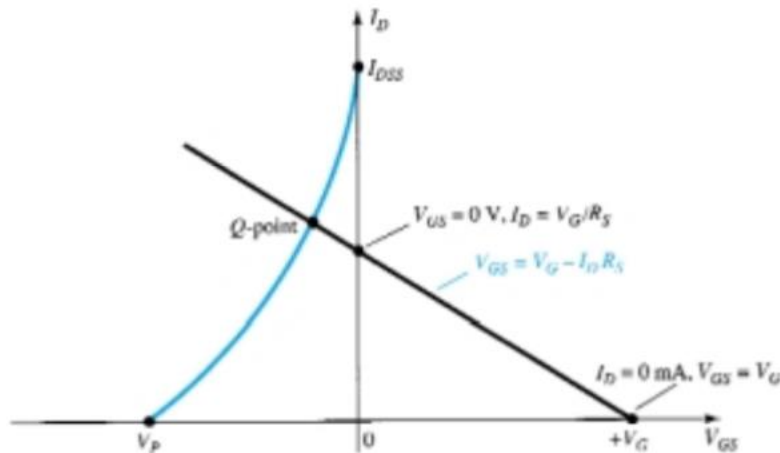

$$V_{DS} = V_{DD} - I_D(R_D + R_S) \quad (6.19)$$

$$V_D = V_{DD} - I_D R_D \quad (6.20)$$

$$V_S = I_D R_S \quad (6.21)$$

Example-3

Determine the following for the network of Fig. 6.24.

- (a) I_{DQ} and V_{GSQ} .
- (b) V_D .
- (c) V_S .
- (d) V_{DS} .
- (e) V_{DG} .

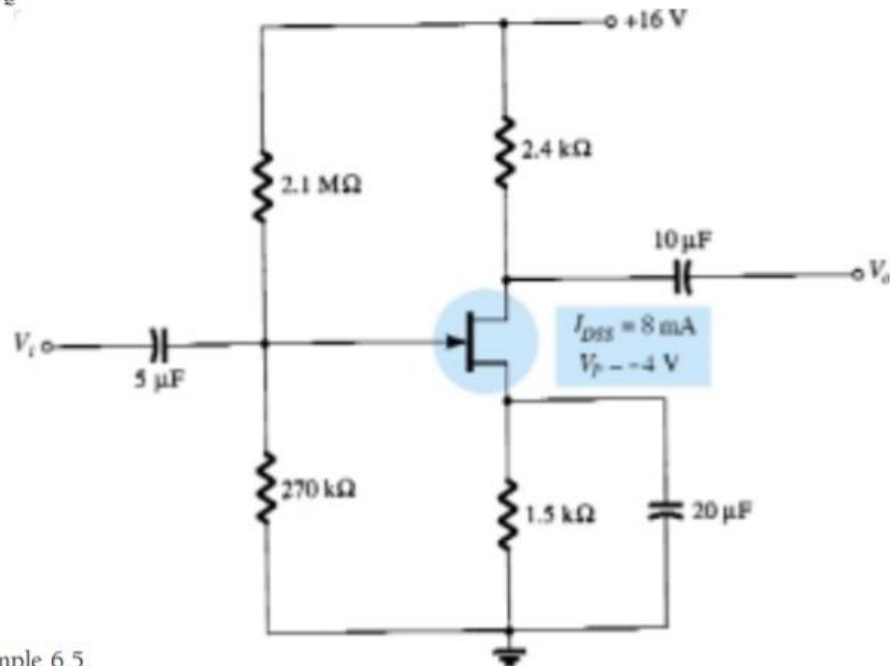


Figure 6.24 Example 6.5.

Solution

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$= \frac{(270 \text{ k}\Omega)(16 \text{ V})}{2.1 \text{ M}\Omega + 0.27 \text{ M}\Omega}$$

$$= 1.82 \text{ V}$$

and

$$V_{GS} = V_G - I_D R_S$$

$$= 1.82 \text{ V} - I_D(1.5 \text{ k}\Omega)$$

When $I_D = 0 \text{ mA}$:

$$V_{GS} = +1.82 \text{ V}$$

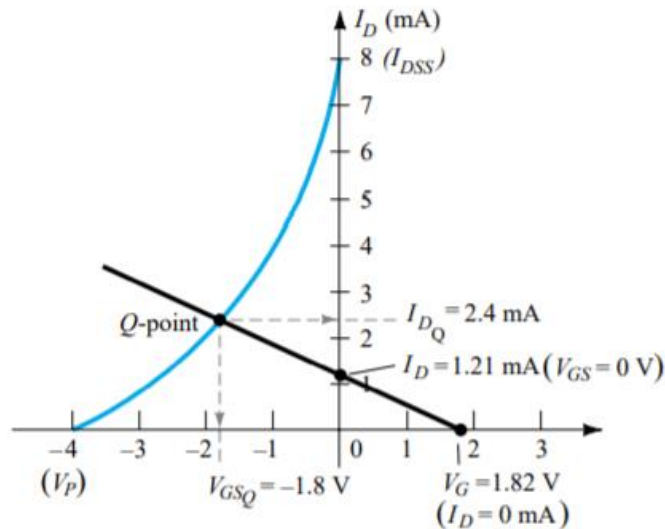


Figure 6.25 Determining the Q -point for the network of Fig. 6.24.

$$(b) \ V_D = V_{DD} - I_D R_D$$

$$= 16 \text{ V} - (2.4 \text{ mA})(2.4 \text{ k}\Omega)$$

$$= \mathbf{10.24 \text{ V}}$$

$$(c) \ V_S = I_D R_S = (2.4 \text{ mA})(1.5 \text{ k}\Omega)$$

$$= \mathbf{3.6 \text{ V}}$$

$$(d) \ V_{DS} = V_{DD} - I_D(R_D + R_S)$$

$$= 16 \text{ V} - (2.4 \text{ mA})(2.4 \text{ k}\Omega + 1.5 \text{ k}\Omega)$$

$$= \mathbf{6.64 \text{ V}}$$

$$\text{or } V_{DS} = V_D - V_S = 10.24 \text{ V} - 3.6 \text{ V}$$

$$= \mathbf{6.64 \text{ V}}$$

Common Gate Configuration

Practice yourself and send me
your feedback, if any.

MOSFET Biasing

DEPLETION-TYPE MOSFETs

The primary difference from JFET is the fact that depletion-type MOSFETs permit operating points with positive values of V_{GS} and levels of I_D that exceed I_{DSS} .

EXAMPLE 6.7

For the n -channel depletion-type MOSFET of Fig. 6.29, determine:

- (a) I_{DQ} and V_{GSQ} .
- (b) V_{DS} .

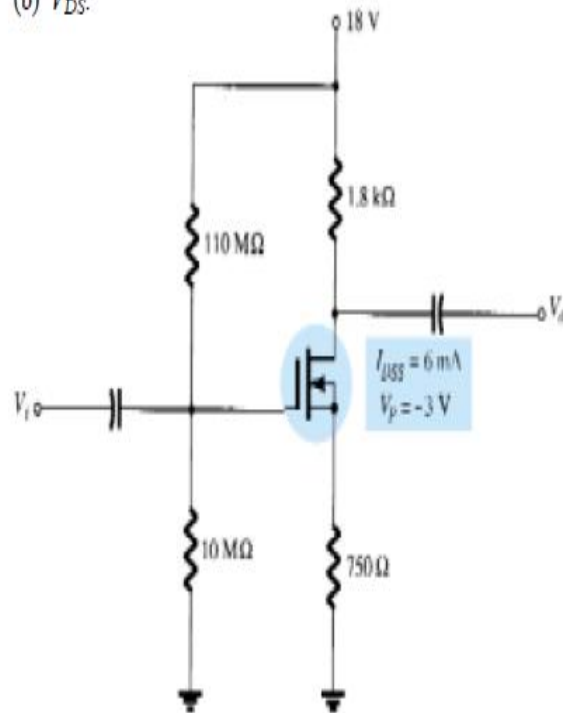


Figure 6.29 Example 6.7

Solution

- (a) For the transfer characteristics, a plot point is defined by $I_D = I_{DSS}/4 = 6 \text{ mA}/4 = 1.5 \text{ mA}$ and $V_{GS} = V_P/2 = -3 \text{ V}/2 = -1.5 \text{ V}$. Considering the level of V_P and the fact that Shockley's equation defines a curve that rises more rapidly as V_{GS} becomes more positive, a plot point will be defined at $V_{GS} = +1 \text{ V}$. Substituting into Shockley's equation yields


$$\begin{aligned} I_D &= I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \\ &= 6 \text{ mA} \left(1 - \frac{+1 \text{ V}}{-3 \text{ V}} \right)^2 = 6 \text{ mA} \left(1 + \frac{1}{3} \right)^2 = 6 \text{ mA}(1.778) \\ &= 10.67 \text{ mA} \end{aligned}$$

The resulting transfer curve appears in Fig. 6.30. Proceeding as described for JFETs, we have:

$$\text{Eq. (6.15): } V_G = \frac{10 \text{ M}\Omega(18 \text{ V})}{10 \text{ M}\Omega + 110 \text{ M}\Omega} = 1.5 \text{ V}$$

$$\text{Eq. (6.16): } V_{GS} = V_G - I_D R_S = 1.5 \text{ V} - I_D(750 \Omega)$$

MOSFET Biasing

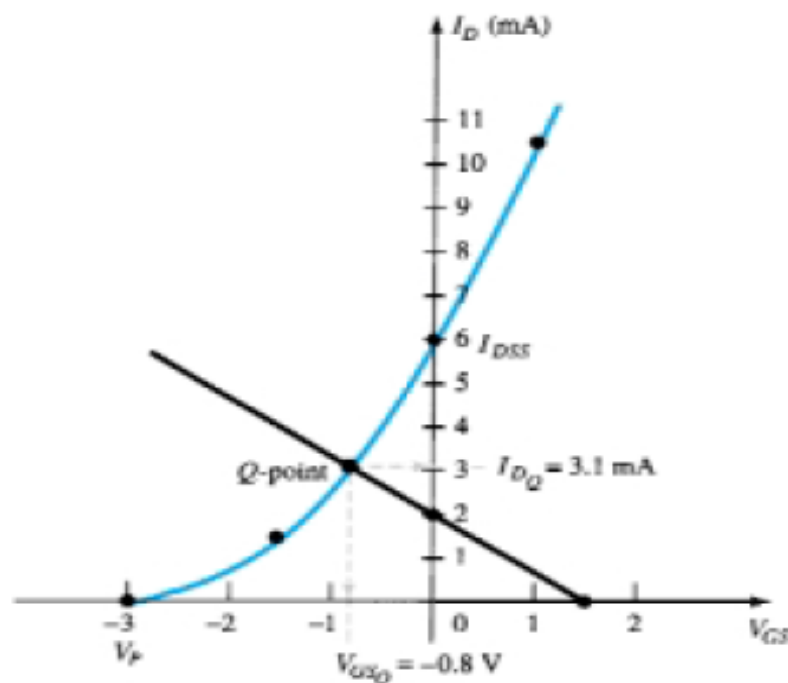

$$\begin{aligned}
 \text{(b) Eq. (6.19): } V_{DS} &= V_{DD} - I_D(R_D + R_S) \\
 &= 18 \text{ V} - (3.1 \text{ mA})(1.8 \text{ k}\Omega + 750 \text{ }\Omega) \\
 &\cong 10.1 \text{ V}
 \end{aligned}$$

Figure 6.30 Determining the Q-point for the network of Fig. 6.29.

Setting $I_D = 0$ mA results in

$$V_{GS} = V_G = 1.5 \text{ V}$$

Setting $V_{GS} = 0$ V yields

$$I_D = \frac{V_G}{R_S} = \frac{1.5 \text{ V}}{750 \text{ }\Omega} = 2 \text{ mA}$$

The plot points and resulting bias line appear in Fig. 6.30. The resulting operating point:

$$I_{DQ} = 3.1 \text{ mA}$$

$$V_{GSQ} = -0.8 \text{ V}$$

Enhancement type MOSFET biasing

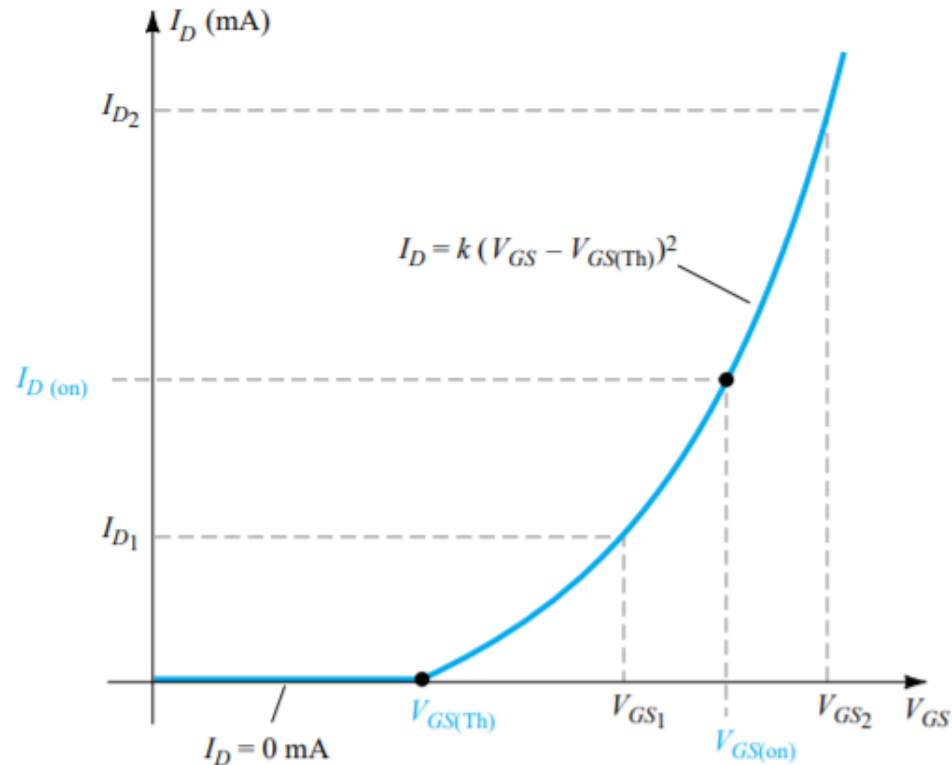


Figure 6.35 Transfer characteristics of an n -channel enhancement-type MOSFET.

Feedback biasing

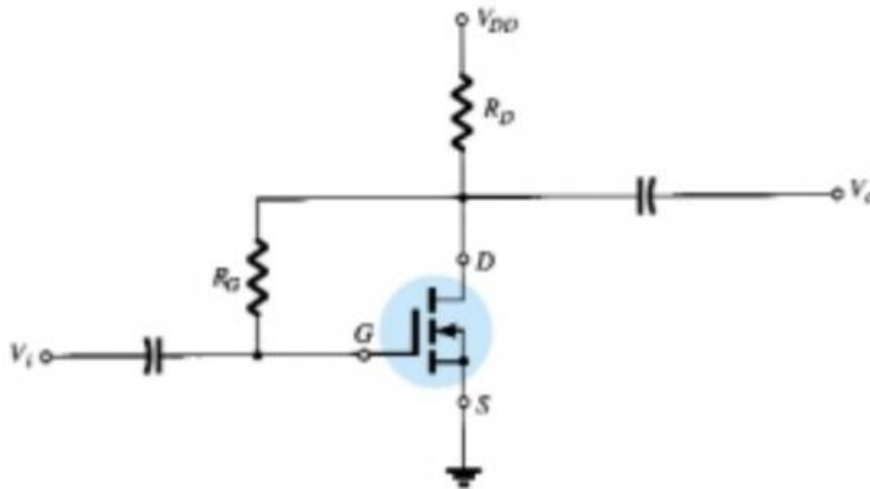


Figure 6.36 Feedback biasing arrangement.


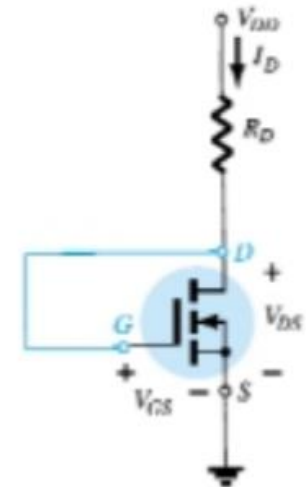


Figure 6.37 DC equivalent of the network of Fig. 6.36.

Analysis

$$V_{GS} = V_{DD} - I_D R_D$$

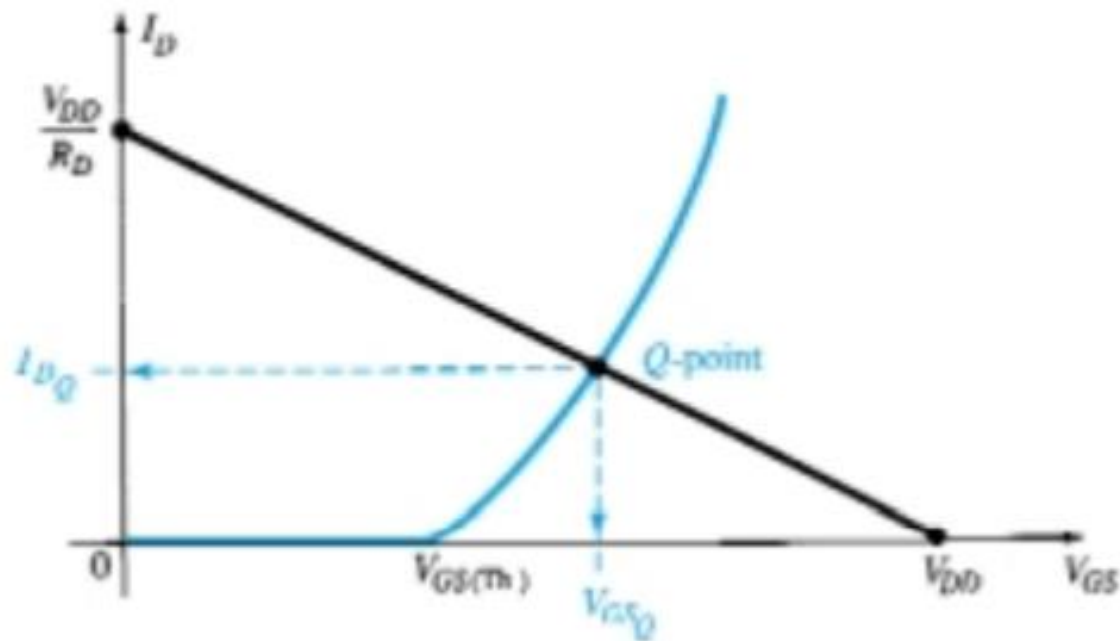

Example-1

Determine I_{DQ} and V_{DSQ} for the enhancement-type MOSFET of Fig. 6.39.

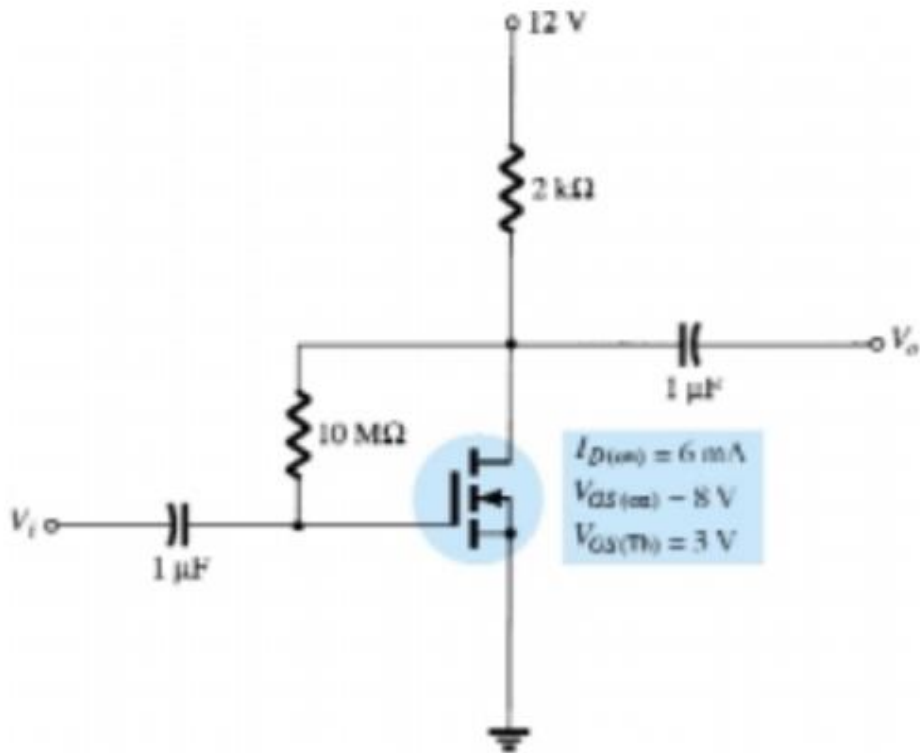


Figure 6.39 Example 6.11.


Solution

Finding k:


$$\begin{aligned}\text{Eq. (6.26): } k &= \frac{I_{D(\text{on})}}{(V_{GS(\text{on})} - V_{GS(\text{Th})})^2} \\ &= \frac{6 \text{ mA}}{(8 \text{ V} - 3 \text{ V})^2} = \frac{6 \times 10^{-3}}{25} \text{ A/V}^2 \\ &= \mathbf{0.24 \times 10^{-3} \text{ A/V}^2}\end{aligned}$$

(between 3 and 8 V):
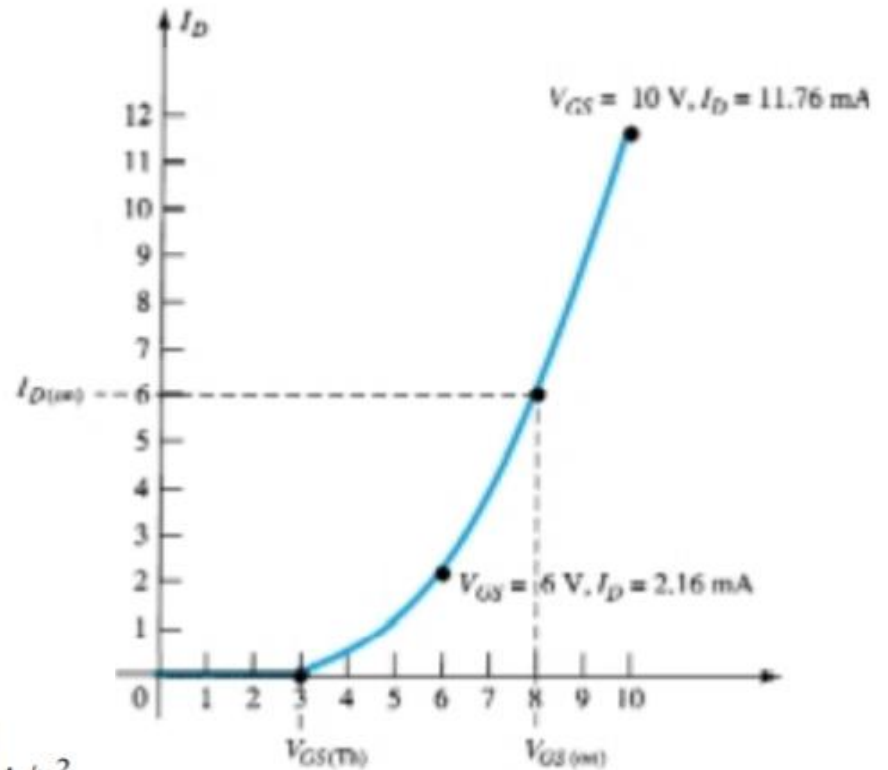
$$\begin{aligned}I_D &= 0.24 \times 10^{-3} (6 \text{ V} - 3 \text{ V})^2 = 0.24 \times 10^{-3} (9) \\ &= 2.16 \text{ mA}\end{aligned}$$



Voltage divider bias

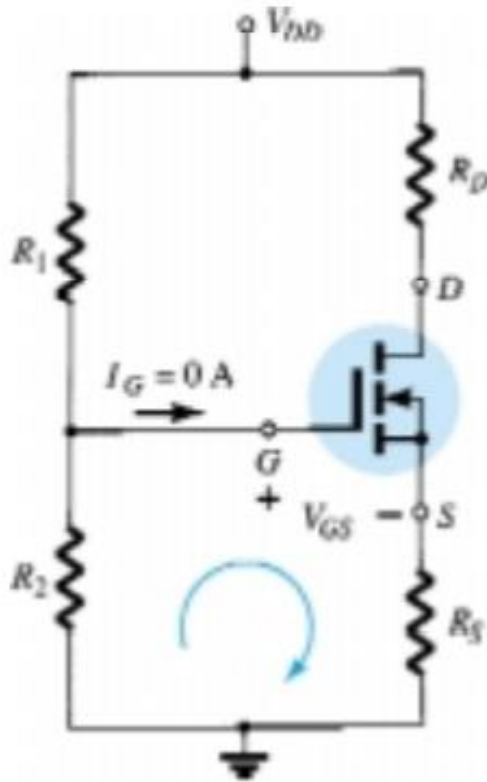

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$+V_G - V_{GS} - V_{R_S} = 0$$

$$V_{GS} = V_G - V_{R_S}$$

$$V_{GS} = V_G - I_D R_S$$

$$V_{R_S} + V_{DS} + V_{R_D} - V_{DD} = 0$$

$$V_{DS} = V_{DD} - V_{R_S} - V_{R_D}$$

$$V_{DS} = V_{DD} - I_D(R_S + R_D)$$

Example-2

Determine I_{DQ} , V_{GSQ} , and V_{DS} for the network of Fig. 6.43.

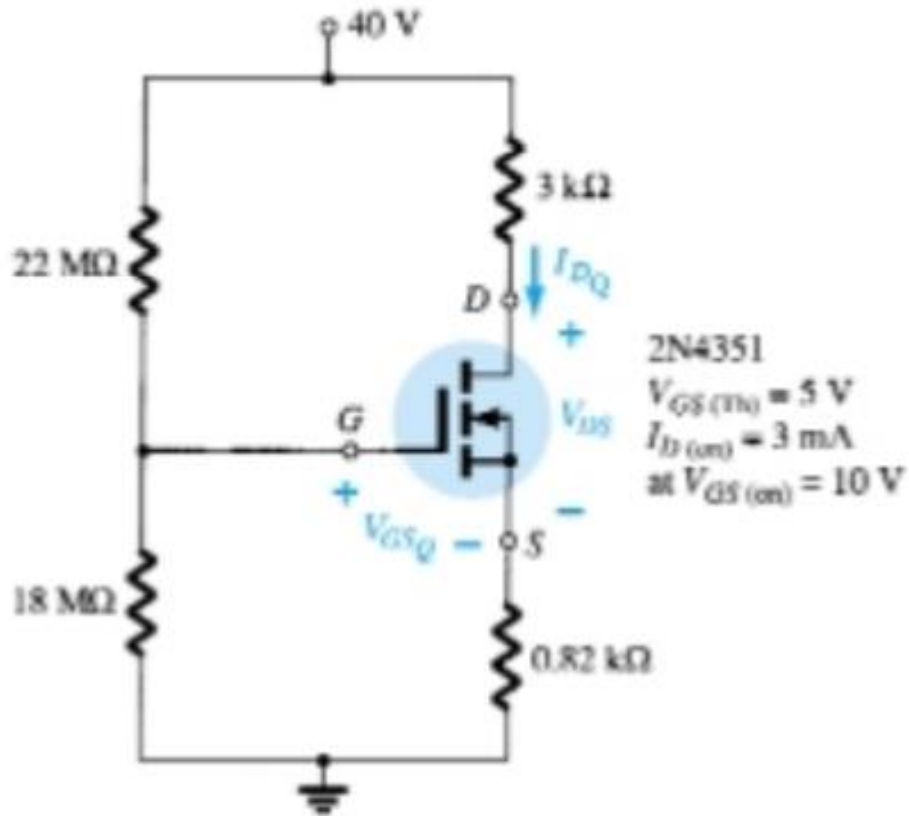


Figure 6.43 Example 6.12.

Solution

$$V_{GS(\text{Th})} = 5 \text{ V}, \quad I_{D(\text{on})} = 3 \text{ mA with } V_{GS(\text{on})} = 10 \text{ V}$$

$$\begin{aligned} \text{Eq. (6.26): } k &= \frac{I_{D(\text{on})}}{(V_{GS(\text{on})} - V_{GS(\text{Th})})^2} \\ &= \frac{3 \text{ mA}}{(10 \text{ V} - 5 \text{ V})^2} = 0.12 \times 10^{-3} \text{ A/V}^2 \end{aligned}$$

$$\begin{aligned} I_D &= k(V_{GS} - V_{GS(\text{Th})})^2 \\ &= 0.12 \times 10^{-3}(V_{GS} - 5)^2 \end{aligned}$$

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2} = \frac{(18 \text{ M}\Omega)(40 \text{ V})}{22 \text{ M}\Omega + 18 \text{ M}\Omega} = 18 \text{ V}$$

$$V_{GS} = V_G - I_D R_S = 18 \text{ V} - I_D(0.82 \text{ k}\Omega)$$

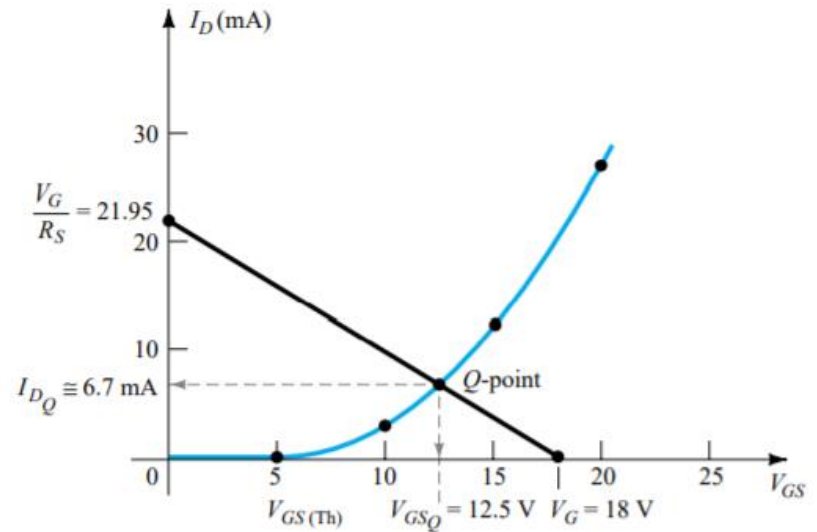


Figure 6.44 Determining the Q -point for the network of Example 6.12.

$$I_{DQ} \cong 6.7 \text{ mA}$$

$$V_{GSQ} = 12.5 \text{ V}$$

$$\begin{aligned} \text{Eq. (6.33): } V_{DS} &= V_{DD} - I_D(R_S + R_D) \\ &= 40 \text{ V} - (6.7 \text{ mA})(0.82 \text{ k}\Omega + 3.0 \text{ k}\Omega) \\ &= 40 \text{ V} - 25.6 \text{ V} \\ &= 14.4 \text{ V} \end{aligned}$$

P-Channel FETs

Practice yourself and send me
your feedback, if any.