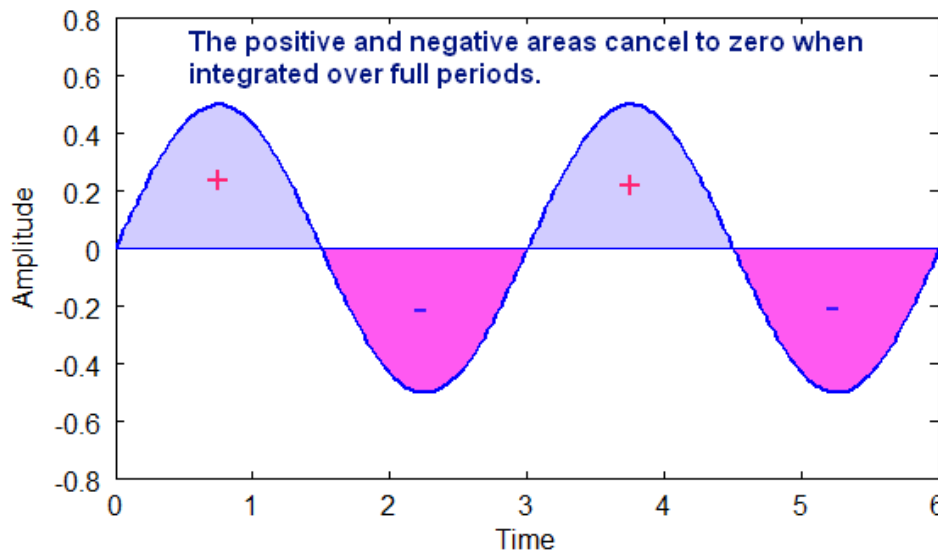


# Diode as Rectifiers

# Rectification

---

- Ac signals have zero average or dc value.
- To create dc level, rectification is necessary.



- Rectifiers are of two types, half wave and full wave rectifiers

# Half wave rectification

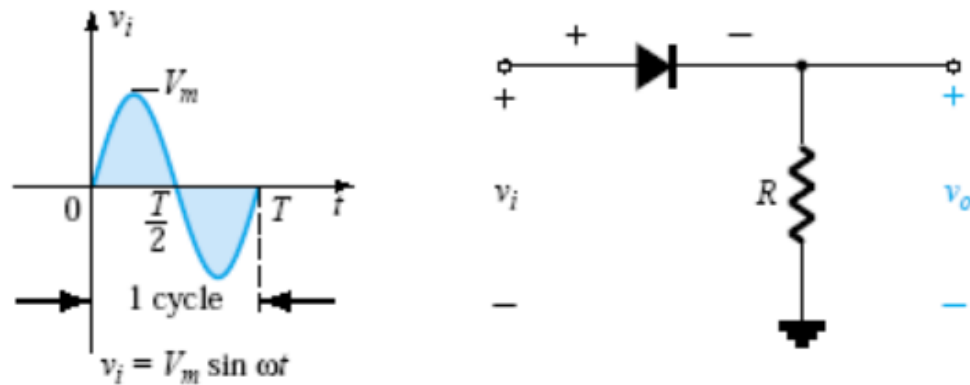


Figure 2.43 Half-wave rectifier.

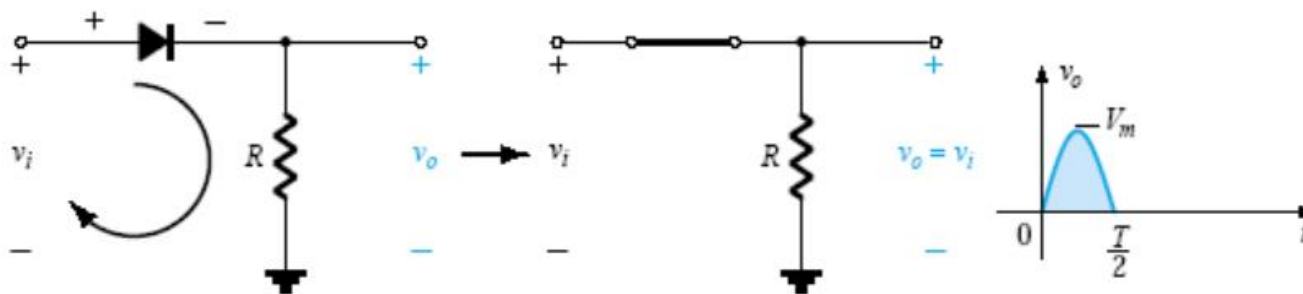


Figure 2.44 Conduction region ( $0 \rightarrow T/2$ ).

# HWR (continue..)

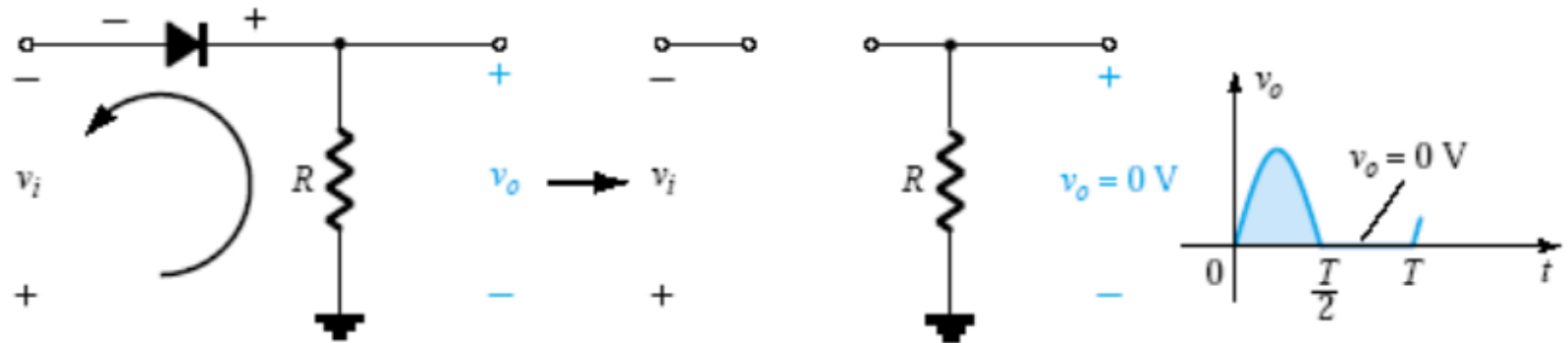


Figure 2.45 Nonconduction region ( $T/2 \rightarrow T$ ).


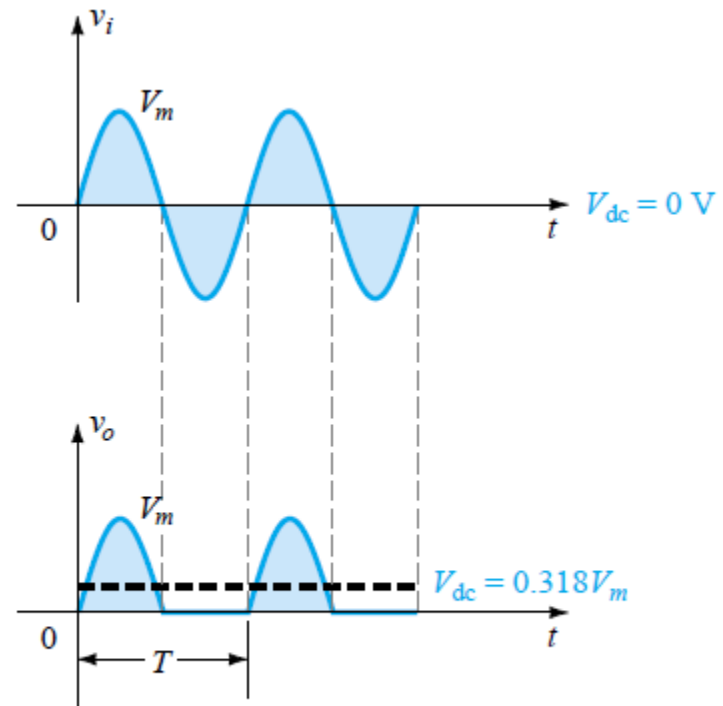


Figure 2.46 Half-wave rectified signal.

# HWR (continue..)

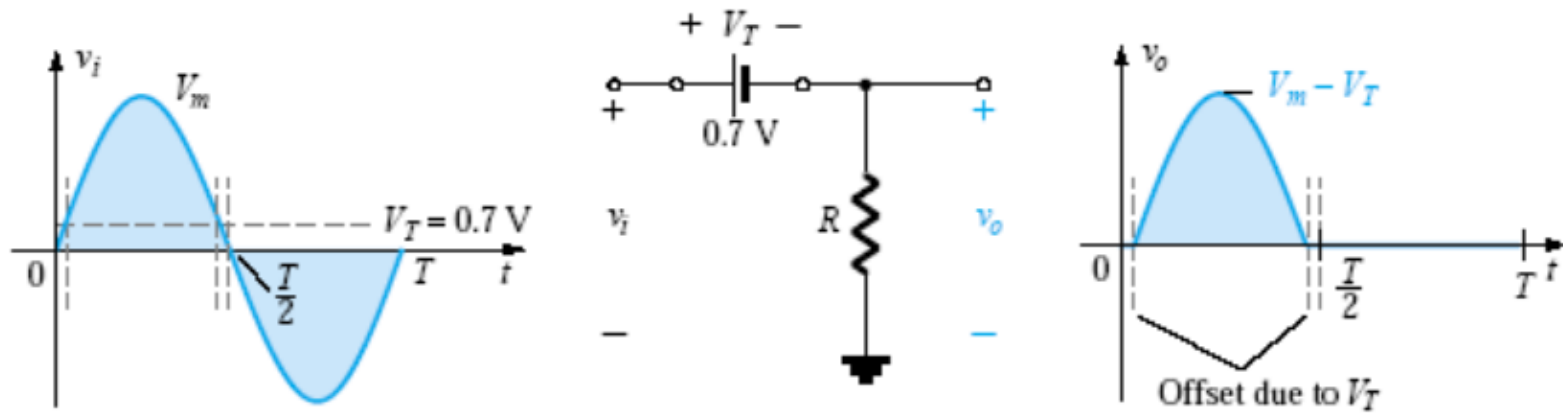

**Figure 2.47** Effect of  $V_T$  on half-wave rectified signal.

# Dc output

---

- Average or dc value of a signal is-

$$V_{dc} = \frac{1}{T} \int_0^T V_m \sin t dt$$

- For half wave rectifier,

$$V_{dc} = \frac{1}{T} \left[ \int_0^{T/2} V_m \sin t dt + \int_{T/2}^T 0 dt \right] = \frac{V_m}{\pi} = 0.318V_m$$


For practical diode,

$$V_{dc} \cong 0.318(V_m - V_T)$$

# PRV/PRV of Diode



$$\text{PIV rating} \geq V_m \quad \text{half-wave rectifier}$$

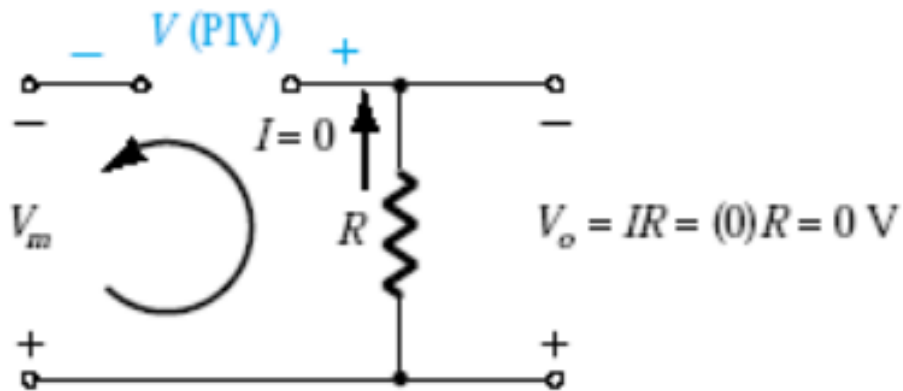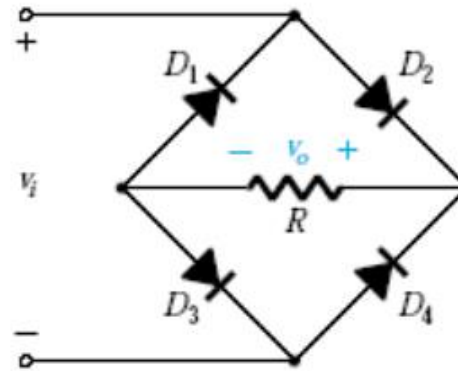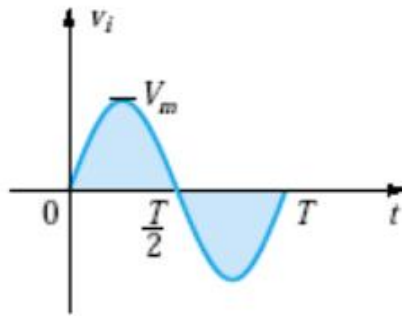(2.9)



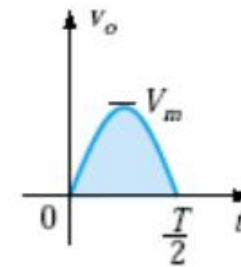


**Figure 2.51** Determining the required PIV rating for the half-wave rectifier.

# Full Wave Bridge Rectifier

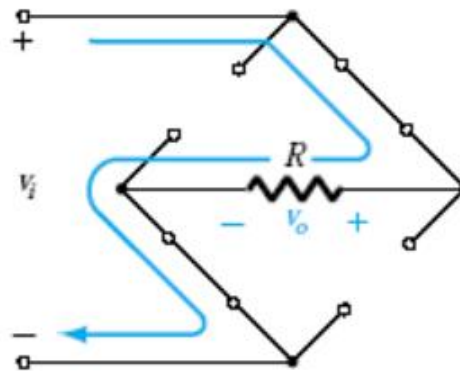


**Figure 2.52** Full-wave bridge rectifier.

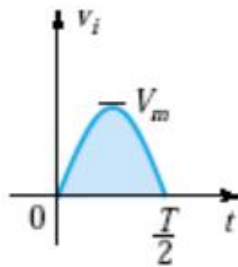


**Figure 2.54** Conduction path for the positive region of  $v_i$ .



# FWBR (continue..)

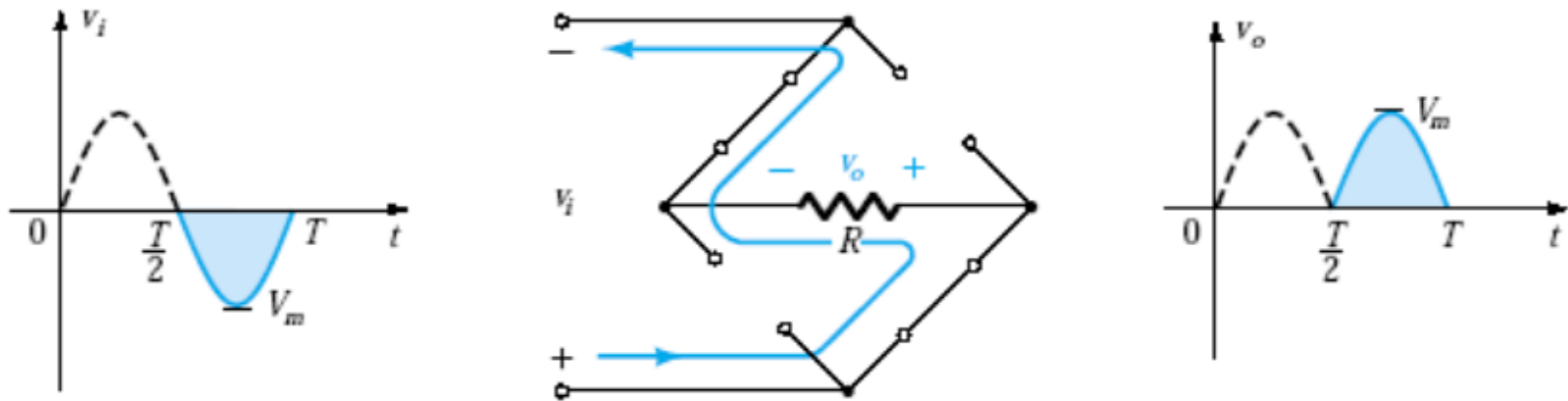

**Figure 2.55** Conduction path for the negative region of  $v_i$ .

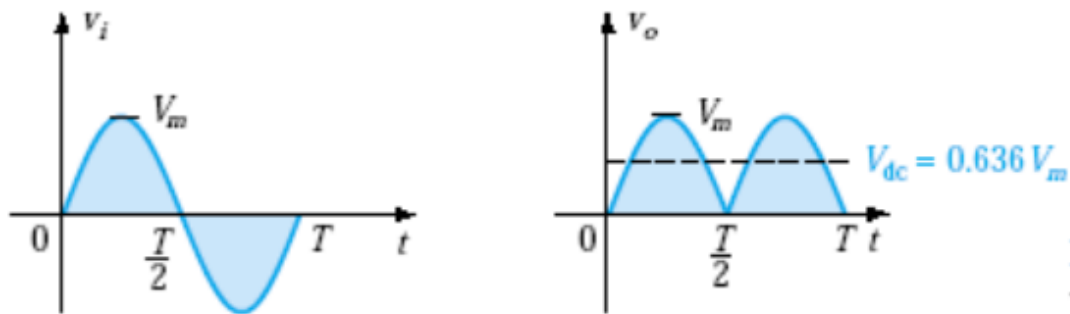

**Figure 2.56** Input and output waveforms for a full-wave rectifier.

# Dc Output

---

- Twice as that of a half wave rectifier.

$$V_{dc} = 2(\text{Eq. 2.7}) = 2(0.318 V_m)$$

$$\boxed{V_{dc} = 0.636 V_m} \text{ full-wave} \quad (2.10)$$

- Needs 4 diodes and a resistor.
- Transformer is necessary to step down the input voltage for direct line voltage rectification using ordinary diodes.
- PIV equals  $V_m$ , same as half wave rectifier.

# FWBR using practical diodes

Applying KVL

$$v_i - V_T - v_o - V_T = 0$$

and


$$v_o = v_i - 2V_T$$

The peak value of the output voltage  $v_o$  is therefore

$$V_{o_{\max}} = V_m - 2V_T$$

For situations where  $V_m \gg 2V_T$ , Eq. (2.11) can be applied for the average value with a relatively high level of accuracy.

$$V_{\text{dc}} \cong 0.636(V_m - 2V_T) \quad (2.11)$$

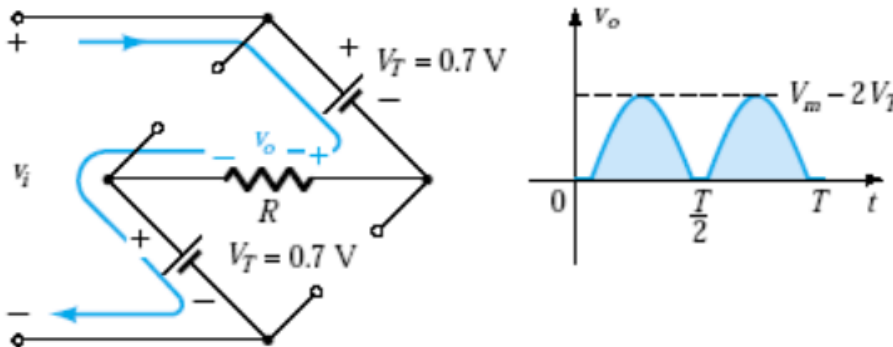

**Figure 2.57** Determining  $V_{o_{\max}}$  for silicon diodes in the bridge configuration.

Then again, if  $V_m$  is sufficiently greater than  $2V_T$ , then Eq. (2.10) is often applied as a first approximation for  $V_{\text{dc}}$ .

# Center-tap Transformer Rectifier

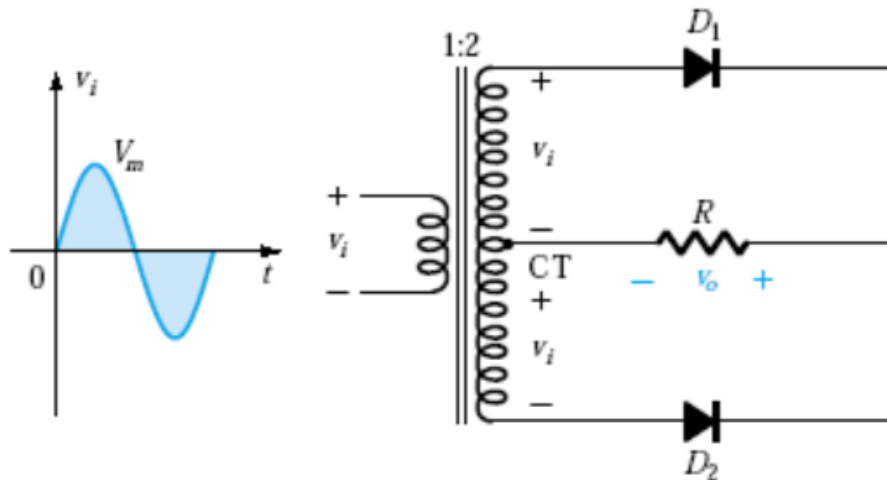


Figure 2.59 Center-tapped transformer full-wave rectifier.


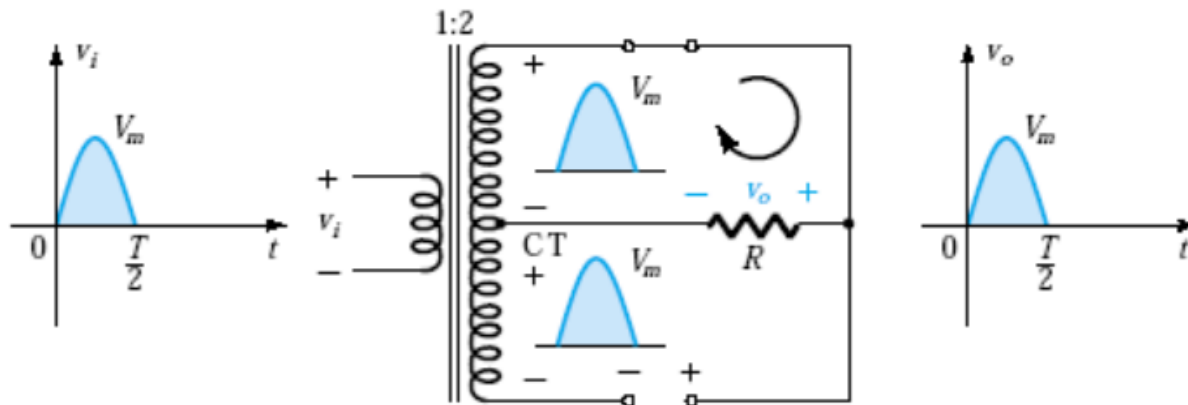


Figure 2.60 Network conditions for the positive region of  $v_i$ .

# CTTR (continue..)

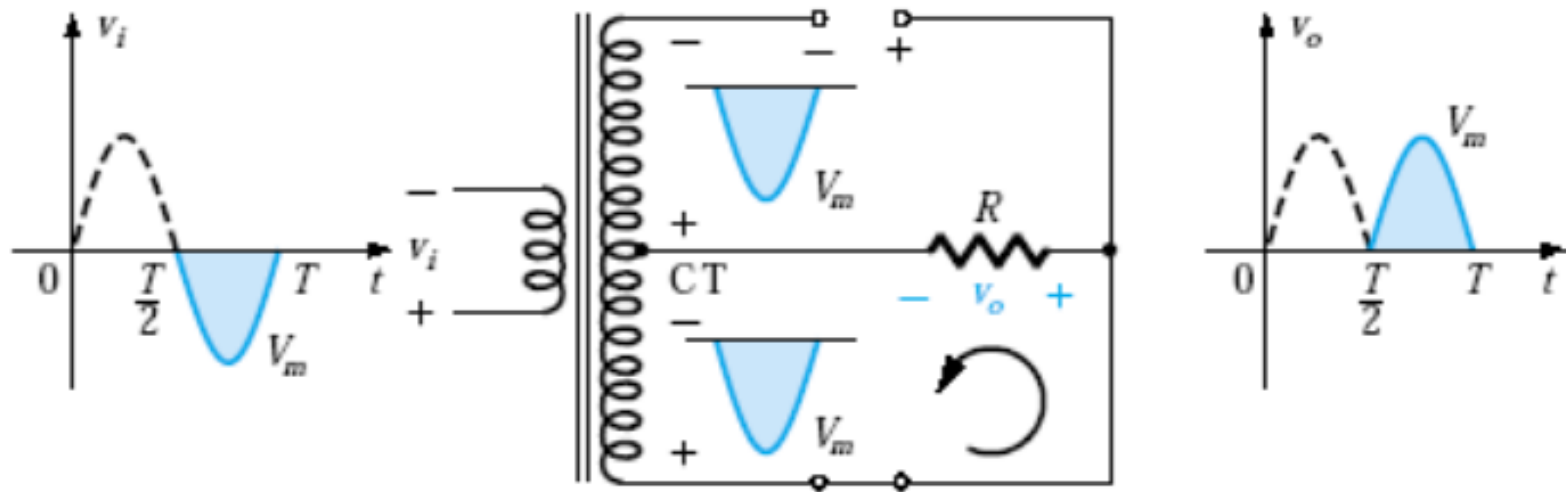


**Figure 2.61** Network conditions for the negative region of  $v_i$ .

# PIV of Diodes

$$\begin{aligned}\text{PIV} &= V_{\text{secondary}} + V_R \\ &= V_m + V_m\end{aligned}$$

$$\text{PIV} \cong 2V_m$$




CT transformer, full-wave rectifier

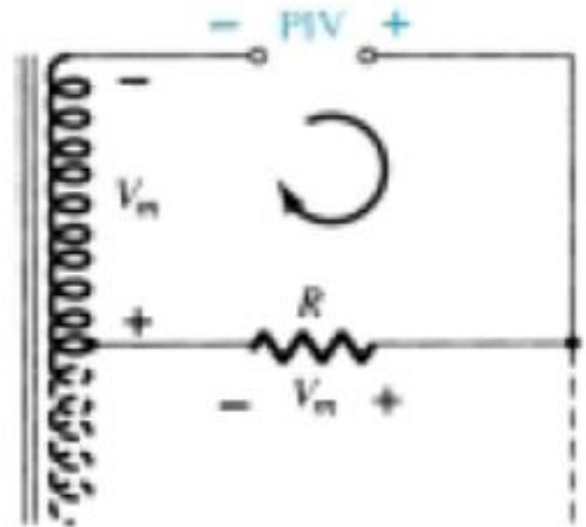



**Figure 2.62** Determining the PIV level for the diodes of the CT transformer full-wave rectifier.

# Oscilloscope display


---

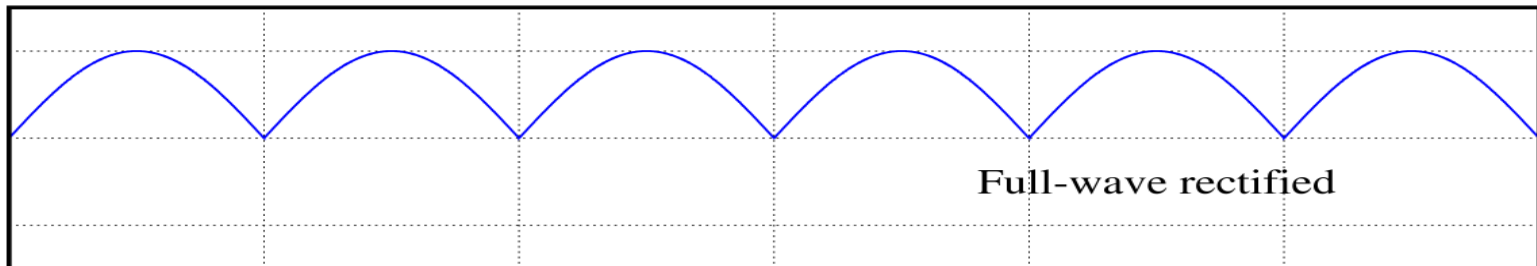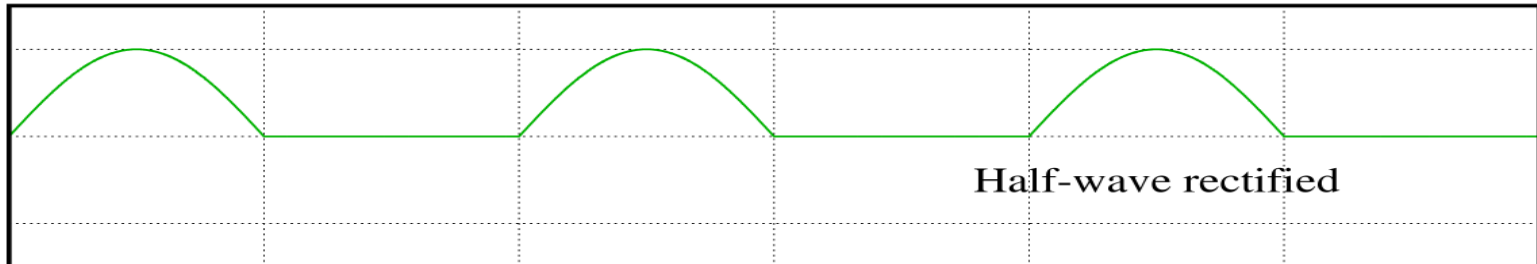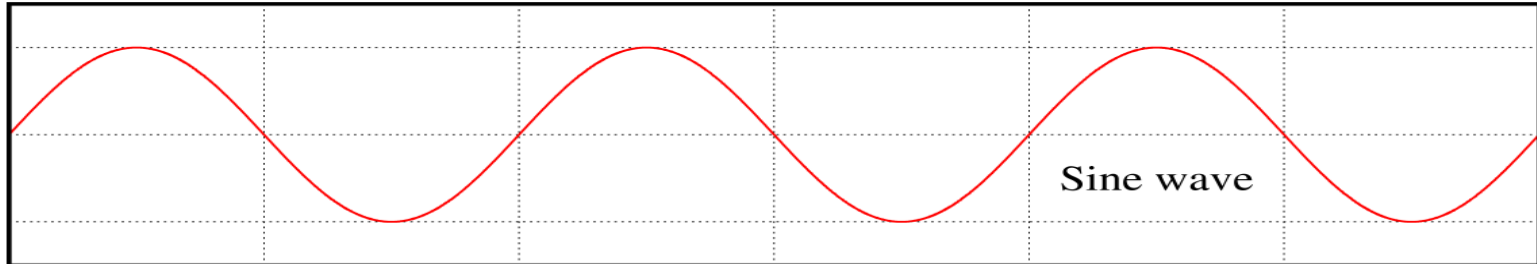

# HWR with capacitor filter

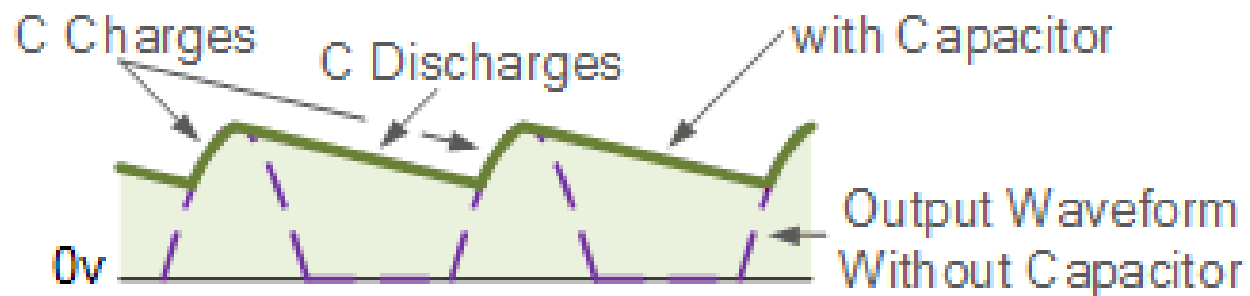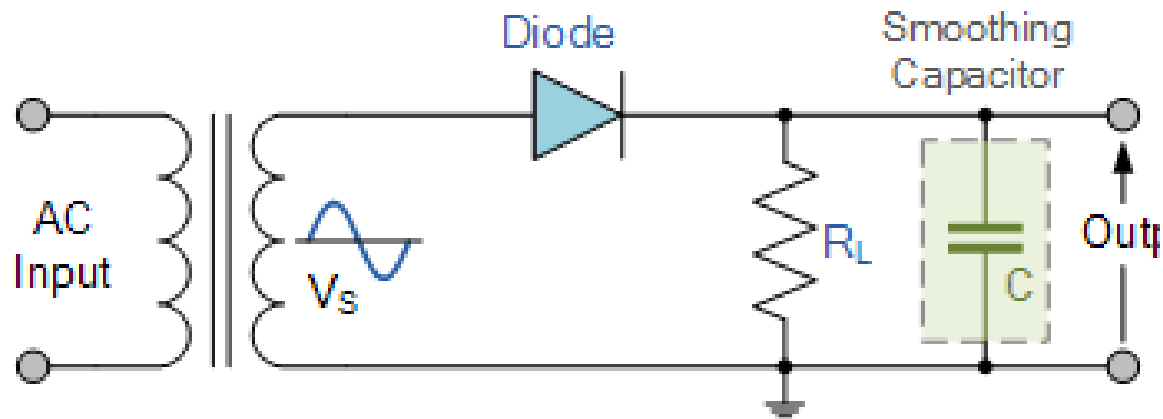



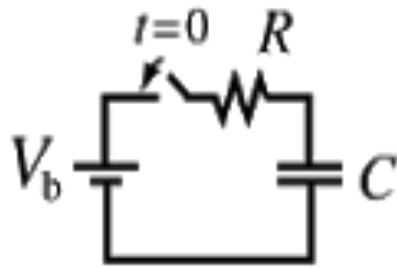

$$V_b = V_R + V_C$$


$$V_b = IR + \frac{Q}{C}$$

As charging progresses,

$$V_b = IR + \frac{Q}{C}$$

↓
↑

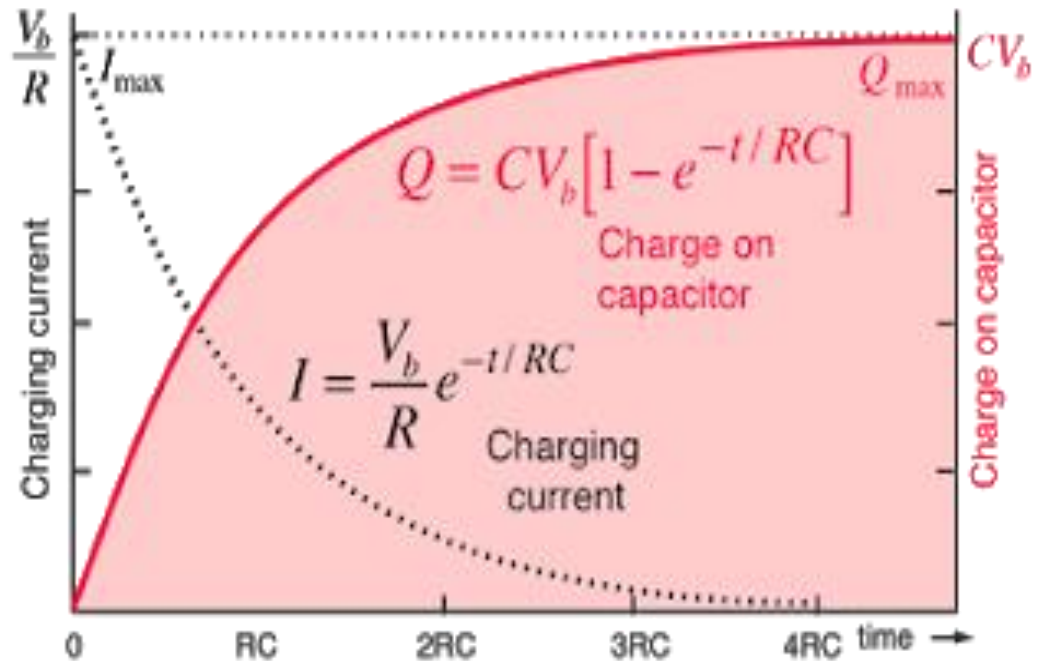current decreases and  
charge increases.



At  $t = 0$

$$Q = 0$$

$$V_C = 0$$

$$I = \frac{V_b}{R}$$


As  $t \rightarrow \infty$

$$Q \rightarrow CV_b$$

$$V_C \rightarrow V_b$$

$$I \rightarrow 0$$

# FWR with capacitor filter

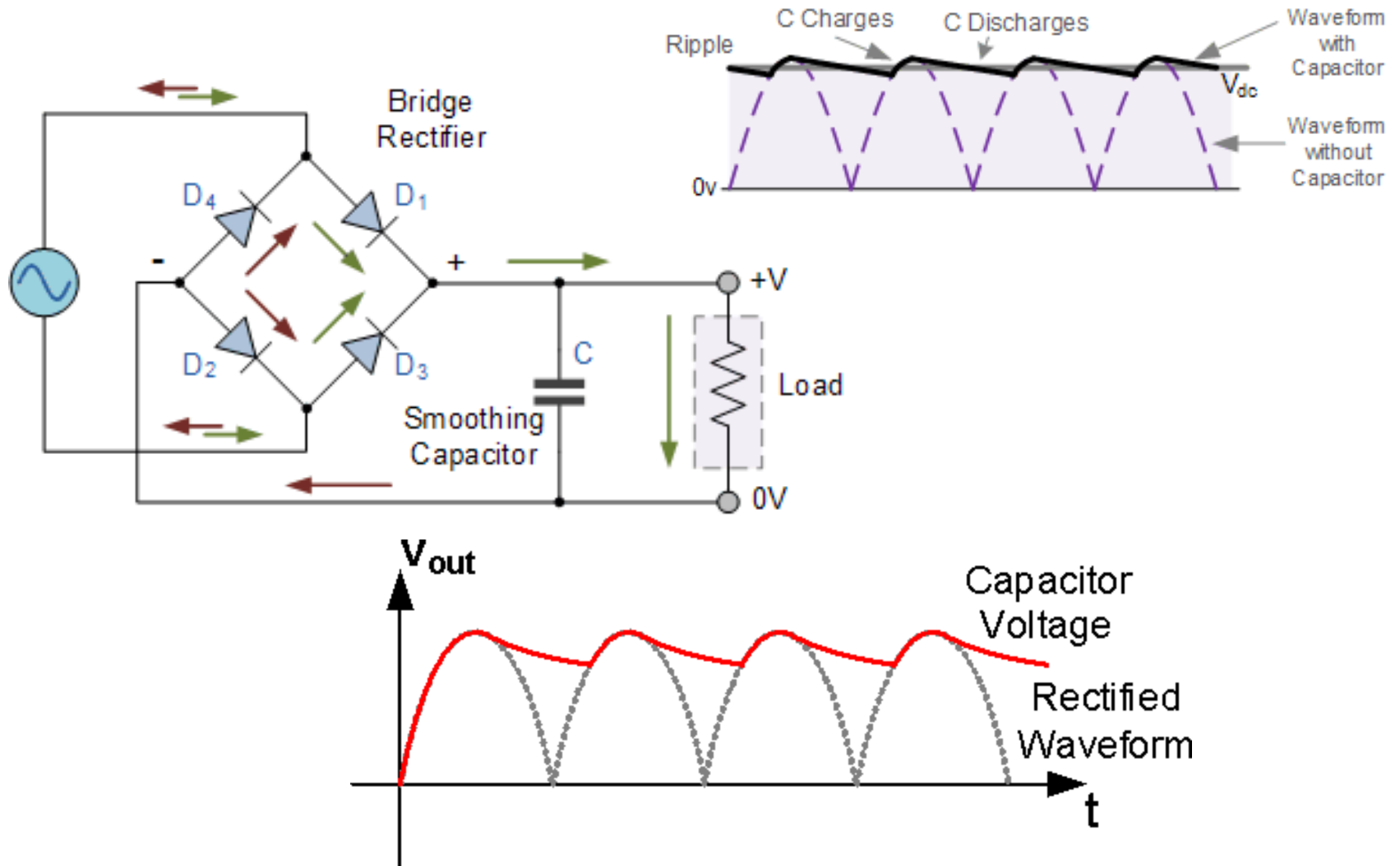

# Comparison

---

	HWR	FWBR	FWCTTR
Available dc	$0.318V_m$	$0.636V_m$	$0.636V_m$
Ripple with filter capacitor	More	Less	Less
PIV of diode	$\geq V_m$	$\geq V_m$	$\geq 2V_m$
No of diodes	1	4	2
Conversion efficiency	Less	More	More

# Efficiency (Half-Wave and Full-Wave Rectifiers)

$$\text{Efficiency } (\eta) = \frac{\text{DC Output Power}}{\text{AC Input Power}}$$

$$\text{DC Output Power of Half Wave Rectifier} = V_o \cdot I_o = (I_o)^2 \cdot R_L$$

$$\text{AC Input Power of Half Wave Rectifier} = V_{or} \cdot I_{or} = (I_{or})^2 \cdot R_L$$

$$\text{Efficiency } (\eta) = \frac{V_o \cdot I_o}{V_{or} \cdot I_{or}} = \frac{(I_o)^2 \cdot R_L}{(I_{or})^2 \cdot R_L}$$


Assuming Diode used in this circuit is ideal means its forward resistance ( $R_F$ ) is 0.

$$\text{Efficiency } (\eta) = \frac{(V_m / \pi)^2}{(V_m / 2)^2} = \frac{4}{\pi^2} = 40.5\%$$

$$\begin{aligned} \eta \% &= \frac{P_{\text{Load}}}{P_{\text{in}}} \times 100\% \\ &= \frac{I_{dc}^2 R}{I_{rms}^2 R} \times 100\% \\ &= \frac{I_m^2 / \pi^2}{I_m^2 / 4} \times 100\% = \frac{4}{\pi^2} \times 100\% \\ \eta \% &= 40.56\% \end{aligned}$$

$P = VI$   
 $P = I^2 R$   
 $I_{dc} = I_m / \pi$   
 $I_{rms} = I_m / 2$

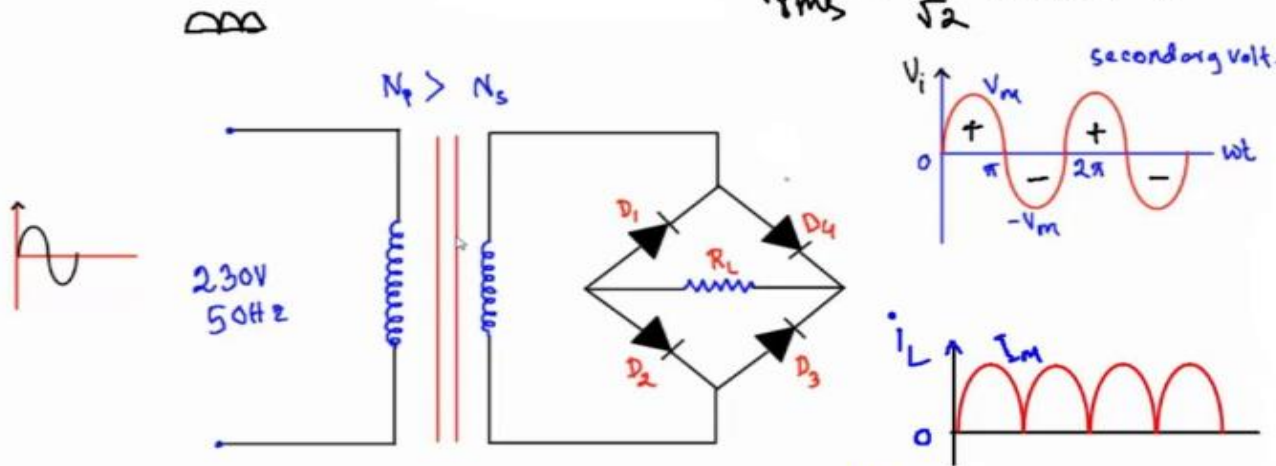Transformer Utilization Factor of Full Wave Rectifier:



$$TUF = 0.812 = \frac{P_{dc}}{P}$$

$$\begin{aligned} TUF &= \frac{I_{dc}^2 R_L}{V_{rms} I_{rms}} \\ &= \frac{\frac{4I_m^2}{\pi^2} \times R_L}{\frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}}} \\ &= \frac{8 I_m^2 R_L}{\pi^2 \times I_m \times V_m} \\ &= \frac{8 I_m R_L}{\pi^2 V_m} \\ &= \frac{8 V_m}{\pi^2 V_m} = 0.812 \end{aligned}$$

# Ripple factor

---

The ripple factor for a half-wave rectifier is 1.21.


This value indicates the degree of AC ripple present in the rectified output, with a higher value suggesting a greater AC content.

The ripple factor of a full-wave rectifier is 0.48.

This value is a measure of the amount of AC ripple or fluctuations present in the DC output of a rectifier circuit.

A lower ripple factor indicates a cleaner, more stable DC output.

# Block diagram of ac to dc conversion

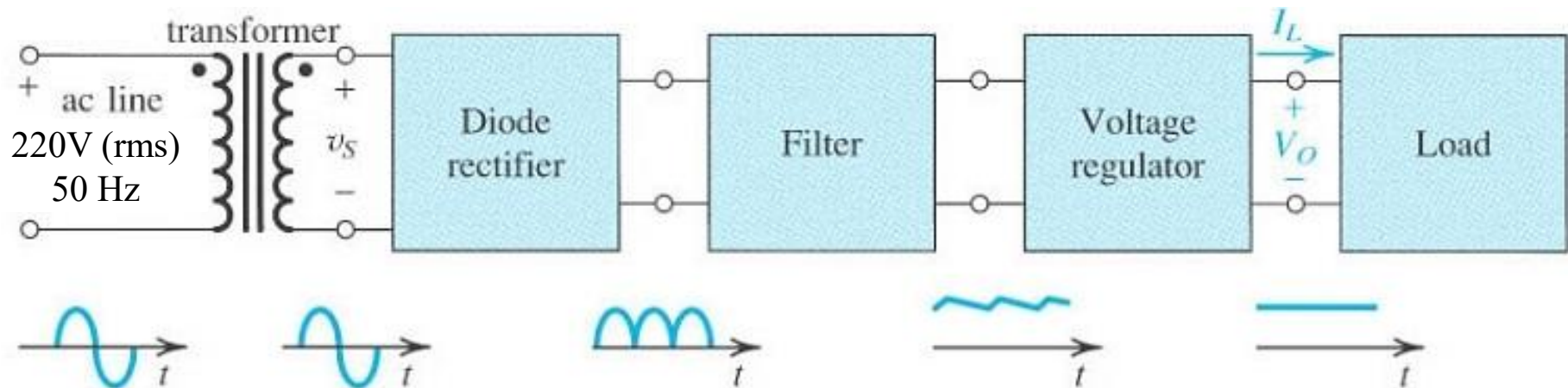

# Home work

---

- Solve problems at the end of Chapter 2
- Problem no 22, 23, 25, 26, 27, 29 and 31.

Thank You