

PRE-LAB REPORT

Experiment No : 07

Name of The Experiment : Experimental Study of op-amp-based integrator and differentiator.

1. Integrator:

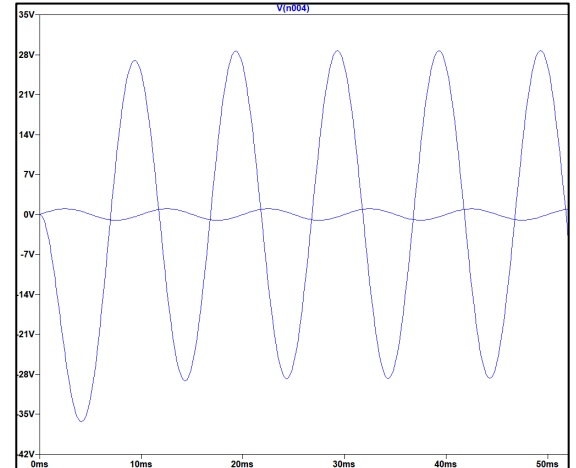
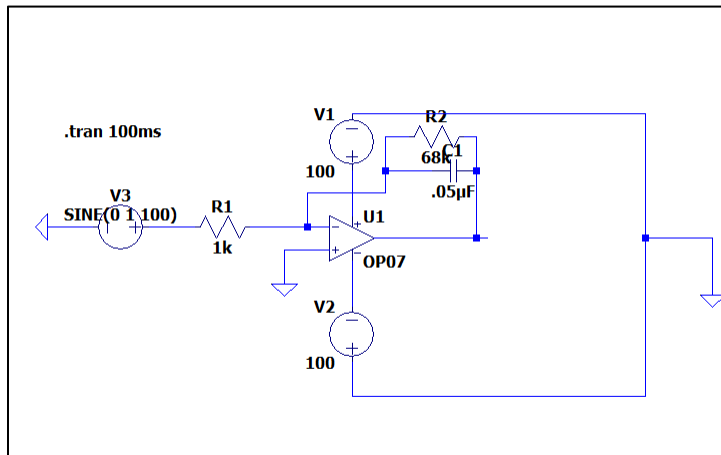


Fig - 01 : Integrator circuit and its input -output result

2. Differentiator:

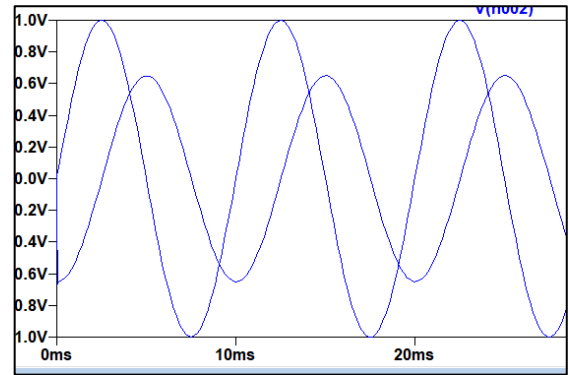
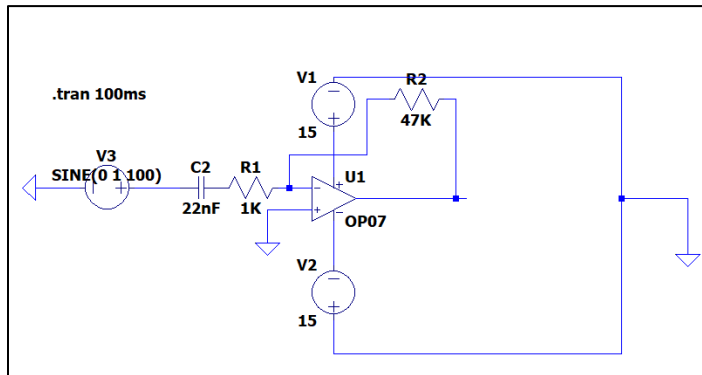


Fig - 02 : Differentiator circuit and its input and output result