

PRE-LAB REPORT

Experiment No : 08

Name of The Experiment : Experimental studies on Precision half wave and full wave rectifier.

Circuit Diagram :

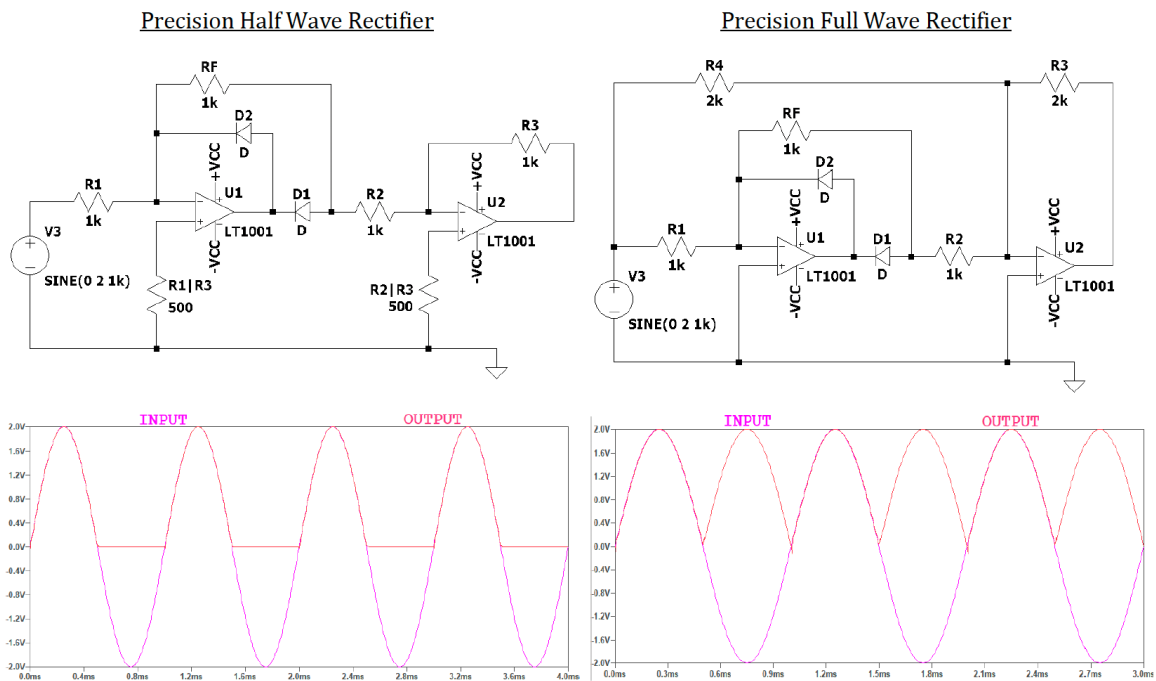


Fig - 01 : Input-Output