

# Bipolar Junction Transistor

Text Book

Electronic Devices and Circuit Theory

*By R. Boylestad and L. Nashelsky*

# History in brief

---

- 1904-1947: Vacuum tubes
- 23 December 1947: The amplifying action of the first transistor was demonstrated at Bell Tel Lab.
- It was a point-contact transistor
- It was smaller and lightweight,
- no heater requirement, hence, no heater loss
- It had a rugged construction
- It was more efficient due to less absorbed power
- Requiring no warm-up period
- The advantages of solid state devices

# The first transistor

---






# Present day Transistor Characteristics



---

- BJT abbreviates bipolar junction transistor
- Three terminals semiconductor device
- Bipolar device: bipolar reflects the fact that holes and electrons participate in injection process
- Current controlled device
- Types: PNP and NPN transistors
- Terminals are- emitter, base, and collector.
- Higher voltage gain
- Applications: amplification and switching

# PNP and NPN Transistor


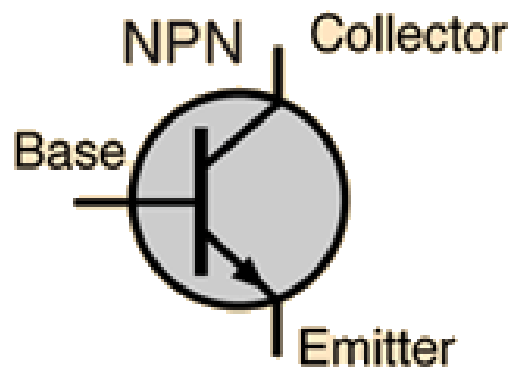
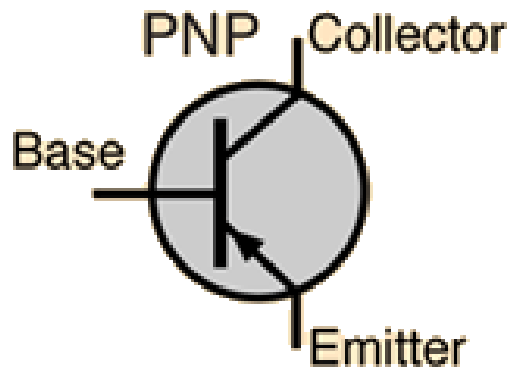
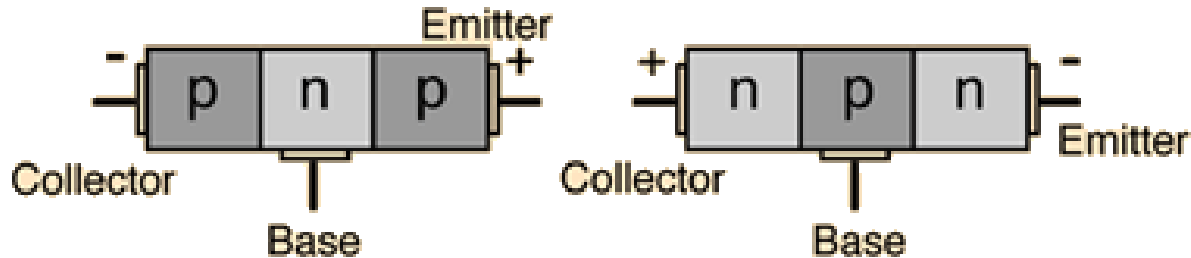


*Bipolar Junction Transistors*

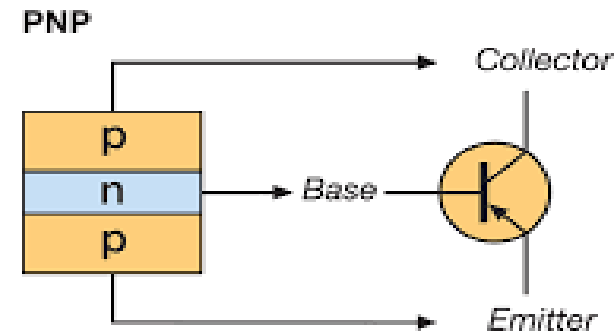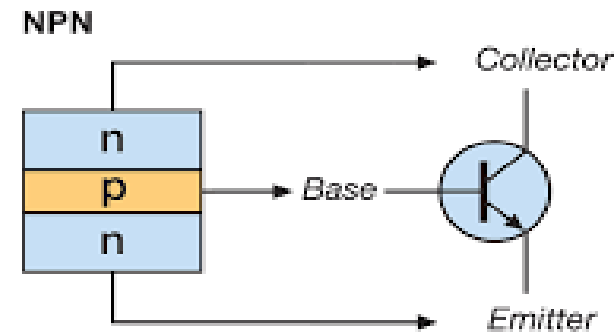

# Transistor equivalence diodes

---

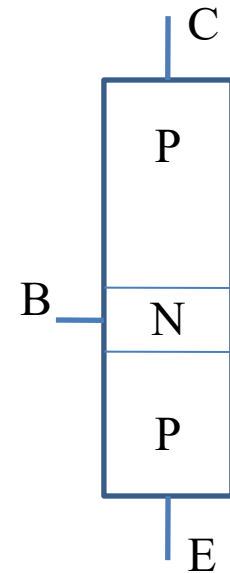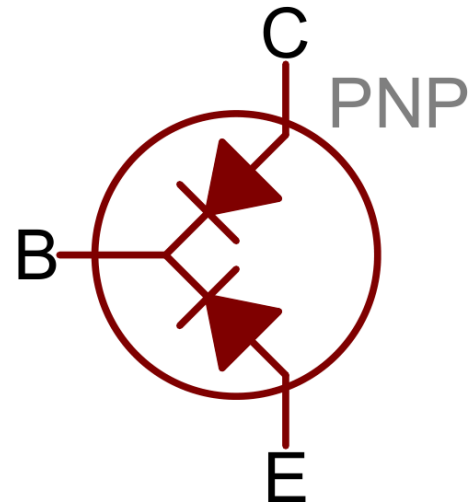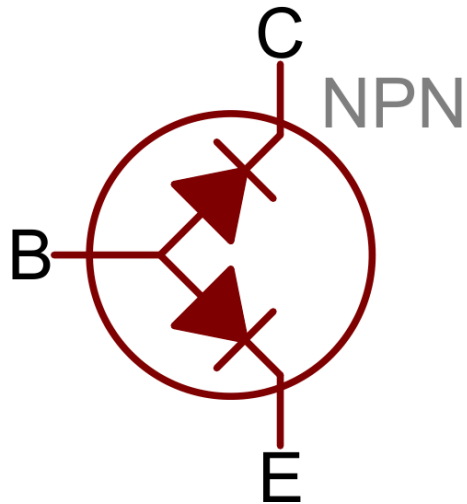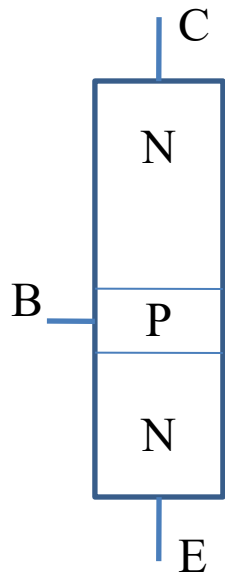

# Junction biasing

---

BE Junction	BC Junction	State of Operation
RB	RB	Cut-off
FB	RB	Active
RB	FB	Reverse-active
FB	FB	Saturation

# Biasing for amplification and switching

---

## BJT as a switch


1. Cut-off: BE and BC Junctions are reverse biased
2. Saturation: BE and BC Junctions are forward biased.

## Amplification (active mode)

- BE junction forward bias, BC reverse bias



# Operation in the active mode

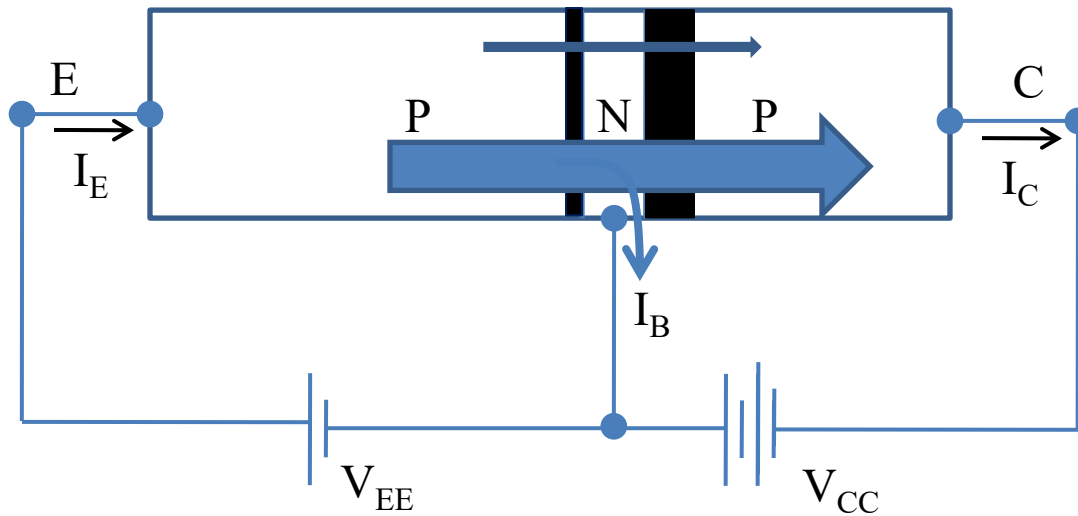

$$I_E = I_C + I_B$$

$$I_E = I_{C_{majority}} + I_{CO_{minority}}$$



# BJT configurations

---


- Common base (CB) configuration
- Common emitter (CE) configuration
- Common collector (CC) configuration
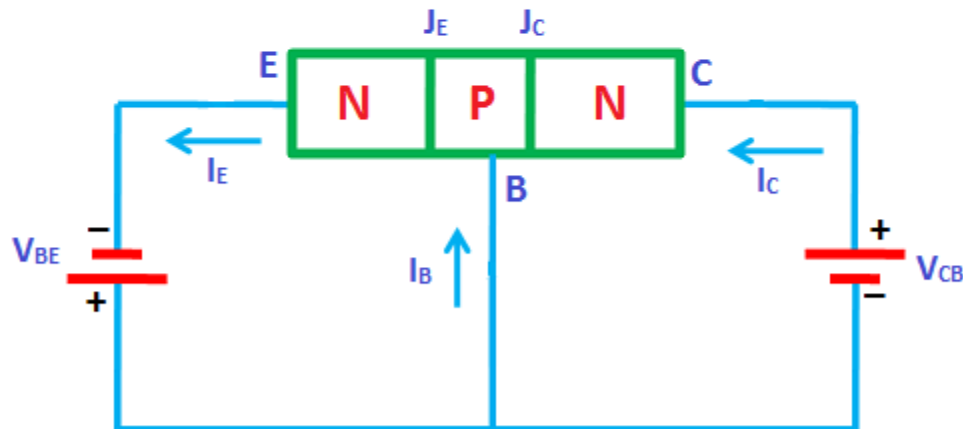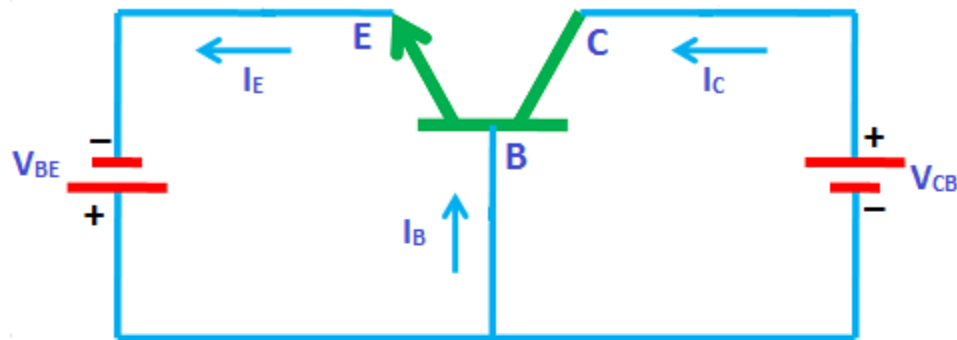
# CB Configuration

Sometimes common base configuration is referred to as common base amplifier, CB amplifier, or CB configuration.



Common base configuration

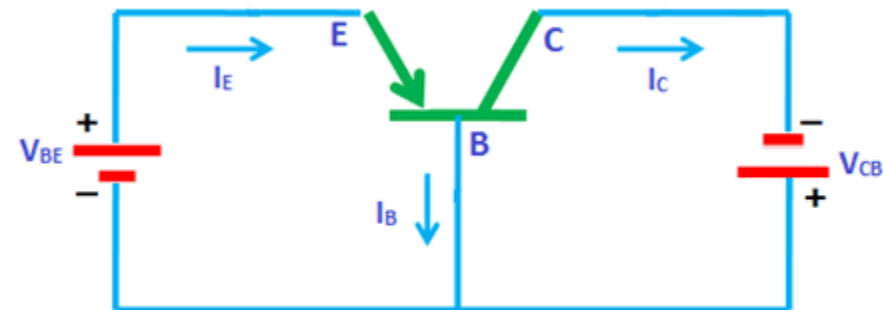


PNP transistor

Common base configuration

# CB Configuration

## Common-Base Configuration

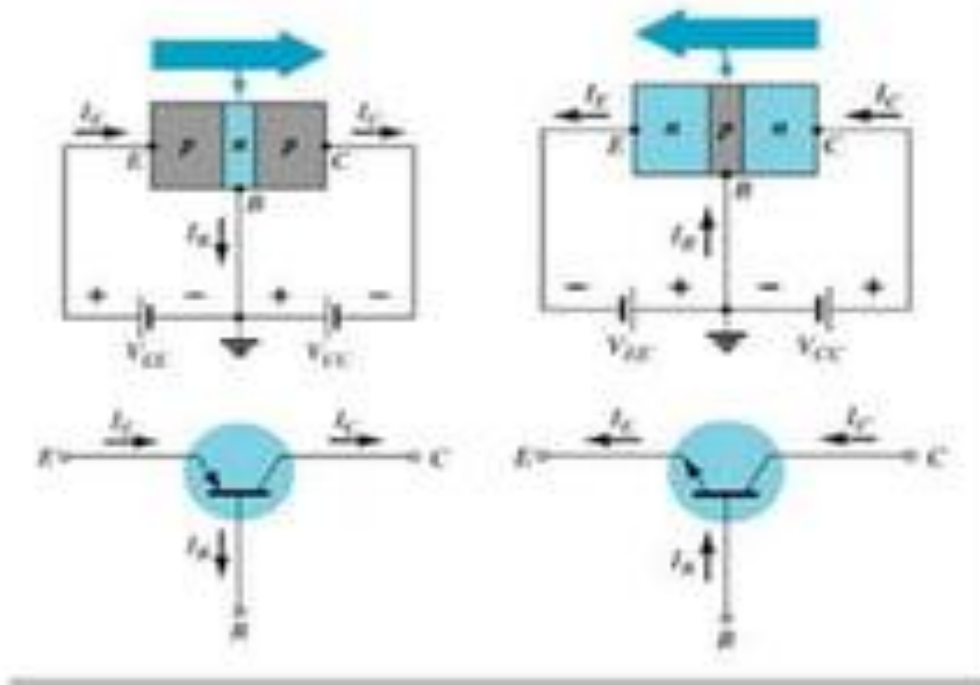


The arrow in the graphic symbol defines the direction of emitter current (conventional flow) through the device.

$$I_E = I_C + I_B$$


The emitter base junction is forward biased while collector base junction is reversed biased

$$I_C = I_{C_{\text{majority}}} + I_{C_{\text{minority}}}$$

# CB Configuration

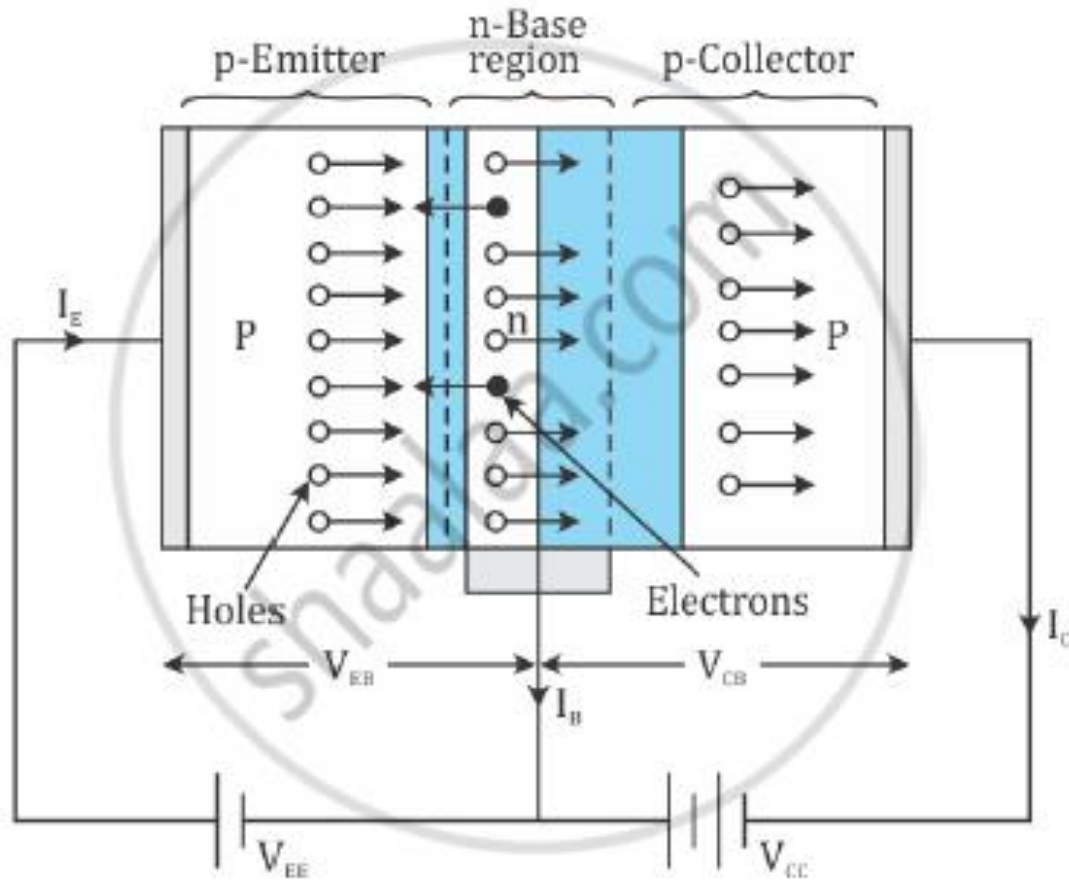




# CB Configuration

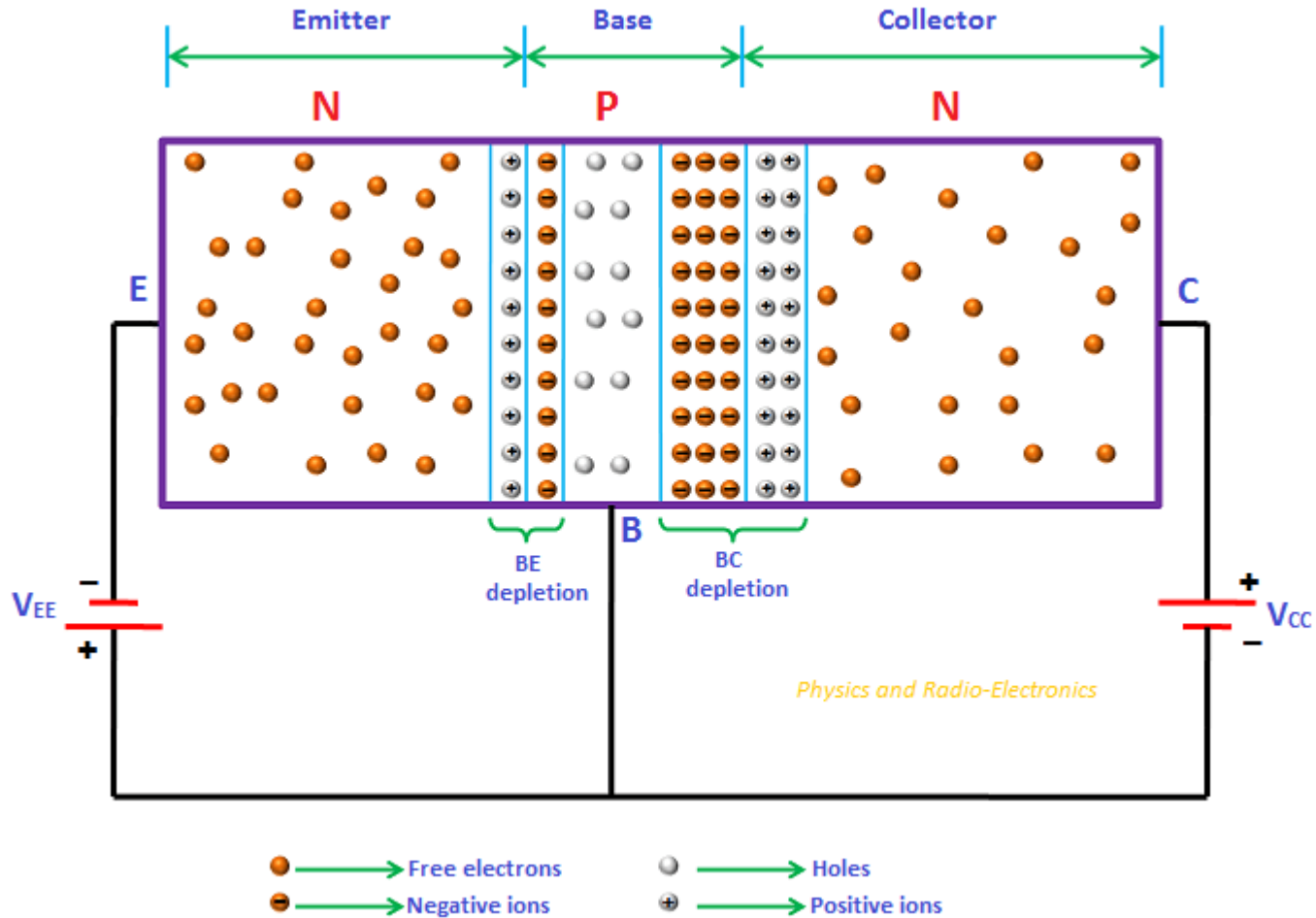

# CB Configuration

The emitter current is the sum of base current and collector current.


$$I_E = I_B + I_C$$

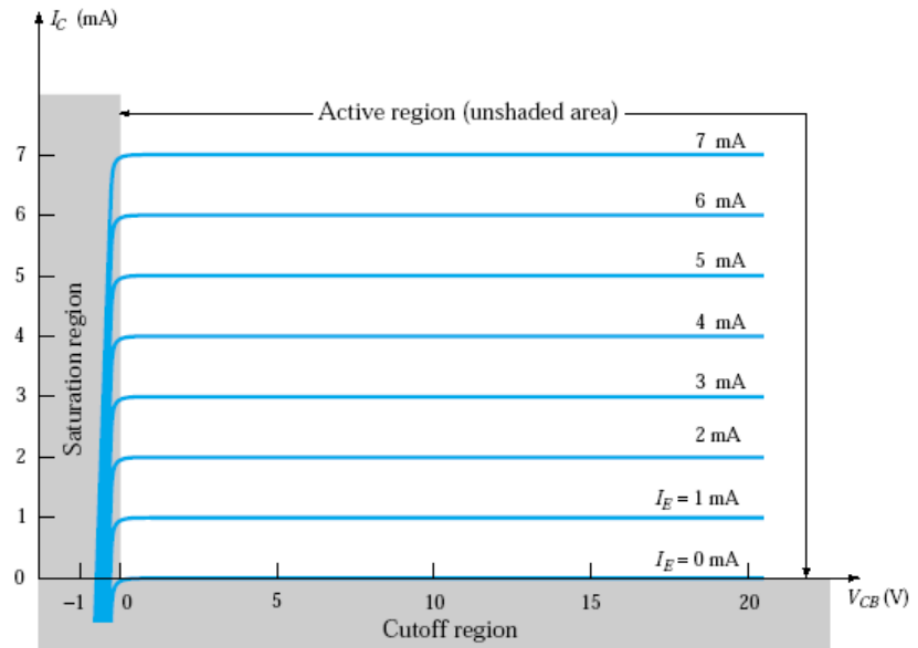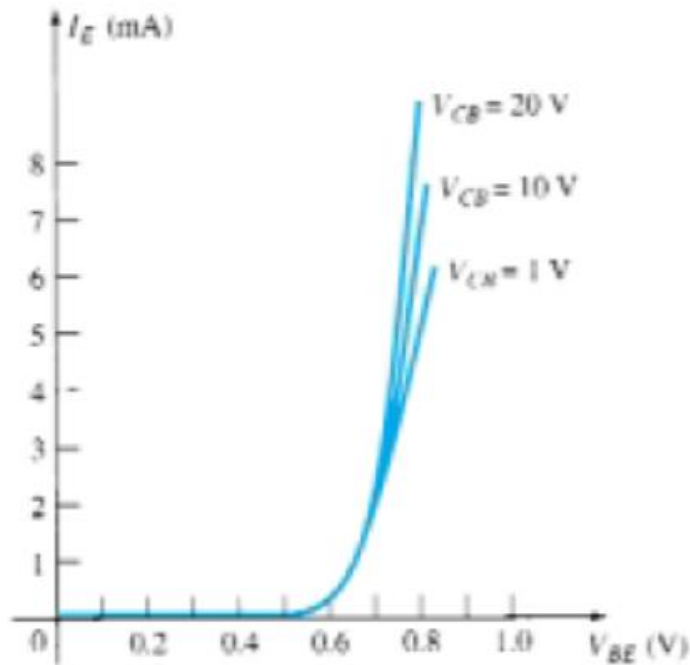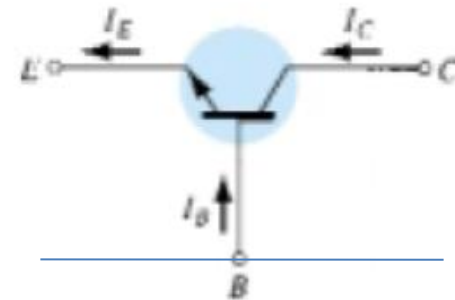

$$R_{in} = \frac{\Delta V_{BE}}{\Delta I_E}$$

Low input impedance

# BE Voltage

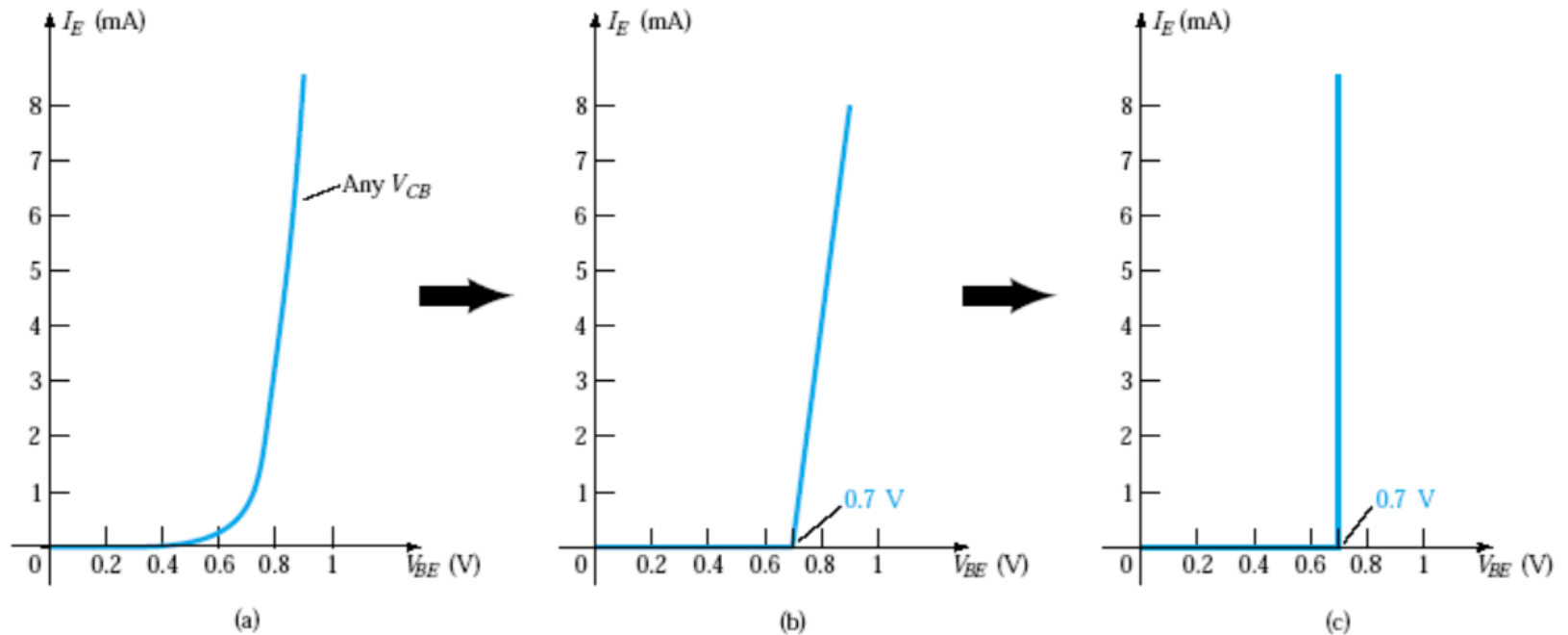

**Figure 3.10** Developing the equivalent model to be employed for the base-to emitter region of an amplifier in the dc mode.



# CB Configuration

---

Dynamic input resistance ( $r_i$ )

$$r_i = \frac{\Delta V_{BE}}{\Delta I_E}, \quad V_{CB} = \text{constant}$$

The input resistance of common base amplifier is very low.

Dynamic output resistance ( $r_o$ )

$$r_o = \frac{\Delta V_{CB}}{\Delta I_C}, \quad I_E = \text{constant}$$

The output resistance of common base amplifier is very high.

# Alpha ( $\alpha$ )

## DC mode,

In the dc mode the levels of  $I_C$  and  $I_E$  due to the majority carriers are related by a quantity called *alpha* and defined by the following equation:

$$\alpha_{dc} = \frac{I_C}{I_E}$$

Generally assume 1 but  
practically 0.90 to 0.998


$$I_C = \alpha I_E + I_{CBO}$$

## AC mode,

$$\alpha_{ac} = \left. \frac{\Delta I_C}{\Delta I_E} \right|_{V_{CB} = \text{constant}}$$

The ac alpha is formally called the *common-base, short-circuit, amplification factor*

# Basic amplification action

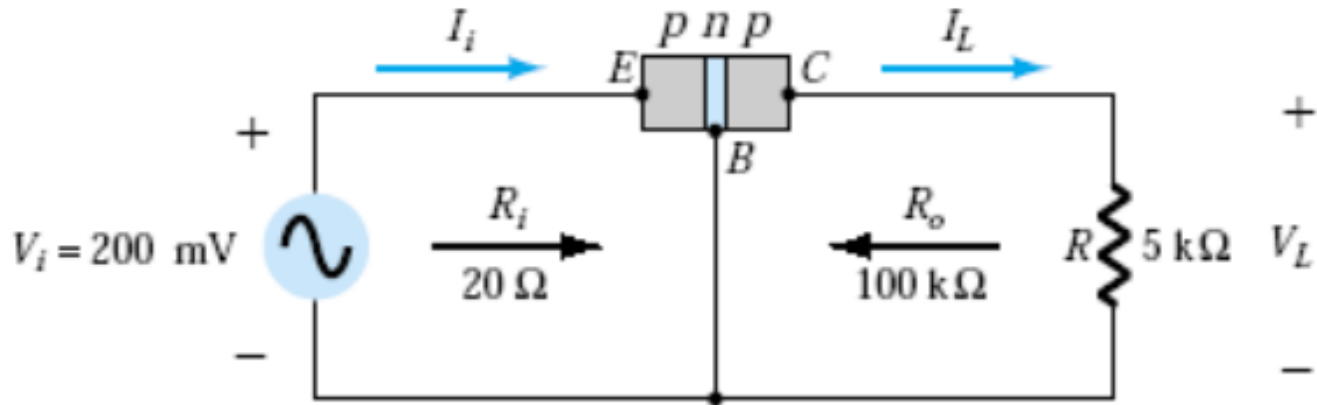

$$I_i = \frac{V_i}{R_i} = \frac{200 \text{ mV}}{20 \Omega} = 10 \text{ mA}$$

If we assume for the moment that  $\alpha_{ac} = 1$  ( $I_c = I_e$ ),





$$I_L = I_i = 10 \text{ mA}$$

and


$$\begin{aligned} V_L &= I_L R \\ &= (10 \text{ mA})(5 \text{ k}\Omega) \\ &= 50 \text{ V} \end{aligned}$$

*Transfer + Resistor  $\rightarrow$  Transistor*



# CE Configuration

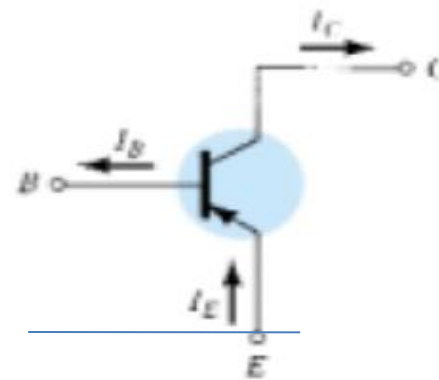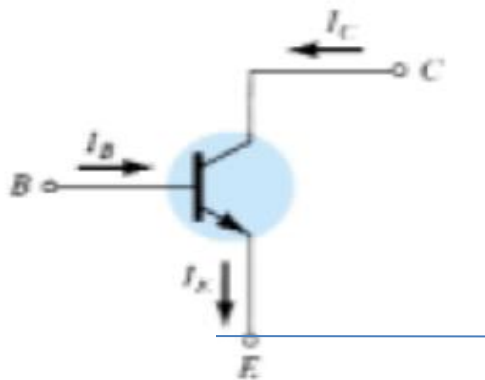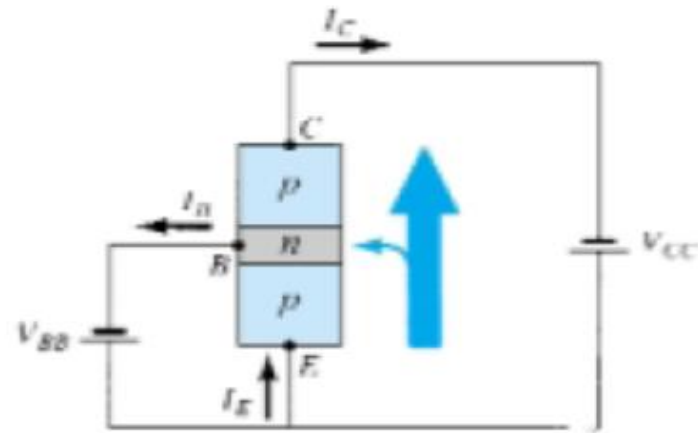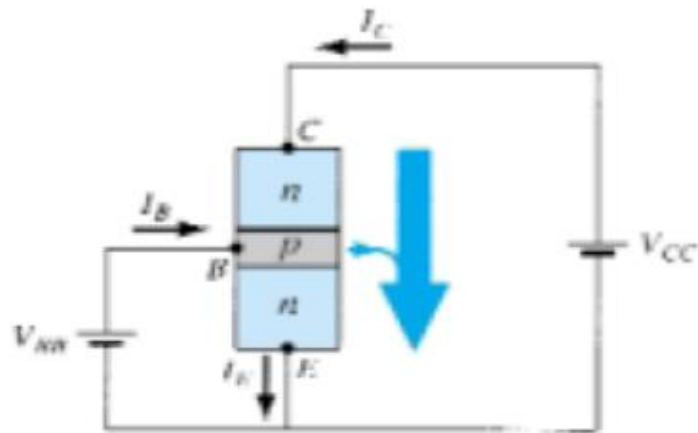

# CE Configuration

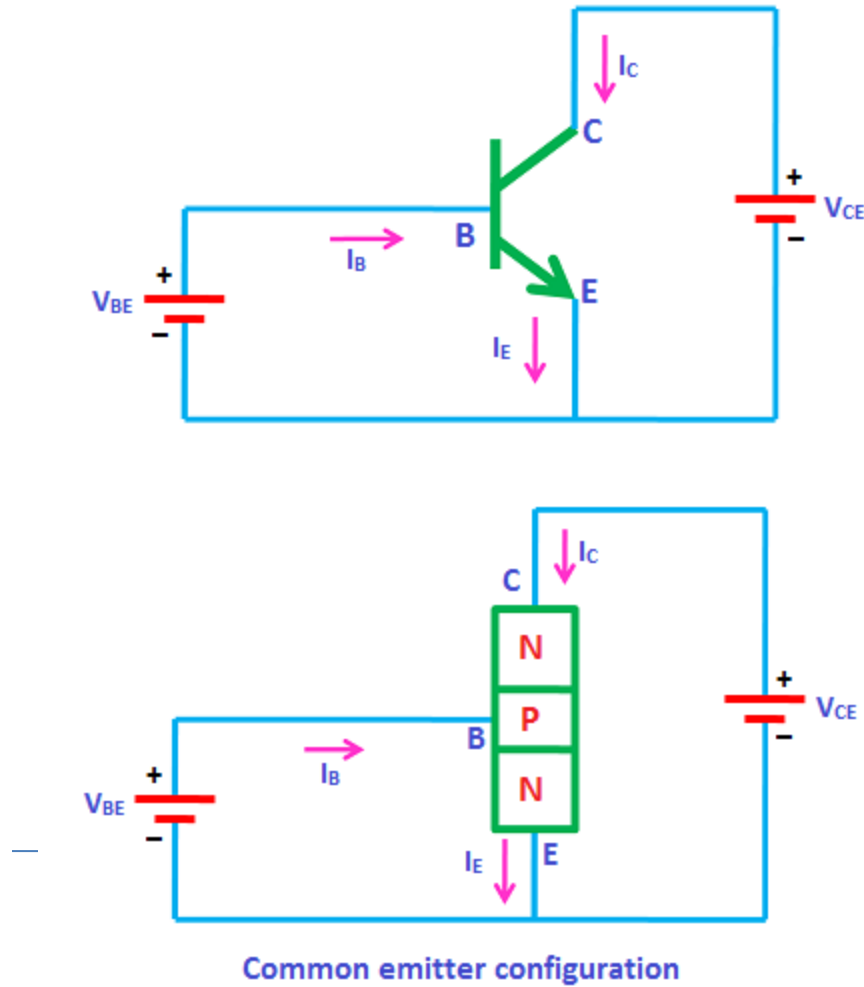

# Input and output characteristics

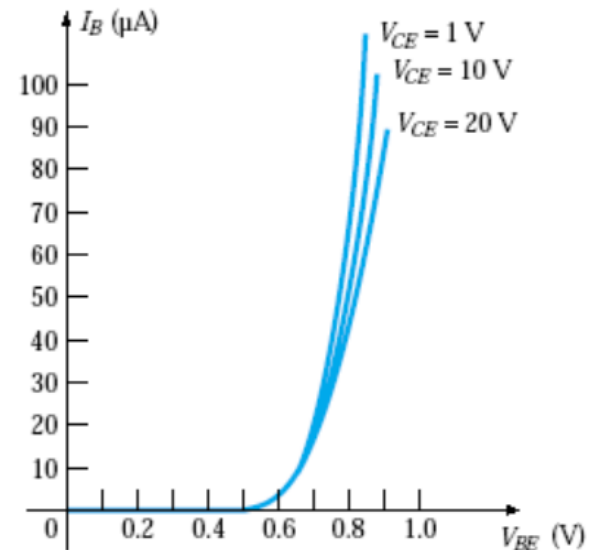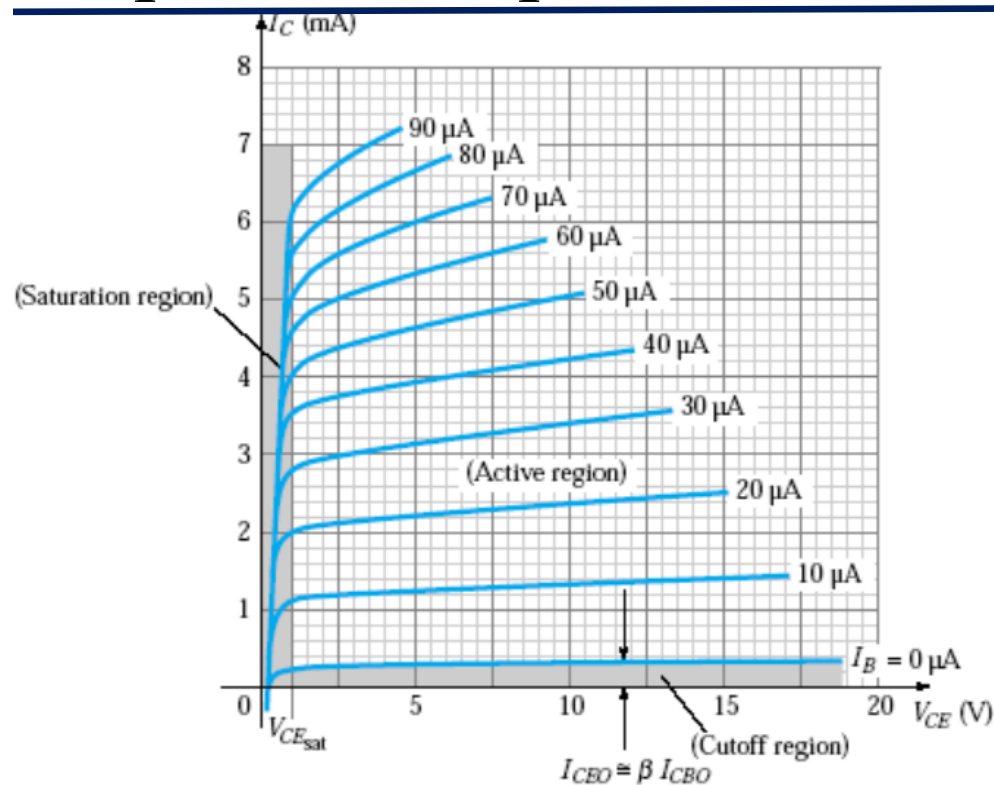

How  $I_C$  is high when  $I_B=0$  :

$$I_C = \alpha I_E + I_{CBO}$$

$$\Rightarrow I_C = \alpha (I_C + I_B) + I_{CBO}$$

$$\Rightarrow (1 - \alpha) I_C = \alpha I_B + I_{CBO}$$

$$\Rightarrow I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{1}{1 - \alpha} I_{CBO}$$

$$\Rightarrow I_C = \beta I_B + \frac{1}{1 - \alpha} I_{CBO}$$

$$= \frac{1}{1 - \alpha} I_{CBO}$$

$$= (\beta + 1) I_{CBO}$$

$$0.95 \rightarrow 0.99$$

$$\beta = \frac{\alpha}{1 - \alpha} \Rightarrow \beta + 1 = \frac{1}{1 - \alpha}$$

$$I_{CEO} = (\beta + 1) I_{CBO}$$

$$\Rightarrow I_{CEO} = 100 \mu A$$

$$\beta = 99$$

$$I_{CBO} = 1 \mu A$$

# Transistor Parameters

Dynamic input resistance ( $r_i$ )

$$r_i = \frac{\Delta V_{BE}}{\Delta I_B}, \quad V_{CE} = \text{constant}$$

In CE configuration, the input resistance is very low.

Dynamic output resistance ( $r_o$ )

$$r_o = \frac{\Delta V_{CE}}{\Delta I_C}, \quad I_B = \text{constant}$$

In CE configuration, the output resistance is high.

Moderate Current Gain  
Moderate Voltage Gain  
High Power Gain  
Moderate Input Impedance  
Moderate Output Impedance

# Beta ( $\beta$ )

---

## DC mode,

In the dc mode the levels of  $I_C$  and  $I_B$  are related by a quantity called *beta* and defined by the following equation:

$$\beta_{dc} = \frac{I_C}{I_B}$$

Range: 50 to 200

## AC mode,

For ac situations an ac beta has been defined as follows:

$$\beta_{ac} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE} = \text{constant}}$$

The formal name for  $\beta_{ac}$  is *common-emitter, forward-current, amplification factor*.



# Relationship between $\alpha$ and $\beta$

---

$$\alpha = \frac{I_C}{I_E}$$

$$\beta = \frac{I_C}{I_B}$$

$$I_E = I_C + I_B$$

$$\frac{I_C}{\alpha} = I_C + \frac{I_C}{\beta}$$

$$\frac{1}{\alpha} = 1 + \frac{1}{\beta}$$

$$\beta = \alpha\beta + \alpha = (\beta + 1)\alpha$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

# Collector and emitter current in terms of base current





---

$$I_C = \beta I_B$$



$$\begin{aligned} I_E &= I_C + I_B \\ &= \beta I_B + I_B \end{aligned}$$

$$I_E = (\beta + 1) I_B$$

# CC Configuration

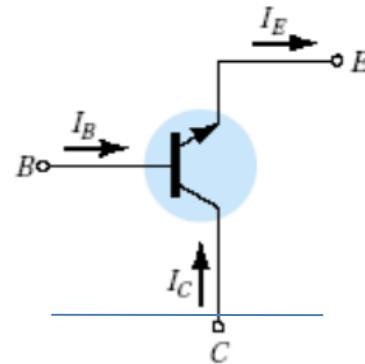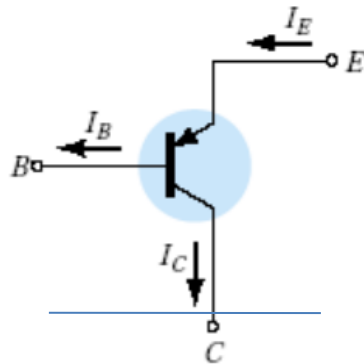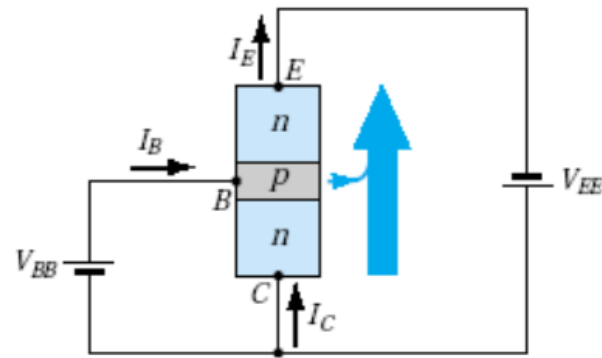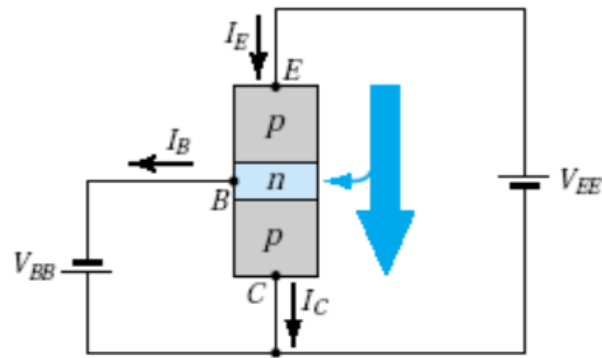

# CC Configuration

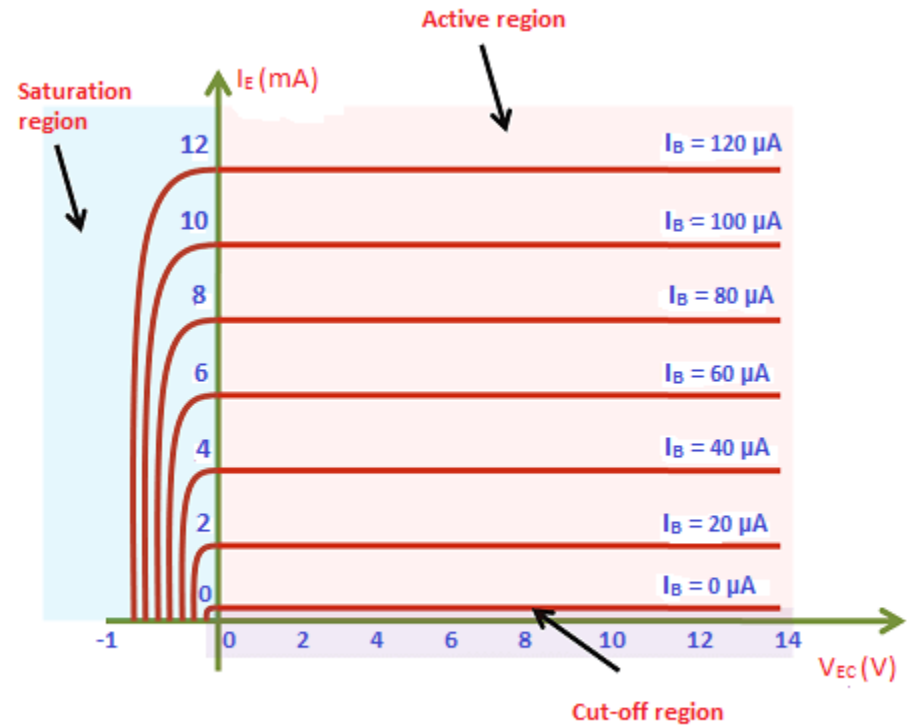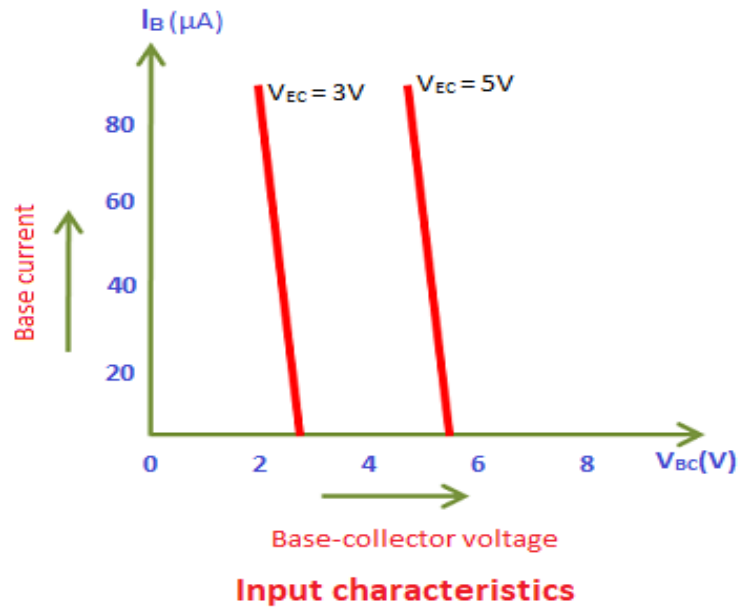

Output characteristics is similar to CE Conf.

High Input Impedance  
Low Output Impedance  
High Current Gain  
Low Voltage Gain  
Low Power Gain

Because :  
 $I_E = \alpha I_C$   
 $I_E \approx I_C$

# CC Configuration

---

Dynamic input resistance ( $r_i$ )

$$r_i = \frac{\Delta V_{BC}}{\Delta I_B}, \quad V_{EC} = \text{constant}$$

The input resistance of common collector amplifier is high.

Dynamic output resistance ( $r_o$ )

$$r_o = \frac{\Delta V_{EC}}{\Delta I_E}, \quad I_B = \text{constant}$$

The output resistance of common collector amplifier is low.

Current amplification factor ( $\gamma$ )

$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$

The current gain of a common collector amplifier is high.

Derive the relationship among three current gain for three types of configurations

# Limits of operation

$$V_{CE}I_C = 300 \text{ mW}$$

$$V_{CE}(50 \text{ mA}) = 300 \text{ mW}$$


$$V_{CE} = \frac{300 \text{ mW}}{50 \text{ mA}} = 6 \text{ V}$$

$$(20 \text{ V})I_C = 300 \text{ mW}$$

$$I_C = \frac{300 \text{ mW}}{20 \text{ V}} = 15 \text{ mA}$$

$$V_{CE}(25 \text{ mA}) = 300 \text{ mW}$$
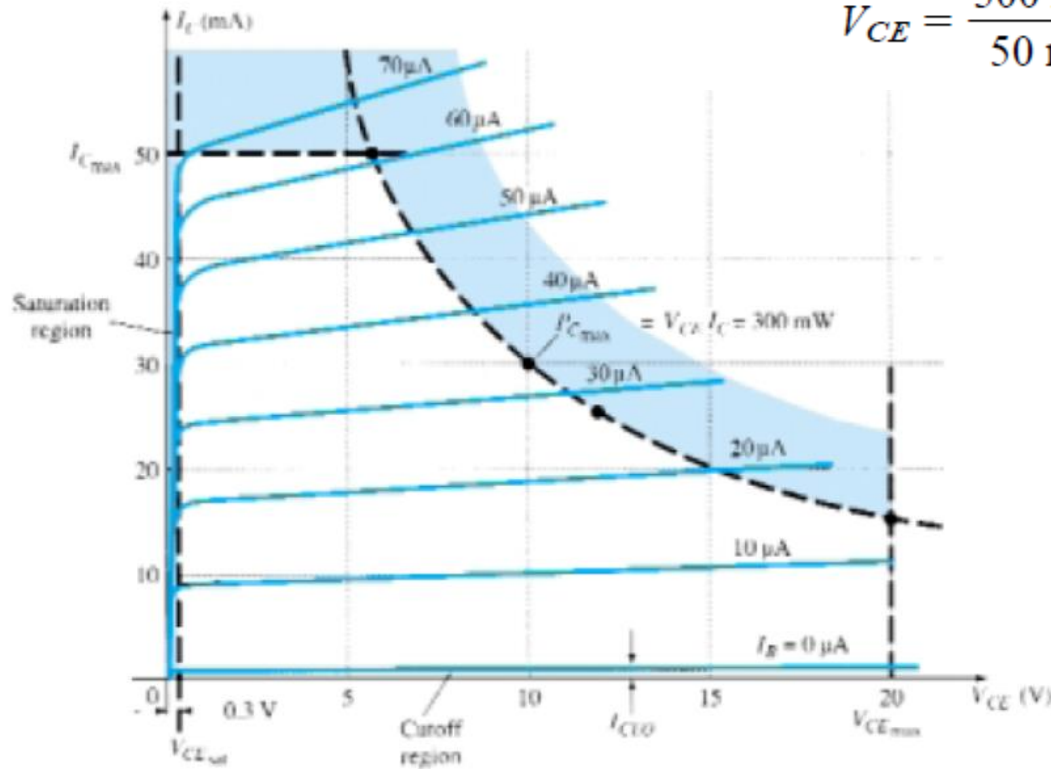
$$V_{CE} = \frac{300 \text{ mW}}{25 \text{ mA}} = 12 \text{ V}$$



$$I_{CEO} \leq I_C \leq I_{C_{\max}}$$

$$V_{CE_{\text{sat}}} \leq V_{CE} \leq V_{CE_{\max}}$$

$$V_{CE}I_C \leq P_{C_{\max}}$$

# Terminal Identification



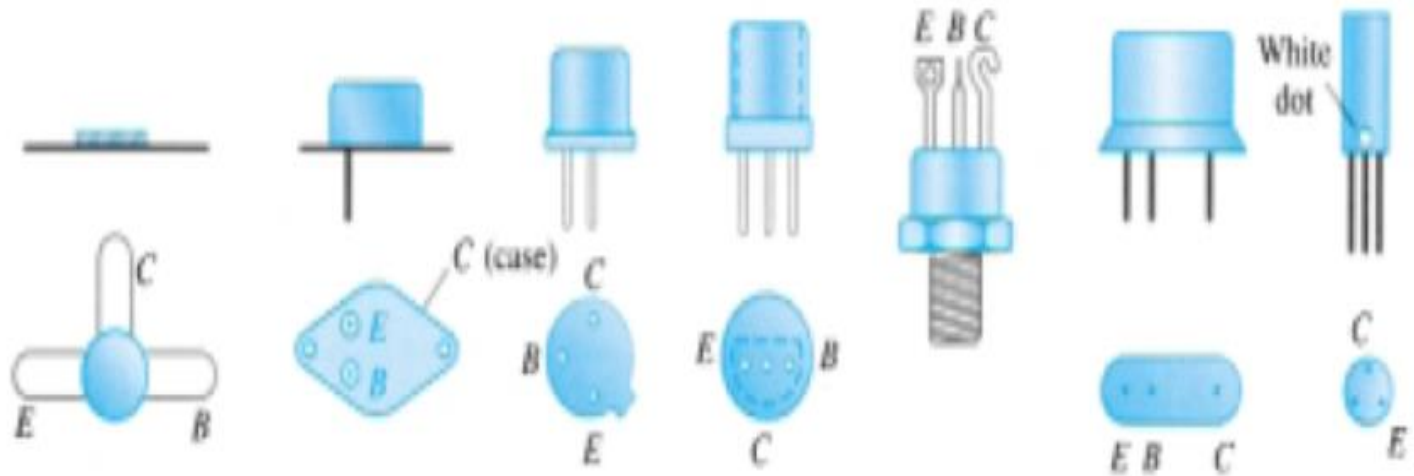


Figure 3.30 Transistor terminal identification.

# Transistor tester: Use of Ohmmeter

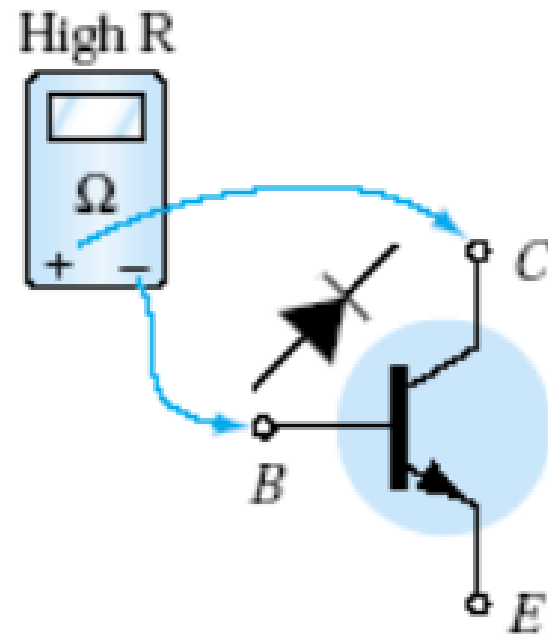

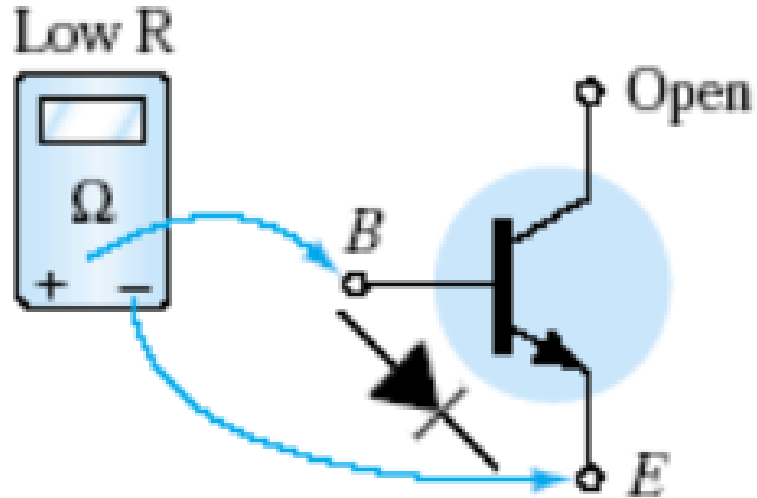

THANKS