

Biasing a BJT

Text Book

Electronic Devices and Circuit Theory

by R Boylestad and L Nashelsky


Basic relationships

$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

Operating point (Q-point)

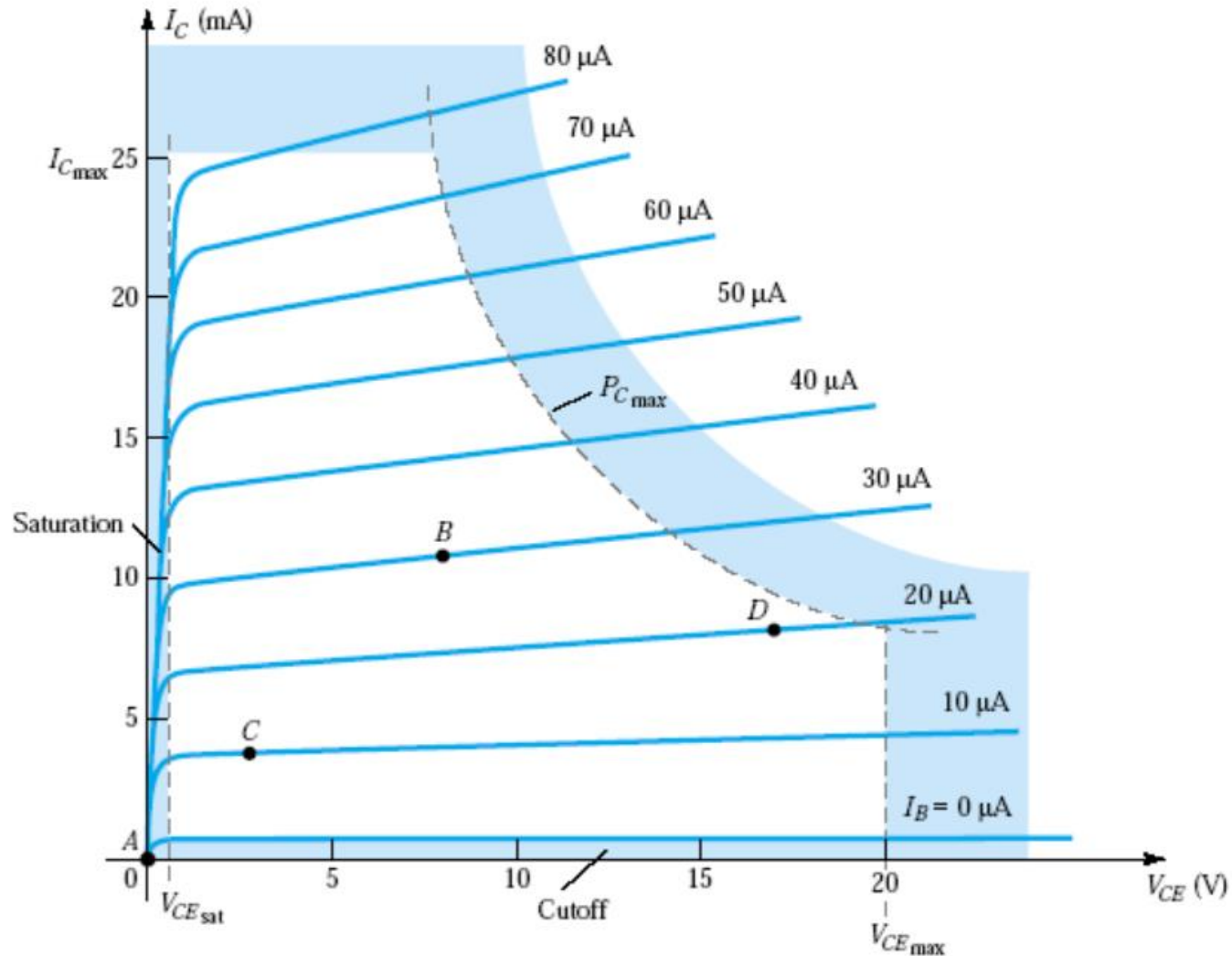

Biasing requirement

For amplification:

1. *Linear-region operation:*
Base–emitter junction forward biased
Base–collector junction reverse biased

For switching:

2. *Cutoff-region operation:*
Base–emitter junction reverse biased
3. *Saturation-region operation:*
Base–emitter junction forward biased
Base–collector junction forward biased

Fixed-bias circuit


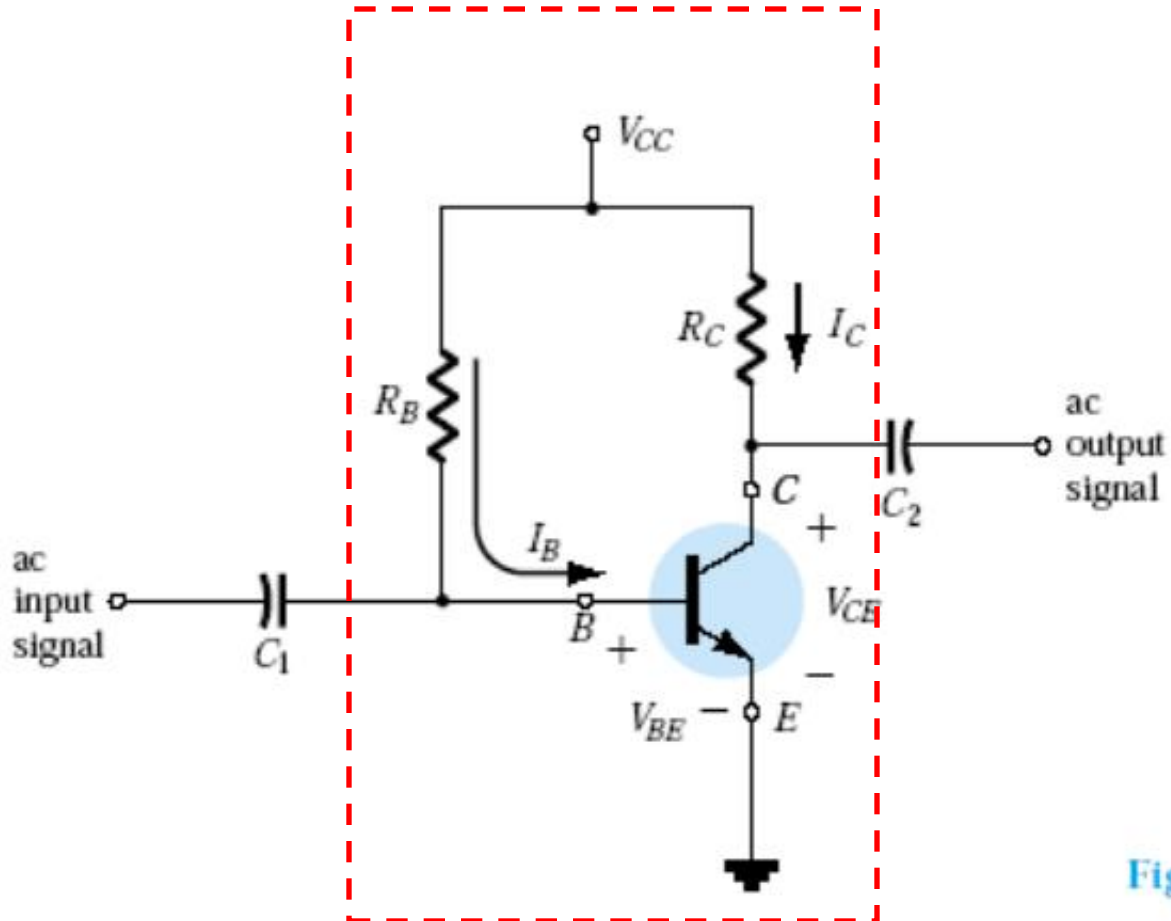
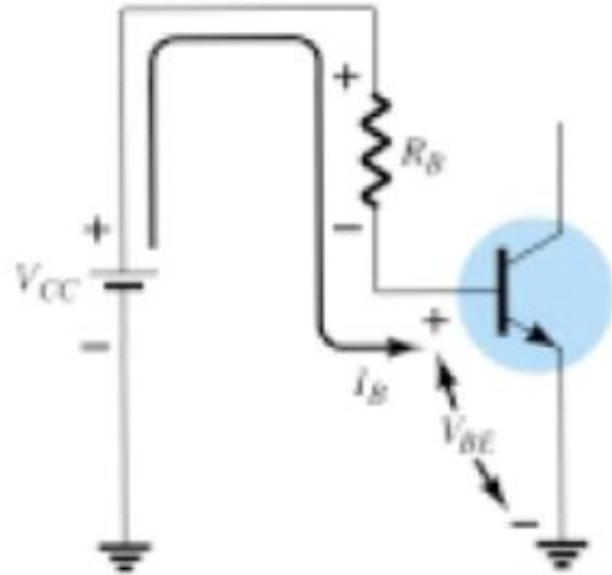


Figure 4.2

Dc analysis steps

- Open all capacitors first
- Redraw the input circuit or loop
- Apply KVL around the input loop and find I_B .
- Find I_C by using $I_C = \beta I_B$
- Apply KVL to the output loop and find V_{CE} .

Dc analysis

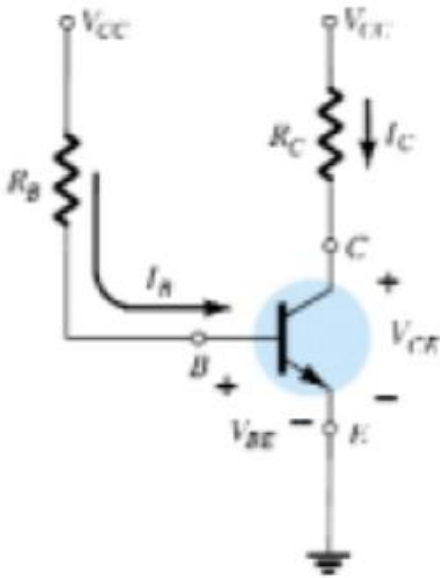

Applying KVL @ input loop:

$$+V_{CC} - I_B R_B - V_{BE} = 0$$

Hence,

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

Dc analysis (continue..)

Therefore,

$$I_C = \beta I_B$$


Applying KVL @ output loop:

$$V_{CE} + I_C R_C - V_{CC} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$

Since,

$$V_{CE} = V_C - V_E$$

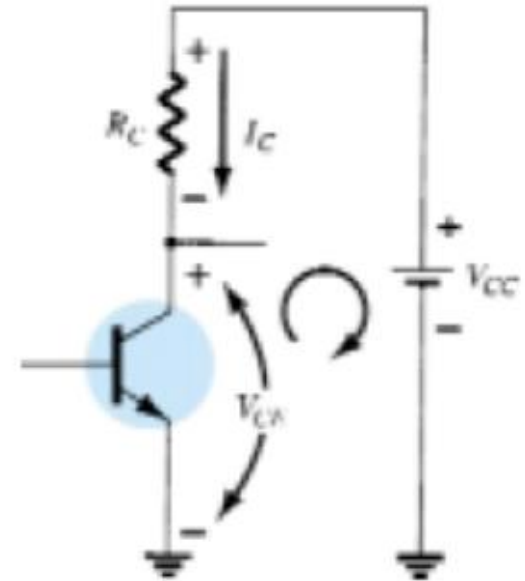


$$V_{CE} = V_C$$

$$V_{BE} = V_B - V_E$$

$$V_{BE} = V_B$$

Dc load line of fixed bias circuit

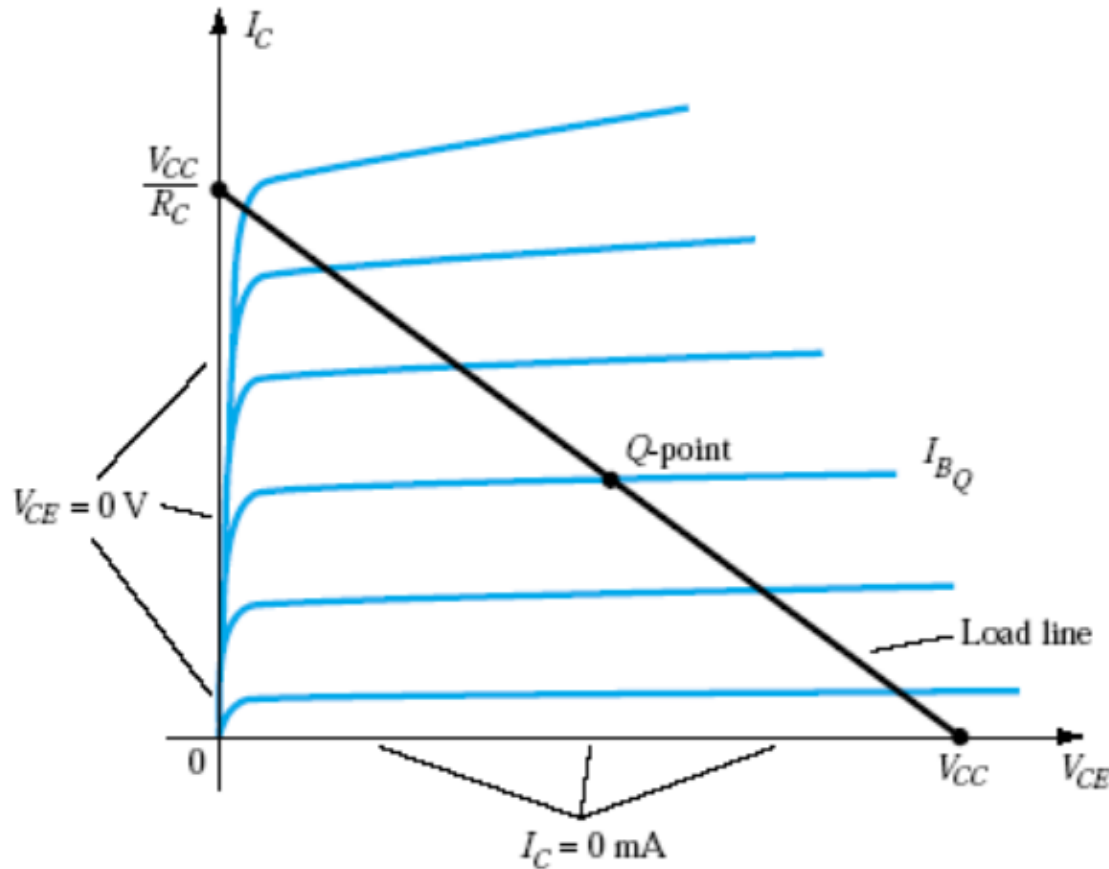

$$V_{CE} = V_{CC} - I_C R_C$$

On the y-axis:

$$0 = V_{CC} - I_C R_C$$


$$I_C = V_{CC} / R_C$$

On the x-axis:


$$V_{CE} = V_{CC} - 0 * R_C$$

$$V_{CE} = V_{CC}$$

Effect of R_B variation

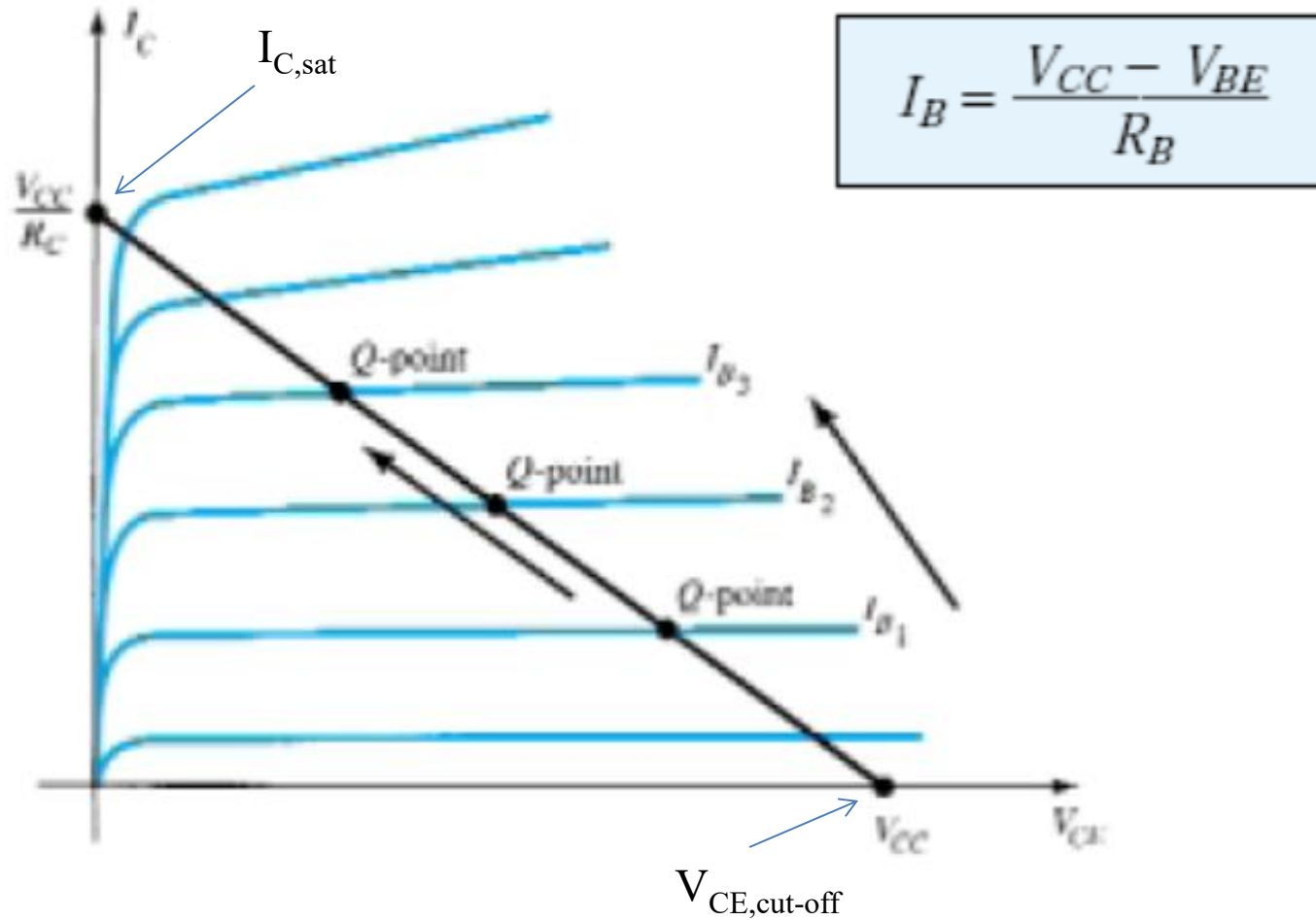


Effect of R_C variation

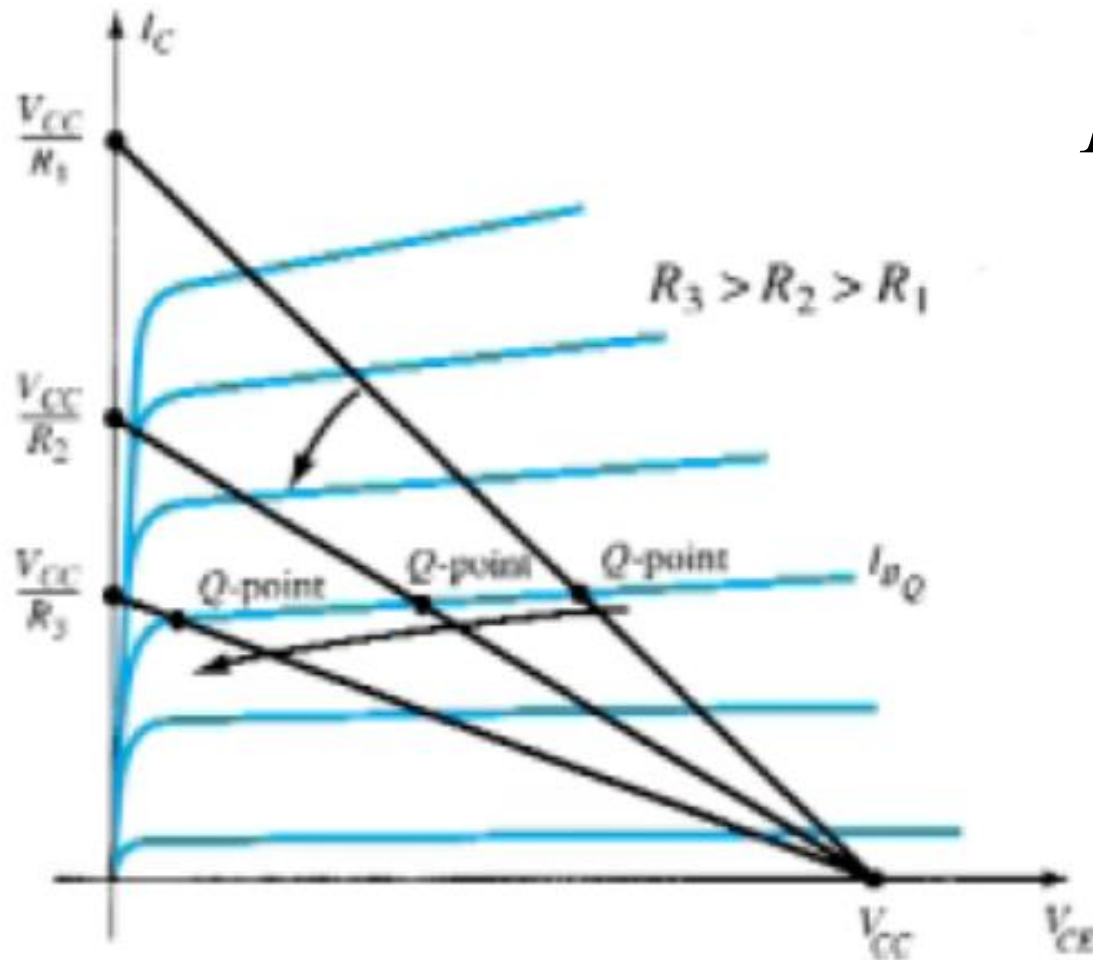


$$I_{C,sat} = \frac{V_{CC}}{R_C}$$


Effect of V_{CC} variation

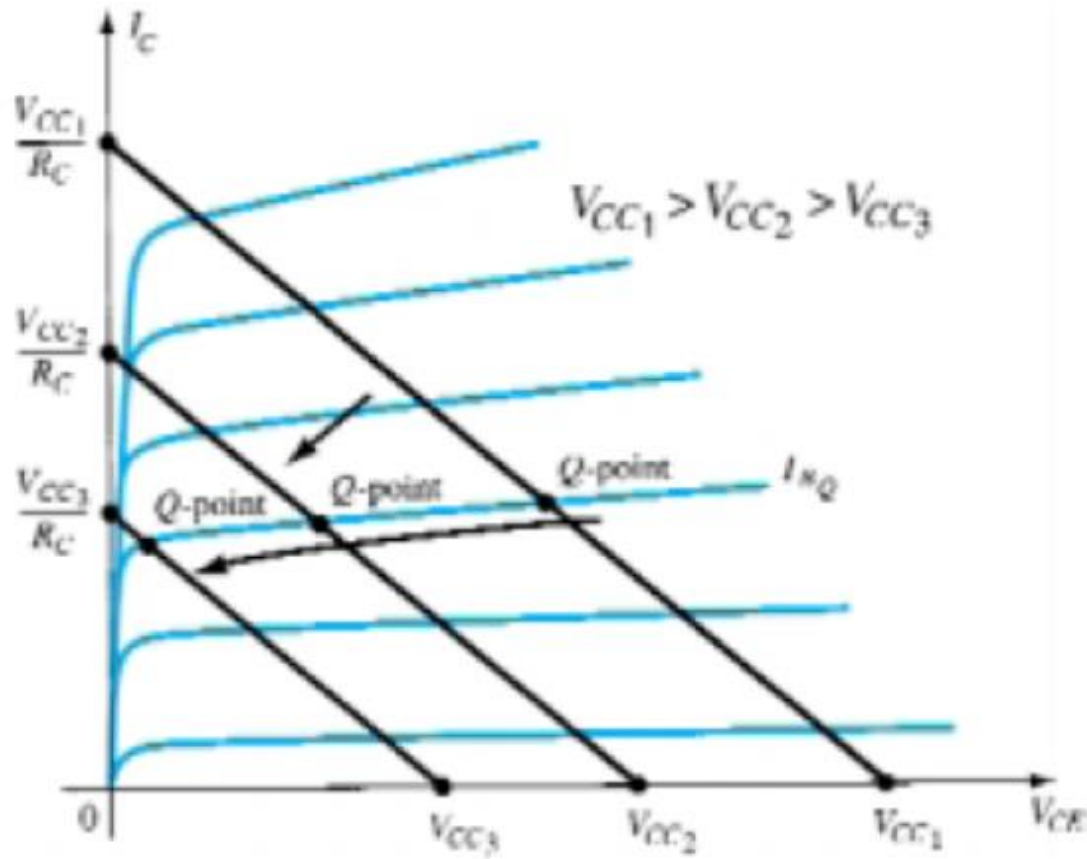

Distortion less maximum amplification

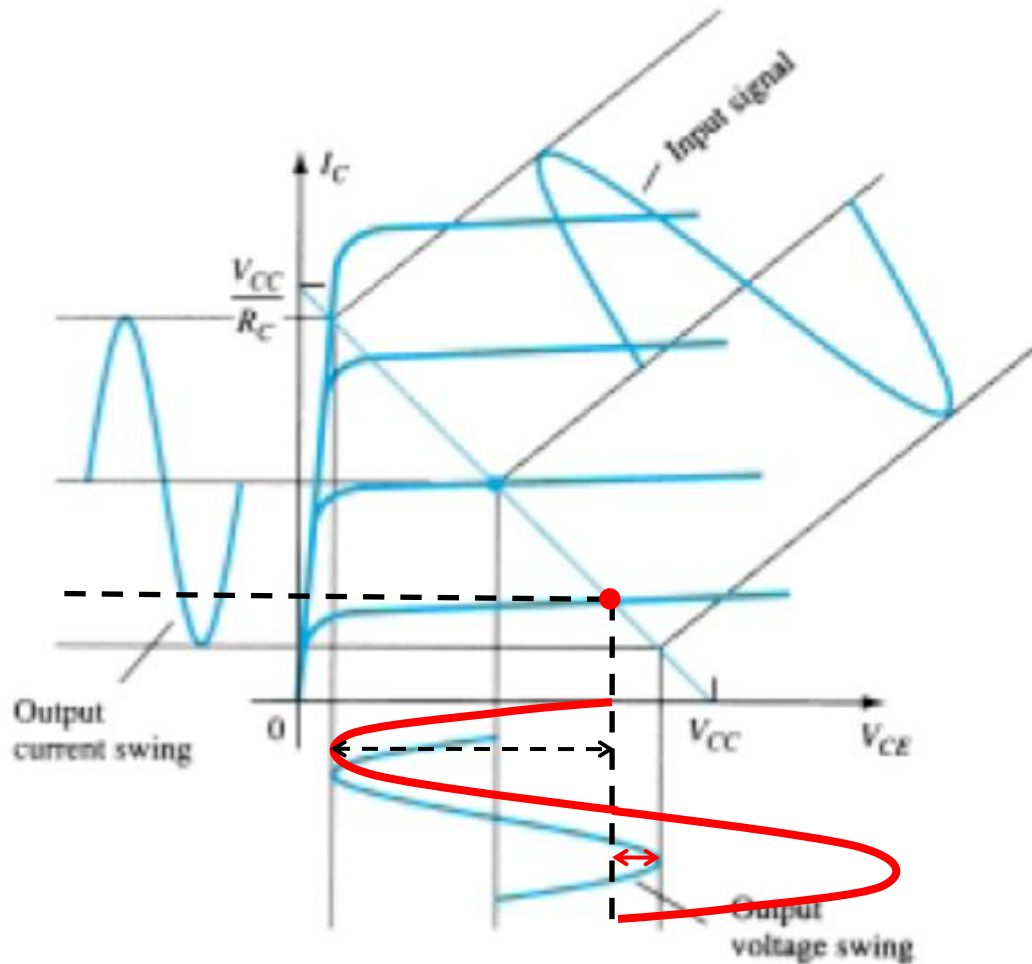

$$V_{CE} = \frac{1}{2} V_{CC}$$

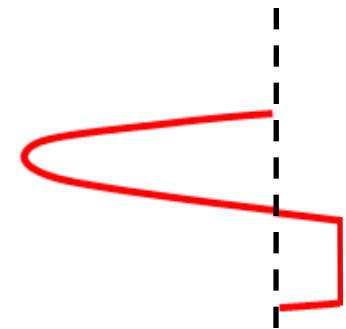

Example-1

Find: I_{BQ} , I_{CQ} , V_{CEQ} , V_B , V_C , V_{BC}

(a) Eq. (4.4): $I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{240 \text{ k}\Omega} = 47.08 \text{ }\mu\text{A}$


Eq. (4.5): $I_{CQ} = \beta I_{BQ} = (50)(47.08 \text{ }\mu\text{A}) = 2.35 \text{ mA}$

(b) Eq. (4.6): $V_{CEQ} = V_{CC} - I_C R_C$
 $= 12 \text{ V} - (2.35 \text{ mA})(2.2 \text{ k}\Omega)$
 $= 6.83 \text{ V}$


(c) $V_B = V_{BE} = 0.7 \text{ V}$
 $V_C = V_{CE} = 6.83 \text{ V}$

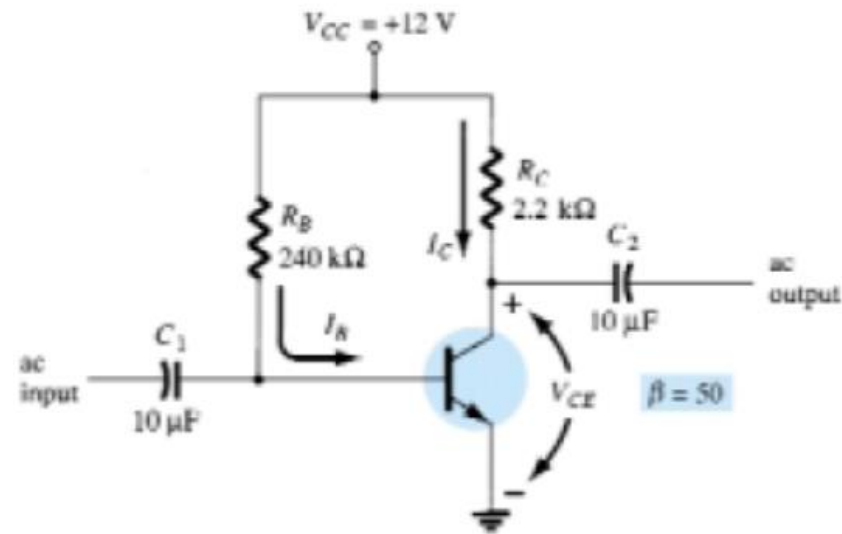(d) Using double-subscript notation yields

$$V_{BC} = V_B - V_C = 0.7 \text{ V} - 6.83 \text{ V}$$
$$= -6.13 \text{ V}$$



Emitter stabilized bias circuit

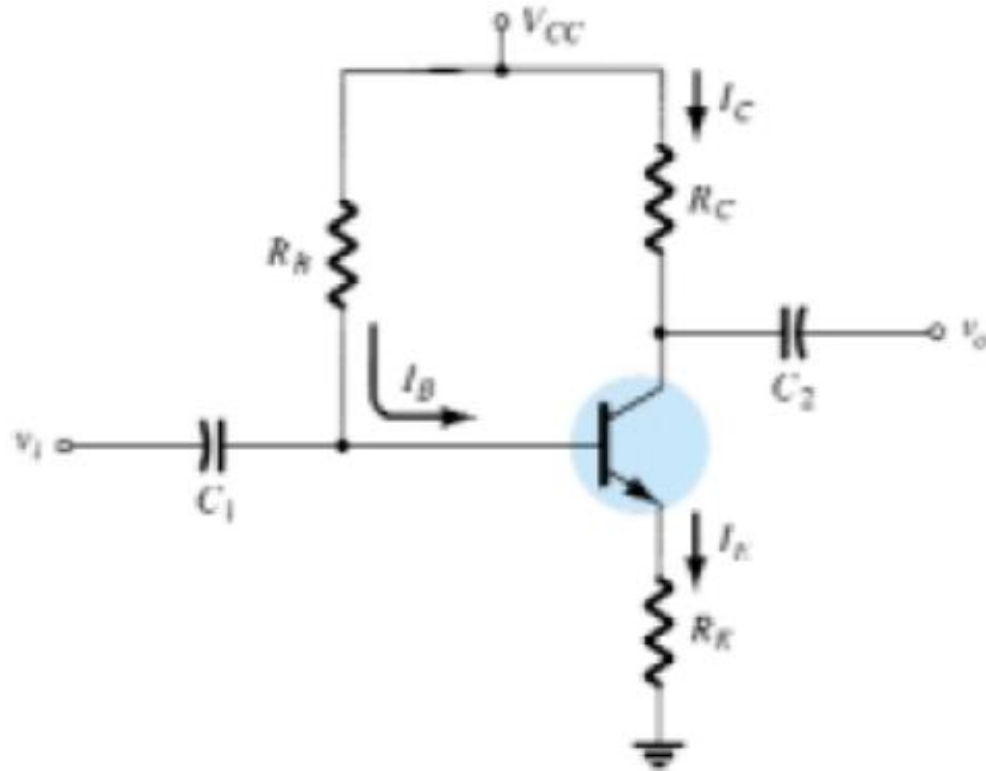

Analysis (input-loop)


Applying KVL @ input loop:

$$+V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

We know, $I_E = (\beta + 1)I_B$

$$V_{CC} - I_B R_B - V_{BE} - (\beta + 1)I_B R_E = 0$$
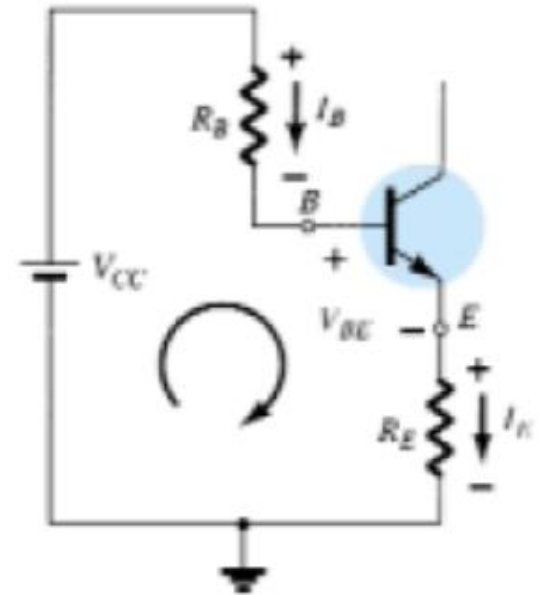
$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$



We want to reduce the effect of beta in the base current which will lead to the less effect on collector current. This can be done by choosing $R_E \gg R_B$ and $\beta + 1 \approx \beta$. Because as $I_C = \beta I_B$, so β term will be cancelled in the output parameter like in I_C Equation. That's how R_E is stabilizing the previous bias configuration.

Analysis (output-loop)

Applying KVL @ output loop:

$$+I_E R_E + V_{CE} + I_C R_C - V_{CC} = 0$$

$$V_{CE} - V_{CC} + I_C (R_C + R_E) = 0$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Now,


$$V_E = I_E R_E$$

Since. $V_{CE} = V_C - V_E$

$$V_C = V_{CE} + V_E$$

Or,

$$V_C = V_{CC} - I_C R_C$$

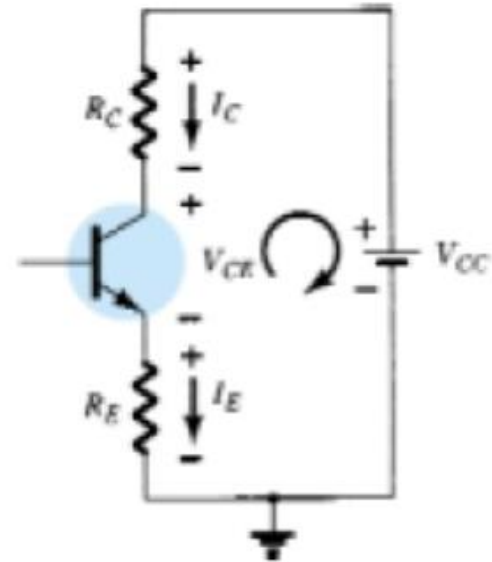


Again,

$$V_B = V_{CC} - I_B R_B$$

Or,

$$V_B = V_{BE} + V_E$$

Dc load line

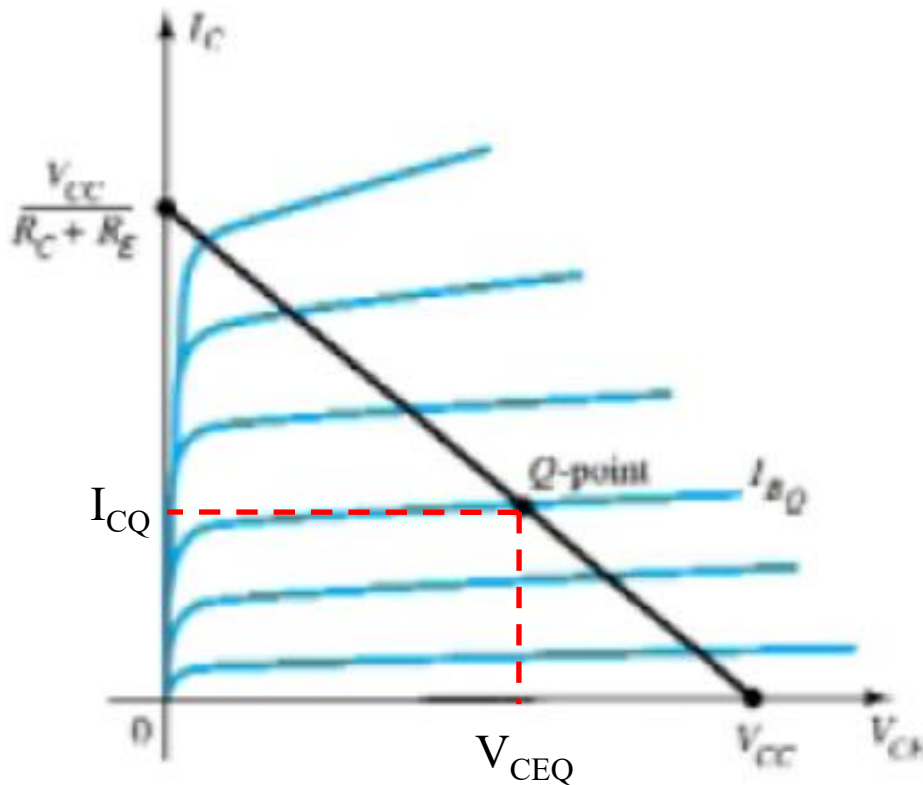

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

On the y-axis:

$$0 = V_{CC} - I_C(R_C + R_E)$$

$$I_C = V_{CC} / (R_C + R_E)$$


On the x-axis:

$$V_{CE} = V_{CC} - 0 * I_C(R_C + R_E)$$

$$V_{CE} = V_{CC}$$

Example-2

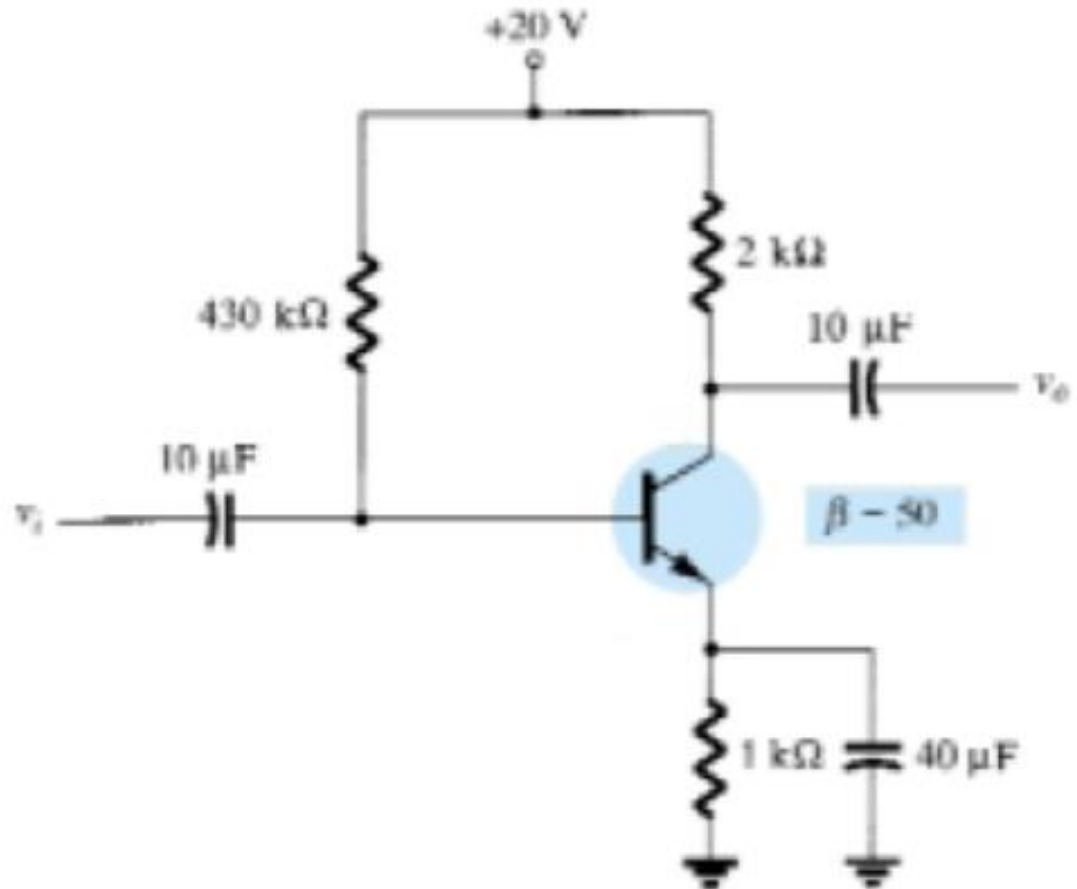- (a) I_B .
- (b) I_C .
- (c) V_{CE} .
- (d) V_C .
- (e) V_E .
- (f) V_B .
- (g) V_{BC} .



Solution

$$\begin{aligned} \text{(a) Eq. (4.17): } I_B &= \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} = \frac{20 \text{ V} - 0.7 \text{ V}}{430 \text{ k}\Omega + (51)(1 \text{ k}\Omega)} \\ &= \frac{19.3 \text{ V}}{481 \text{ k}\Omega} = \mathbf{40.1 \text{ }\mu\text{A}} \end{aligned}$$

$$\begin{aligned} \text{(b) } I_C &= \beta I_B \\ &= (50)(40.1 \text{ }\mu\text{A}) \\ &\cong \mathbf{2.01 \text{ mA}} \end{aligned}$$

$$\begin{aligned} \text{(c) Eq. (4.19): } V_{CE} &= V_{CC} - I_C(R_C + R_E) \\ &= 20 \text{ V} - (2.01 \text{ mA})(2 \text{ k}\Omega + 1 \text{ k}\Omega) = 20 \text{ V} - 6.03 \text{ V} \\ &= \mathbf{13.97 \text{ V}} \end{aligned}$$

$$\begin{aligned} \text{(d) } V_C &= V_{CC} - I_C R_C \\ &= 20 \text{ V} - (2.01 \text{ mA})(2 \text{ k}\Omega) = 20 \text{ V} - 4.02 \text{ V} \\ &= \mathbf{15.98 \text{ V}} \end{aligned}$$


$$\begin{aligned} \text{(e) } V_E &= V_C - V_{CE} \\ &= 15.98 \text{ V} - 13.97 \text{ V} \\ &= \mathbf{2.01 \text{ V}} \end{aligned}$$

$$\begin{aligned} \text{or } V_E &= I_E R_E \cong I_C R_E \\ &= (2.01 \text{ mA})(1 \text{ k}\Omega) \\ &= \mathbf{2.01 \text{ V}} \end{aligned}$$



$$\begin{aligned} \text{(f) } V_B &= V_{BE} + V_E \\ &= 0.7 \text{ V} + 2.01 \text{ V} \\ &= \mathbf{2.71 \text{ V}} \end{aligned}$$

$$\begin{aligned} \text{(g) } V_{BC} &= V_B - V_C \\ &= 2.71 \text{ V} - 15.98 \text{ V} \\ &= \mathbf{-13.27 \text{ V}} \quad (\text{reverse-biased as required}) \end{aligned}$$


Voltage divider bias

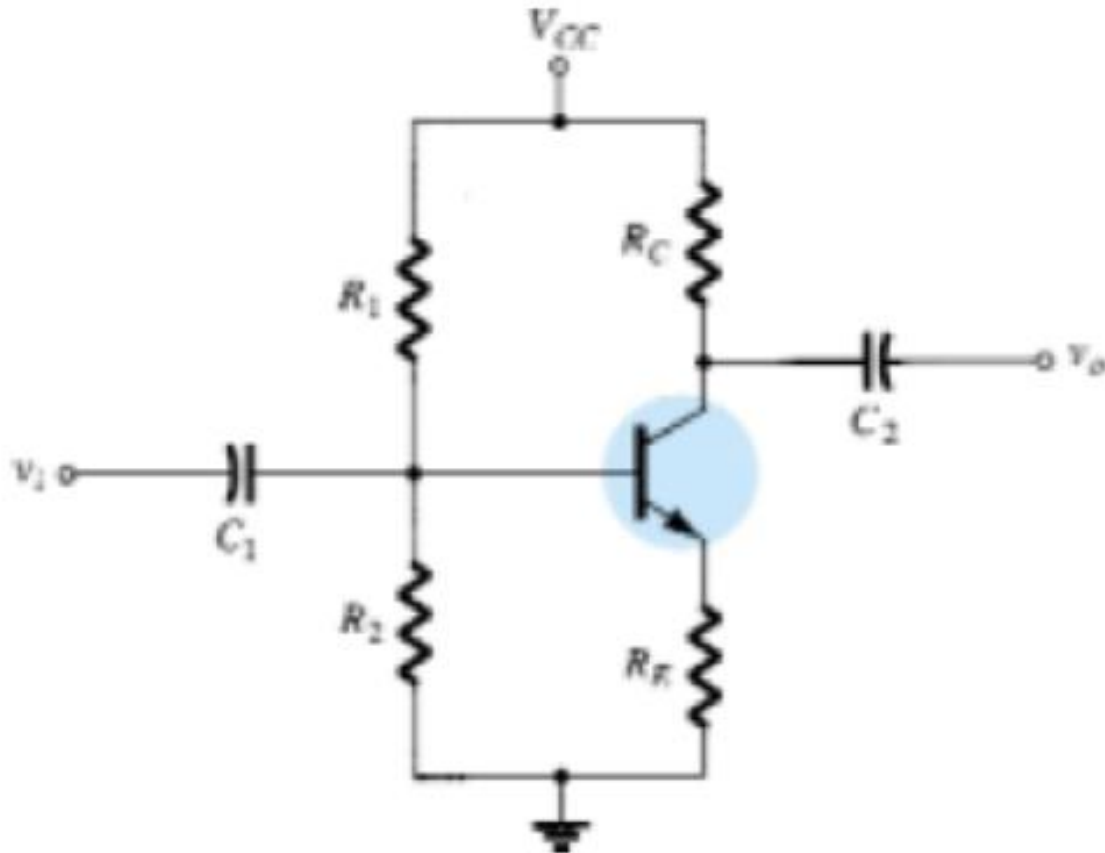

Input loop

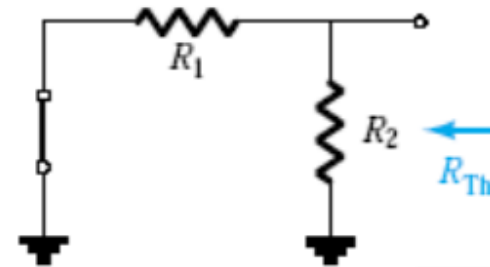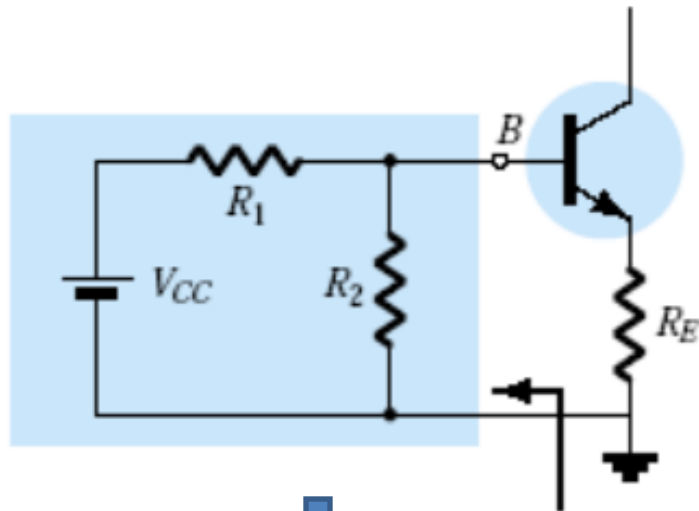

$$R_{Th} = R_1 || R_2$$

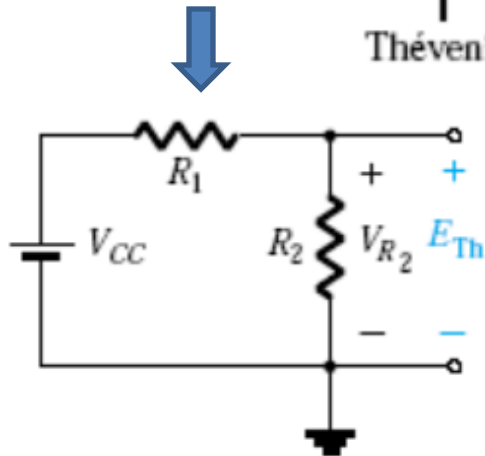

$$E_{Th} = V_{R_2} = \frac{R_2 V_{CC}}{R_1 + R_2}$$

Analysis (input loop)



Applying KVL @ input loop:

$$E_{Th} - I_B R_{Th} - V_{BE} - I_E R_E = 0$$

$$I_B = \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1)R_E}$$


Applying KVL @ output loop:

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

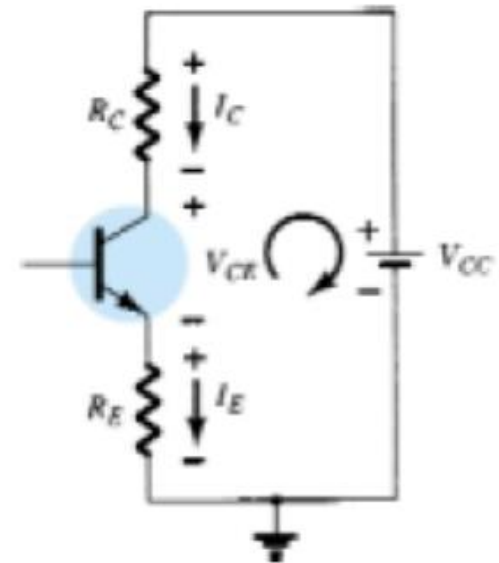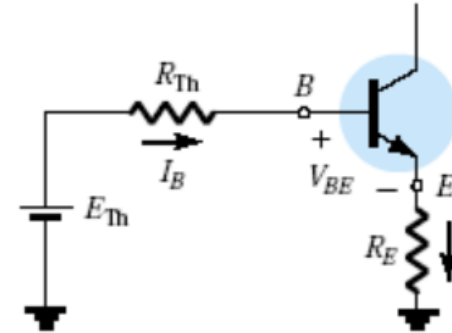

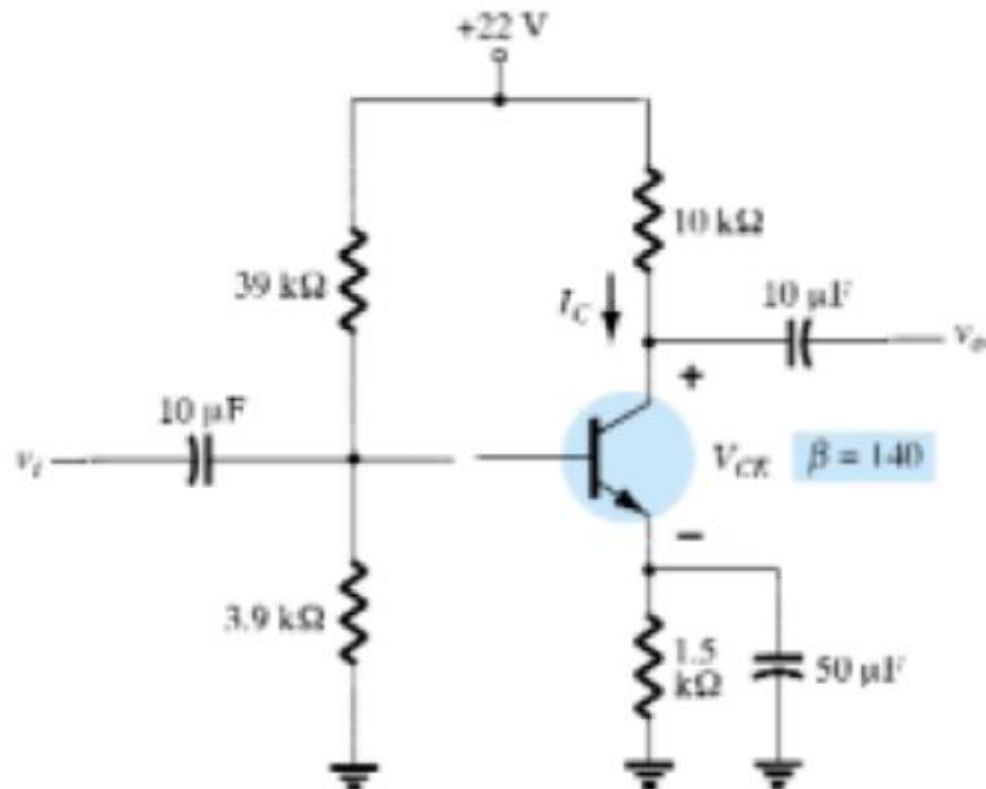Example-3

Determine the dc bias voltage V_{CE} and current I_C .



Solution

$$\begin{aligned}\text{Eq. (4.28): } R_{Th} &= R_1 \parallel R_2 \\ &= \frac{(39 \text{ k}\Omega)(3.9 \text{ k}\Omega)}{39 \text{ k}\Omega + 3.9 \text{ k}\Omega} = 3.55 \text{ k}\Omega\end{aligned}$$

$$\begin{aligned}\text{Eq. (4.29): } E_{Th} &= \frac{R_2 V_{CC}}{R_1 + R_2} \\ &= \frac{(3.9 \text{ k}\Omega)(22 \text{ V})}{39 \text{ k}\Omega + 3.9 \text{ k}\Omega} = 2 \text{ V}\end{aligned}$$

$$\begin{aligned}\text{Eq. (4.30): } I_B &= \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1)R_E} \\ &= \frac{2 \text{ V} - 0.7 \text{ V}}{3.55 \text{ k}\Omega + (141)(1.5 \text{ k}\Omega)} = \frac{1.3 \text{ V}}{3.55 \text{ k}\Omega + 211.5 \text{ k}\Omega} \\ &= 6.05 \text{ }\mu\text{A}\end{aligned}$$

$$\begin{aligned}I_C &= \beta I_B \\ &= (140)(6.05 \text{ }\mu\text{A}) \\ &= 0.85 \text{ mA}\end{aligned}$$

$$\begin{aligned}\text{Eq. (4.31): } V_{CE} &= V_{CC} - I_C(R_C + R_E) \\ &= 22 \text{ V} - (0.85 \text{ mA})(10 \text{ k}\Omega + 1.5 \text{ k}\Omega) \\ &= 22 \text{ V} - 9.78 \text{ V} \\ &= 12.22 \text{ V}\end{aligned}$$

Collector-Feedback conf.

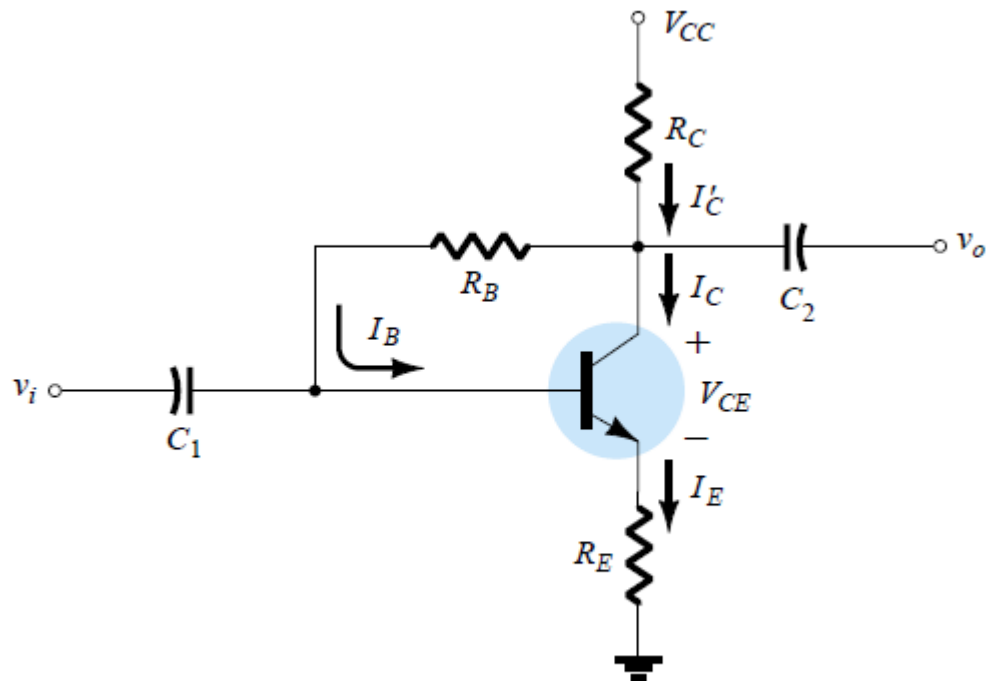


Figure 4.34 dc bias circuit with voltage feedback.

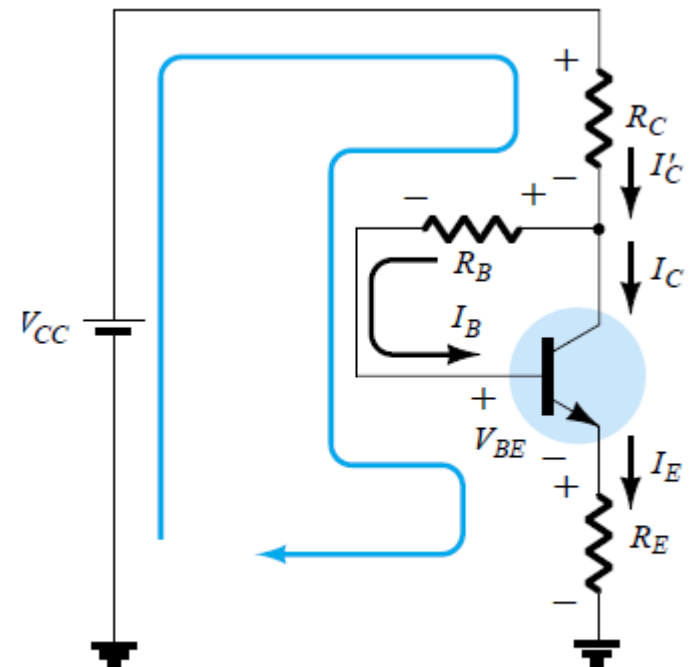


Figure 4.35 Base-emitter loop for the network of Fig. 4.34.

Collector-Emitter conf.

$$V_{CC} - I_C R_C - I_B R_B - V_{BE} - I_E R_E = 0$$

$$V_{CC} - \beta I_B R_C - I_B R_B - V_{BE} - \beta I_B R_E = 0$$

Gathering terms, we have

$$V_{CC} - V_{BE} - \beta I_B (R_C + R_E) - I_B R_B = 0$$

and solving for I_B yields

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)}$$

Collector–Emitter Loop

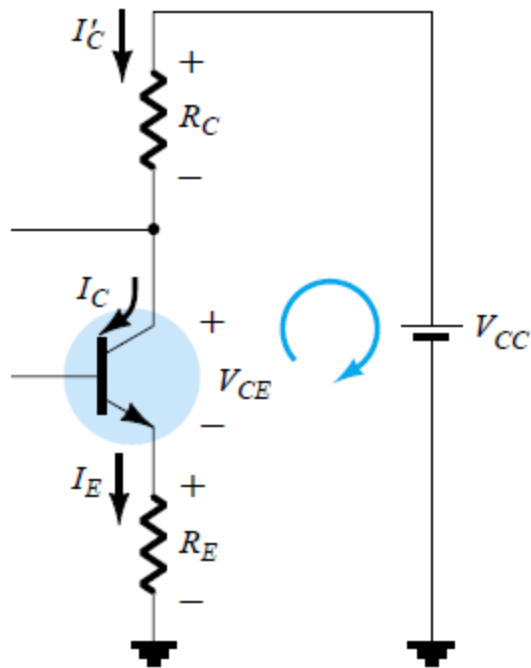


Figure 4.36 Collector–emitter loop for the network of Fig. 4.34.

Since $I'_C \cong I_C$ and $I_E \cong I_C$, we have

$$I_C(R_C + R_E) + V_{CE} - V_{CC} = 0$$

and

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

EXAMPLE 4.11

Determine the quiescent levels of I_{C_Q} and V_{CE_Q} for the network of Fig. 4.37.

Solution

$$\begin{aligned}\text{Eq. (4.41): } I_B &= \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)} \\ &= \frac{10 \text{ V} - 0.7 \text{ V}}{250 \text{ k}\Omega + (90)(4.7 \text{ k}\Omega + 1.2 \text{ k}\Omega)} \\ &= \frac{9.3 \text{ V}}{250 \text{ k}\Omega + 531 \text{ k}\Omega} = \frac{9.3 \text{ V}}{781 \text{ k}\Omega} \\ &= 11.91 \text{ }\mu\text{A}\end{aligned}$$

$$\begin{aligned}I_{C_Q} &= \beta I_B = (90)(11.91 \text{ }\mu\text{A}) \\ &= \mathbf{1.07 \text{ mA}}\end{aligned}$$

$$\begin{aligned}V_{CE_Q} &= V_{CC} - I_C(R_C + R_E) \\ &= 10 \text{ V} - (1.07 \text{ mA})(4.7 \text{ k}\Omega + 1.2 \text{ k}\Omega) \\ &= 10 \text{ V} - 6.31 \text{ V} \\ &= \mathbf{3.69 \text{ V}}\end{aligned}$$

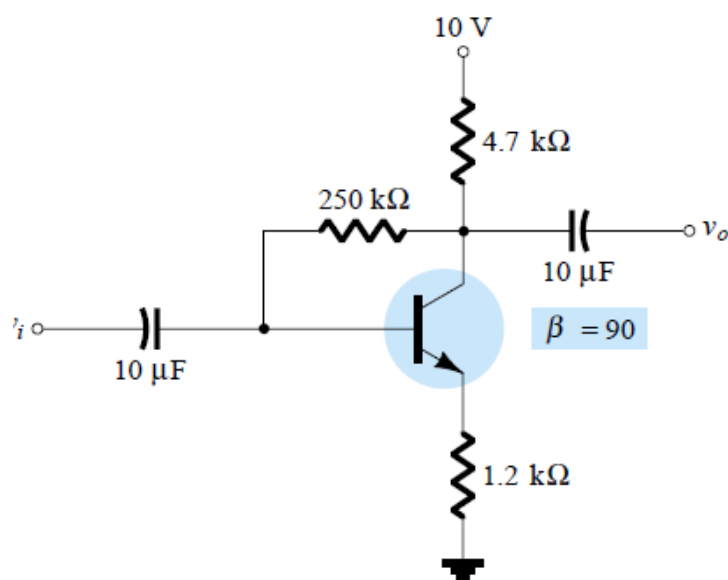


Figure 4.37 Network for Example 4.11.

Common-collector (emitter-follower) configuration

Determine V_{CEQ} and I_E for the network of Fig. 4.41.

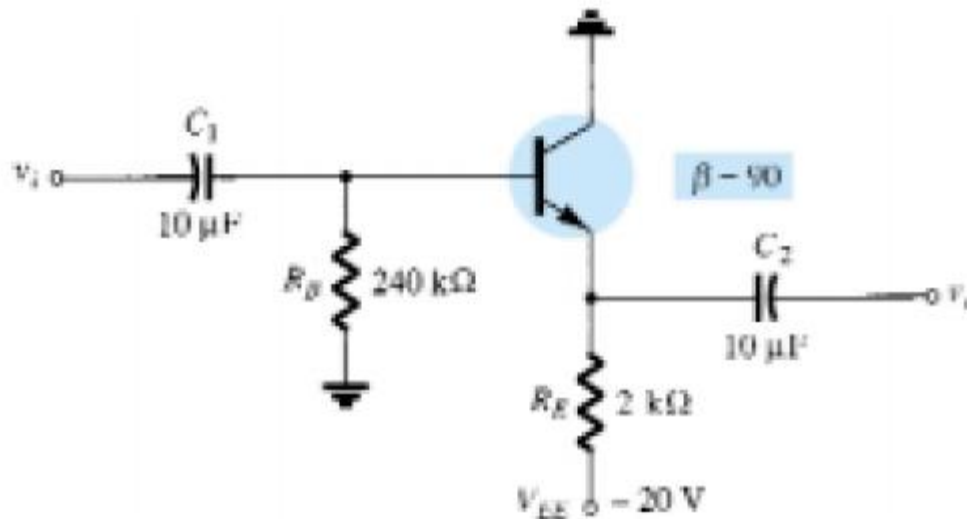


Figure 4.41 Common-collector (emitter-follower) configuration.

Common-base configuration.

EXAMPLE 4.17

Determine the voltage V_{CB} and the current I_B for the common-base configuration of Fig. 4.42.


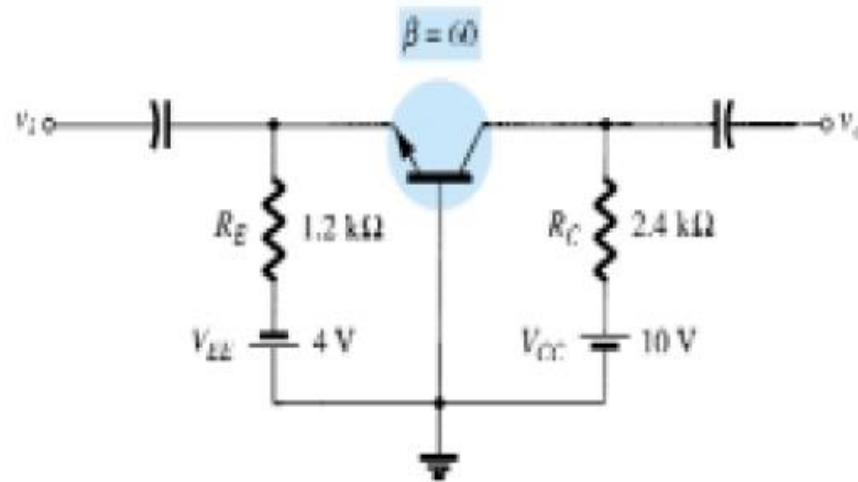


Figure 4.42 Common-base configuration.

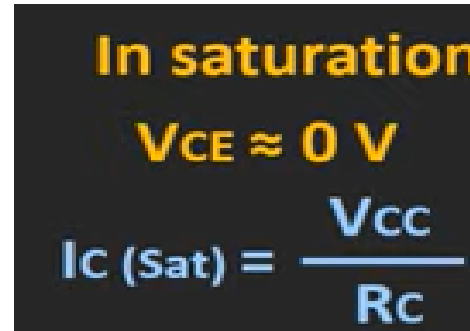Tricky question: Why the term Saturation comes?



In saturation

$V_{CE} \approx 0 \text{ V}$

$I_C (\text{Sat}) = \frac{V_{CC}}{R_C}$

This ($I_C(\text{sat})$) is the maximum current passing through the collector.

If $I_C > I_C(\text{sat})$ then the BJT will operate in saturation region.

That mean, I_C which is depending on the input side parameters, can not be greater than $I_C(\text{sat})$.

Practice yourself and send me
your feedback, if any.