


Md. Abdul Malek

Assistant Professor, Dept. of Electrical & Electronic Engineering (EEE)
Rajshahi University of Engineering & Technology (RUET)



Source Transformation

- Ideal voltage source have no internal resistance.

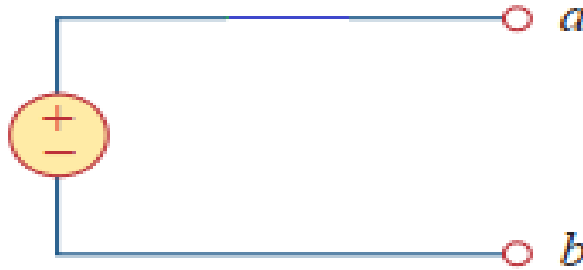- Practical voltage source v_s connected small internal resistance.



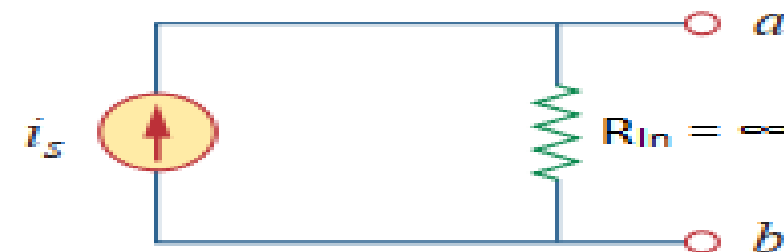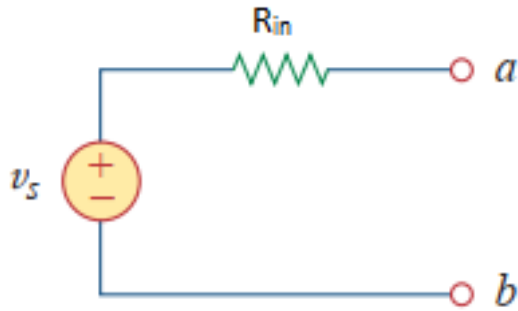- Ideal voltage source and internal resistance connected in series. Internal resistance connected in parallel. Value of internal resistance is infinite.



Source Transformation

- A voltage source in series with a resistor can be transformed to a current source in parallel with a resistor.
- A current source in parallel with a resistor can be transformed to a voltage source in series with a resistor.


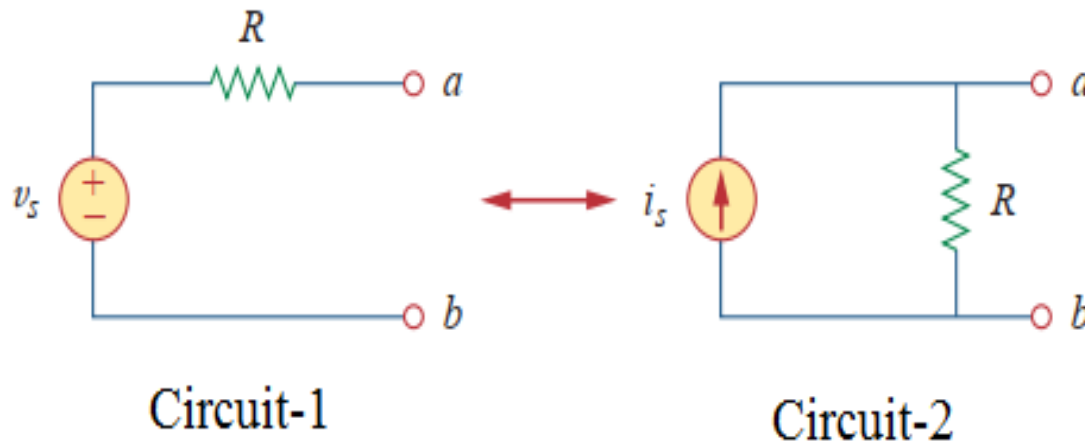



Fig. 4: Transformation of independent sources.

Source Transformation


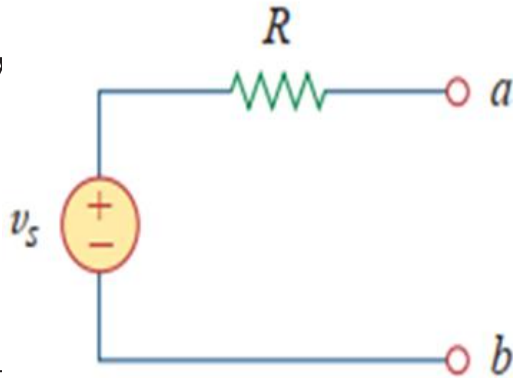
- The voltage source and the resistor in series can be replaced by a current source in parallel with the resistor.
- When the current source is defined as $i_s = v_s / R$, the two circuits will have the same open-circuit voltage and the same short-circuit current.



Circuit-1

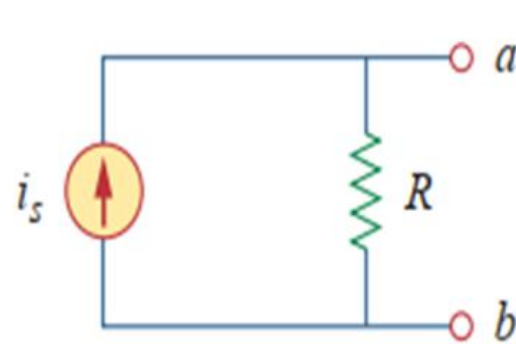

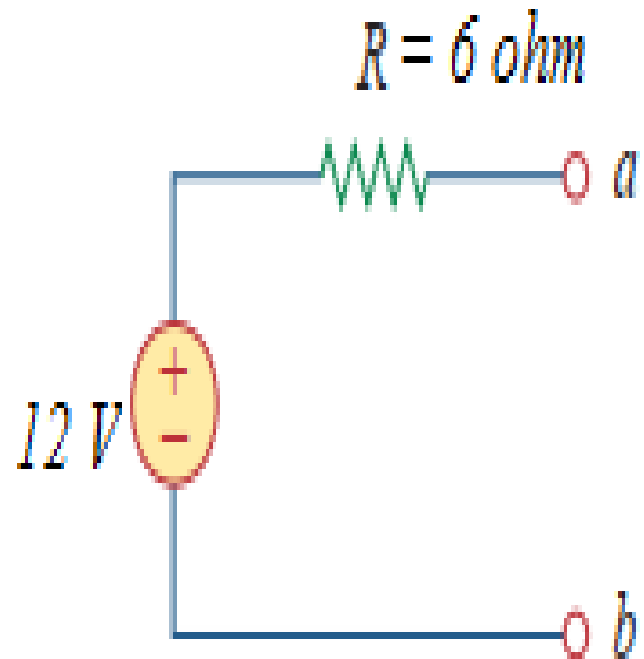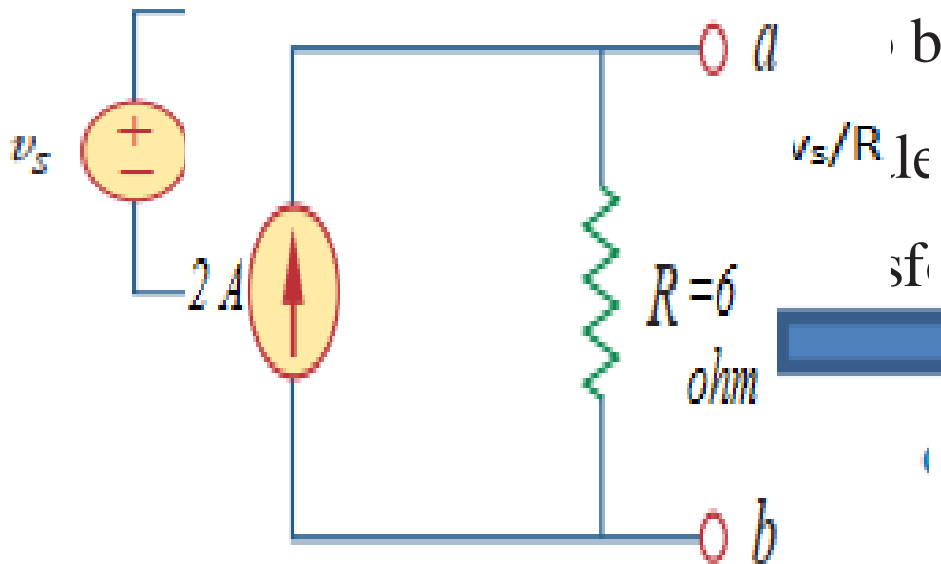will have the same open-circuit voltage and the same short-circuit current.




short-circuit current

Source Transformation

A source transformation is the process of replacing a voltage source v_s in series with a resistor R by a current source i_s in parallel with a resistor R , or vice versa.

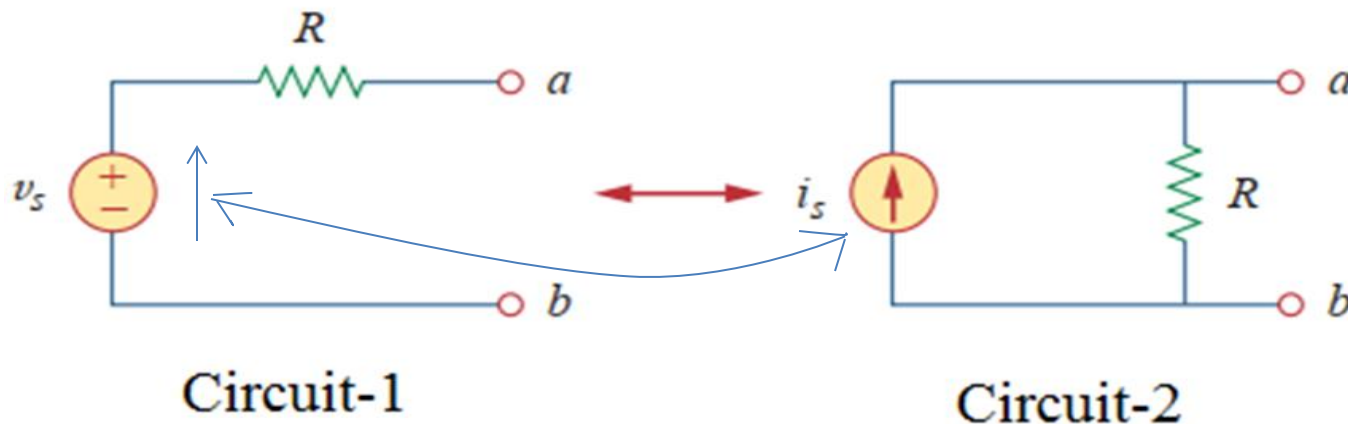- Source transformation is not possible when $R=0$.
- Arrow of the current source is directed toward the positive terminal of the voltage source.



Source Transformation

Problem: Use source transformation to find v_o in the circuit of Fig. 5.

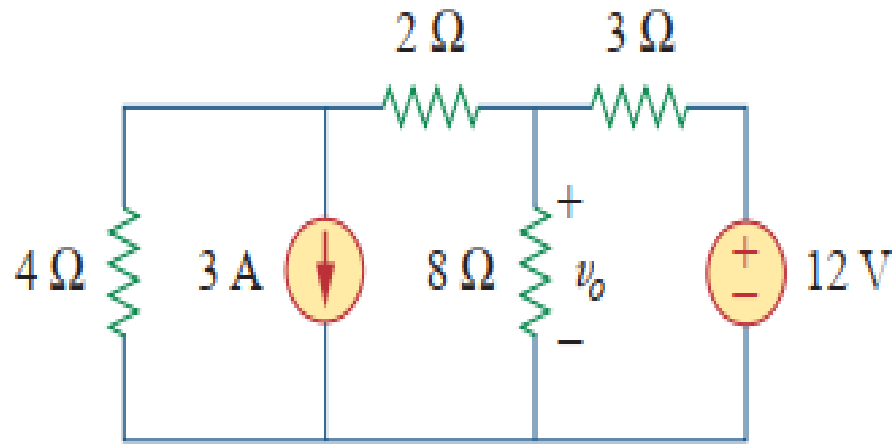


Fig. 5.

Source Transformation

Solution:

- First transform the 3 A current source to voltage sources and 12 V voltage source to current source. This circuit is shown in Fig. 6.


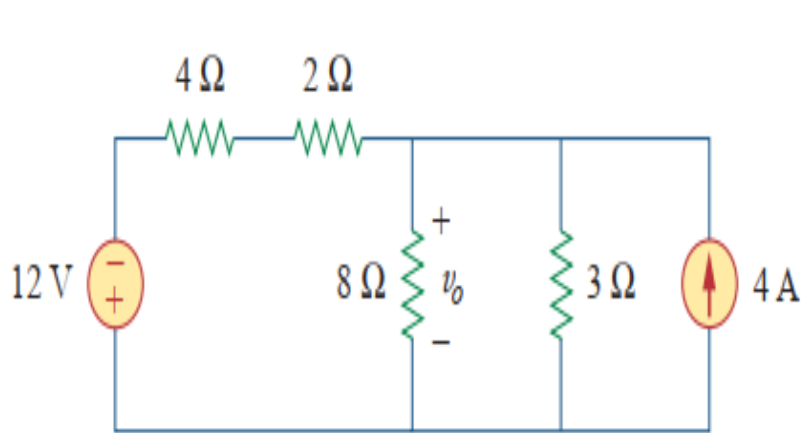


Fig. 6

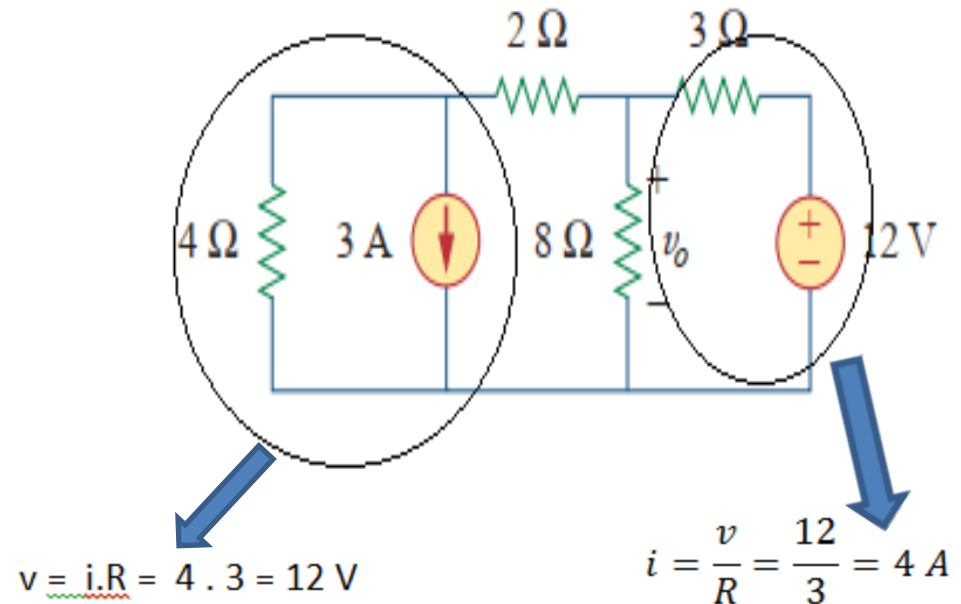

Source Transformation

- Combining $4\ \Omega$ and $2\ \Omega$ the resistors and obtain $6\ \Omega$ resistors (shown in Fig. 7).


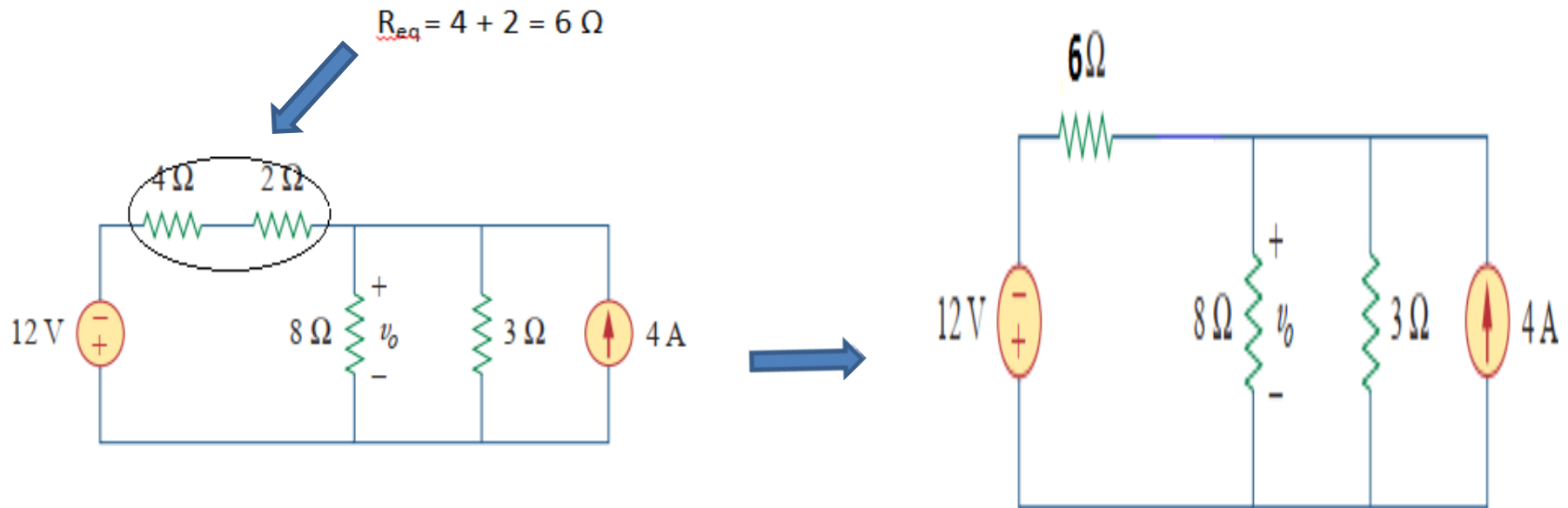


Fig. 7

Source Transformation


Solution:

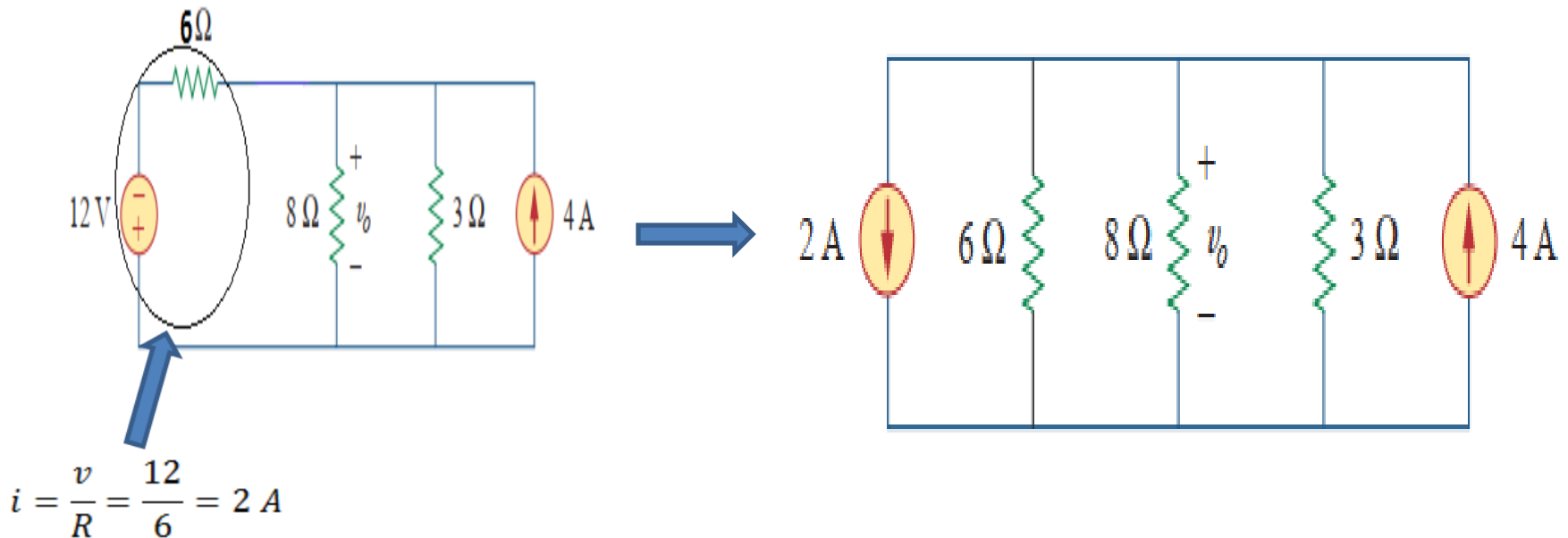- Transforming the 12-V voltage source and 6 Ω resistor to 2 A Current source in parallel with 6 Ω resistors.




Source Transformation

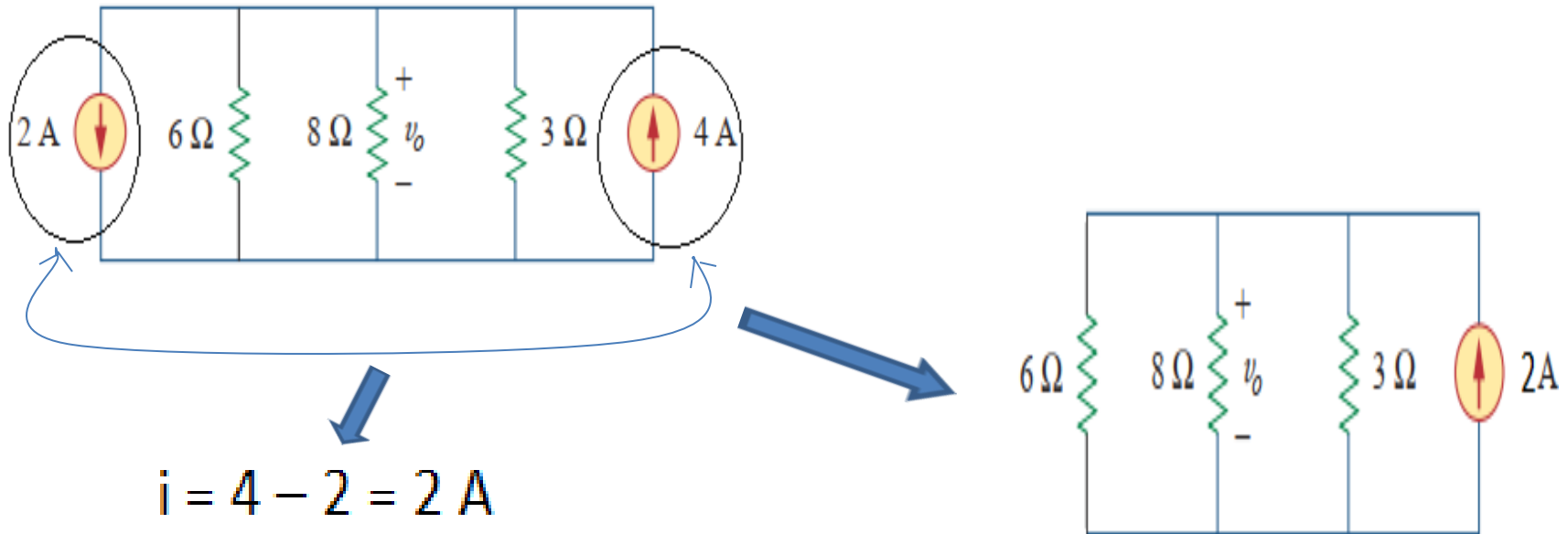- Combine the 2 A and 4 A current sources to get a 2 A source



Source Transformation

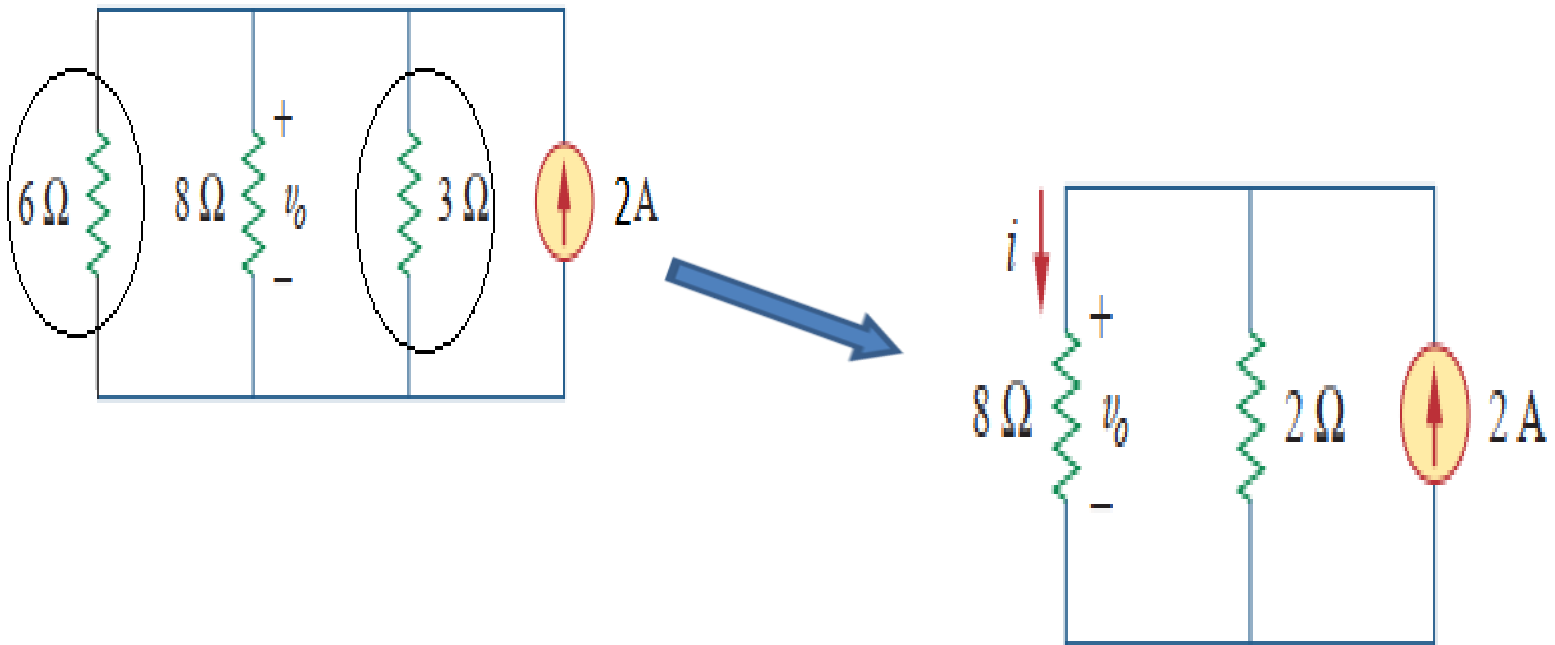- Combining the parallel connected $6\ \Omega$ and $3\ \Omega$ the resistors to get $2\ \Omega$ resistors.




Source Transformation

- We use current divider rule to get i

$$i = \frac{2}{2 + 8}(2) = 0.4 \text{ A}$$

- Voltage v_o is

$$v_o = 8i = 8(0.4) = 3.2 \text{ V}$$

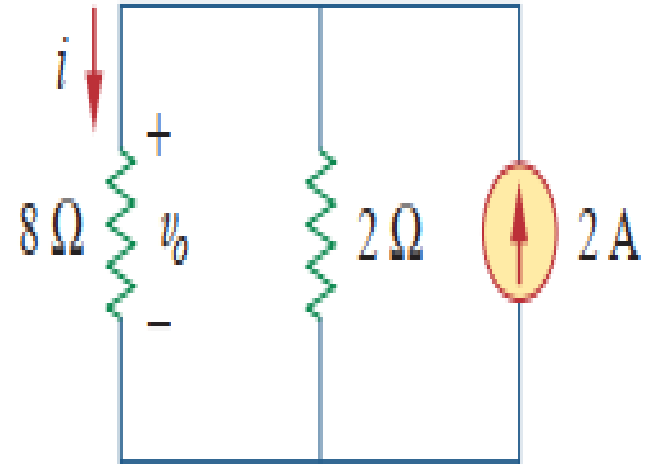

Thank You