

FET

AC small signal analysis

Text Book

Electronic Devices and Circuit Theory

by R Boylestad and L Nashelsky

Basics on FET Amplifier

- Field-effect transistor amplifiers provide an excellent voltage gain with the added feature of a high input impedance.
- They are also considered low-power consumption configurations with good frequency range and minimal size and weight.
- Because of the high input characteristic of FETs, the ac equivalent model is somewhat simpler than that employed for BJTs.
- BJT had an amplification factor β (beta), the FET has a transconductance factor, g_m .

JFET small signal model

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

Graphical Determination of g_m

$$g_m = m = \frac{\Delta y}{\Delta x} = \frac{\Delta I_D}{\Delta V_{GS}}$$

 


Figure 9.1 Definition of g_m using transfer characteristic.

FET small signal model

Mathematical Definition of g_m


$$\begin{aligned} g_m &= \left. \frac{\Delta I_D}{\Delta V_{GS}} \right|_{Q\text{-pt.}} = \left. \frac{dI_D}{dV_{GS}} \right|_{Q\text{-pt.}} = \frac{d}{dV_{GS}} \left[I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \right] \\ &= I_{DSS} \frac{d}{dV_{GS}} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = 2I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right] \frac{d}{dV_{GS}} \left(1 - \frac{V_{GS}}{V_P} \right) \\ &= 2I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right] \left[\frac{d}{dV_{GS}} (1) - \frac{1}{V_P} \frac{dV_{GS}}{dV_{GS}} \right] = 2I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right] \left[0 - \frac{1}{V_P} \right] \end{aligned}$$

$$g_m = \frac{2I_{DSS}}{|V_P|} \left[1 - \frac{V_{GS}}{V_P} \right]$$


$$g_m = \frac{2I_{DSS}}{|V_P|} \left[1 - \frac{0}{V_P} \right]$$

$$g_{m0} = \frac{2I_{DSS}}{|V_P|}$$

JFET AC equivalent circuit/model

 


Fixed bias circuit (JFET and D-MOSFET)

 

Voltage gain,
 $A_V = -g_m R_D$

$$\left| \begin{array}{l} Z_i = R_G \quad \Omega \\ Z_o = r_d \parallel R_D \cong R_D \quad \Omega \end{array} \right.$$

 

Voltage gain

$$V_o = -g_m V_{gs} (r_d \parallel R_D)$$

$$V_{gs} = V_i$$


$$V_o = -g_m V_i (r_d \parallel R_D)$$

$$A_v = \frac{V_o}{V_i} = -g_m (r_d \parallel R_D)$$

$$A_v = \frac{V_o}{V_i} = -g_m R_D$$

$$r_d \geq 10 R_D$$

Example-3

 

$$(a) \quad g_{m0} = \frac{2I_{DSS}}{|V_P|} = \frac{2(10 \text{ mA})}{8 \text{ V}} = 2.5 \text{ mS}$$

$$g_m = g_{m0} \left(1 - \frac{V_{GS_Q}}{V_P} \right) = 2.5 \text{ mS} \left(1 - \frac{(-2 \text{ V})}{(-8 \text{ V})} \right) = \mathbf{1.88 \text{ mS}}$$

$$(b) \quad r_d = \frac{1}{y_{os}} = \frac{1}{40 \mu\text{S}} = \mathbf{25 \text{ k}\Omega}$$

$$(c) \quad Z_i = R_G = \mathbf{1 \text{ M}\Omega}$$

$$(d) \quad Z_o = R_D \parallel r_d = 2 \text{ k}\Omega \parallel 25 \text{ k}\Omega = \mathbf{1.85 \text{ k}\Omega}$$

$$(e) \quad A_v = -g_m(R_D \parallel r_d) = -(1.88 \text{ mS})(1.85 \text{ k}\Omega) \\ = \mathbf{-3.48}$$

$$(f) \quad A_v = -g_m R_D = -(1.88 \text{ mS})(2 \text{ k}\Omega) = \mathbf{-3.76}$$

JFET SELF-BIAS CONFIGURATION (Bypassed R_S)


 


Figure 9.15 Self-bias JFET configuration

 JFET SELF-BIAS CONFIGURATION (Bypassed R_S)



$$Z_i = R_G$$

Z_o :

$$Z_o = r_d \parallel R_D$$

If $r_d \geq 10R_D$,

$$Z_o \cong R_D$$

$r_d \geq 10R_D$


A_v :

$$A_v = -g_m(r_d \parallel R_D)$$

If $r_d \geq 10R_D$,

$$A_v = -g_m R_D$$

$r_d \geq 10R_D$

 

Voltage divider bias


 


Figure 9.21 JFET voltage-divider configuration.

 

DEPLETION-TYPE MOSFETs

 


Figure 9.33 D-MOSFET ac equivalent model.

ENHANCEMENT-TYPE MOSFETs

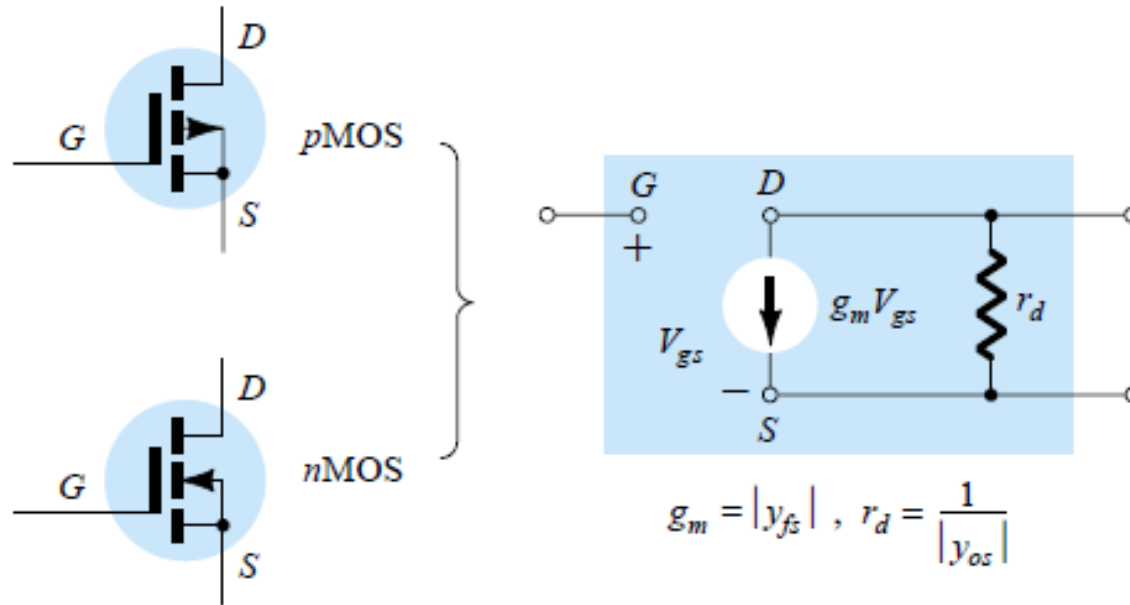


Figure 9.36 Enhancement MOSFET ac small-signal model.

Practice yourself by including other remaining configurations and send me your feedback, if any.